

## Electronic circuit - I (ECE2101)

Group Assignment (Group of 5 students maximum , Due date: 26/04/2023)

1. For the circuit shown below in Figure 1, Calculate  $I_B$ ,  $I_C$ ,  $I_E$  and  $V_{CE}$

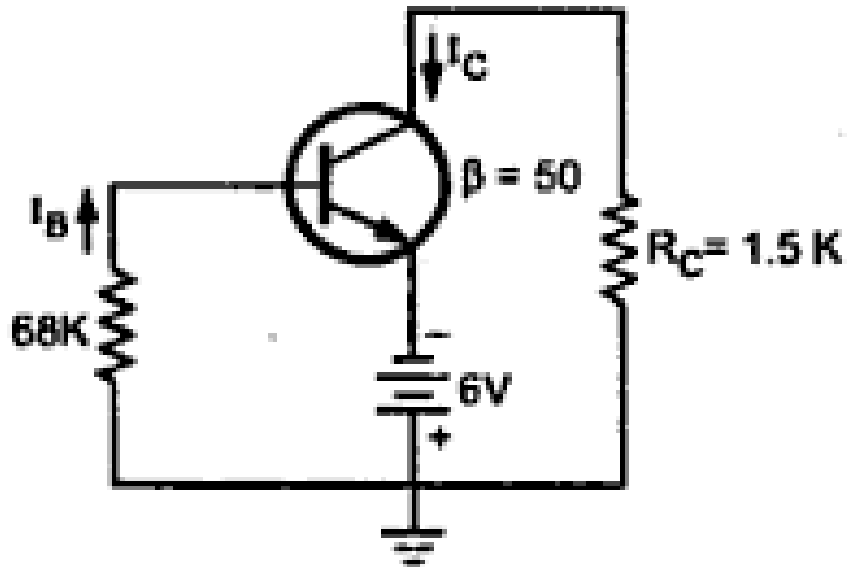


Figure 1

2. Draw the circuit diagram of a collector-base bias circuit of common base (CB) and (CC), and derive expression of both input and output analysis
3. In the circuit shown in Figure 2 find  $I_C$  when  $V_{CB} = 8V$  and  $V_{CB}$  when  $I_C = 2mA$

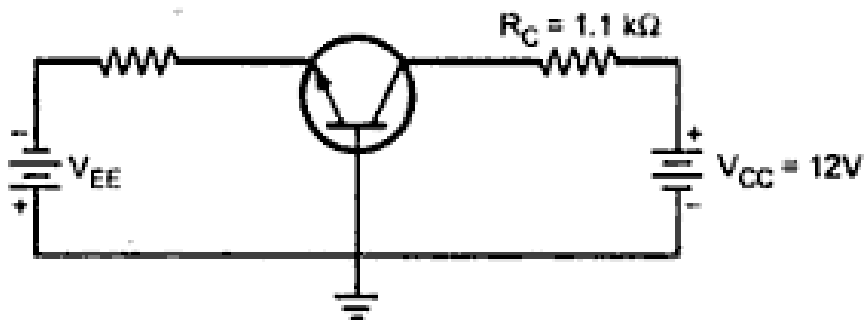


Figure 2

4. In the circuit shown below in Figure 3, calculate  $I_B$ ,  $I_C$  and  $V_{CE}$

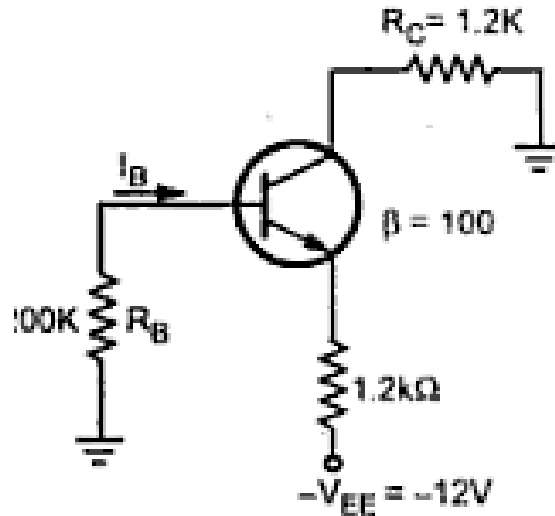


Figure 3

5. Using the approximate h-parameter model, obtain the expression for a CB and CC circuit for  $A_i$ ,  $Z_i$ ,  $A_v$  and  $Z_o$ .
6. The transistor amplifier shown in Figure 4 uses a transistor whose h-parameters as follows:  $h_i = 1.2K\Omega$ ,  $h_f = 75$ ,  $h_o = 25 \times 10^{-6}\Omega$ . Calculate  $A_i$ ,  $A_v$ ,  $Z_{in}$  and  $Z_o$

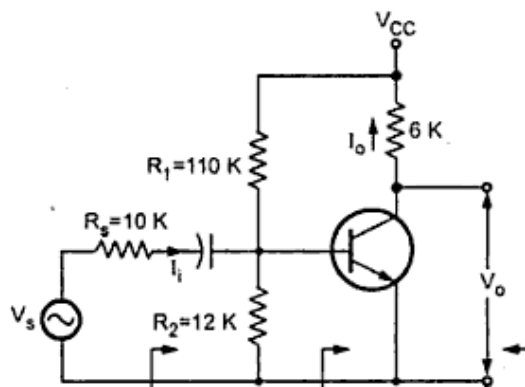


Figure 4

7. In the circuit shown below in Figure 5, Calculate  $V_{GSQ}$ ,  $I_{DQ}$ ,  $V_{DSQ}$  and  $V_D$

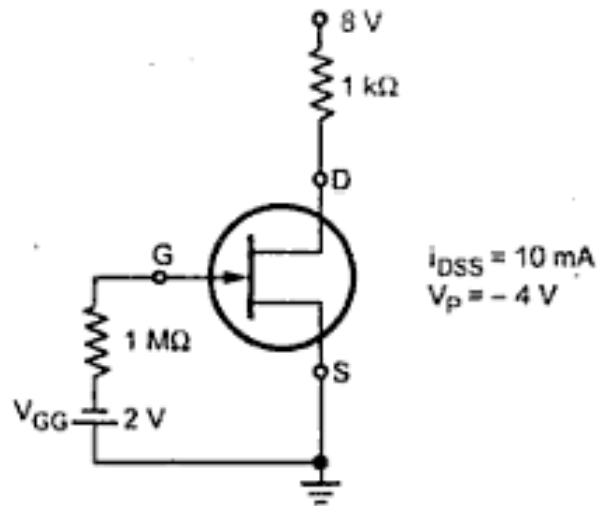


Figure 5

8. Derive the expression for  $A_V$ ,  $Z_i$  and  $Z_o$  of a JFET source follower.
9. For the amplifier shown in Figure 6, calculate  $A_V$ ,  $Z_i$ ,  $Z_o$ . Assume for FET  $g_m = 2\text{ mA/V}$ ,  $r_d = 10\text{ K}\Omega$

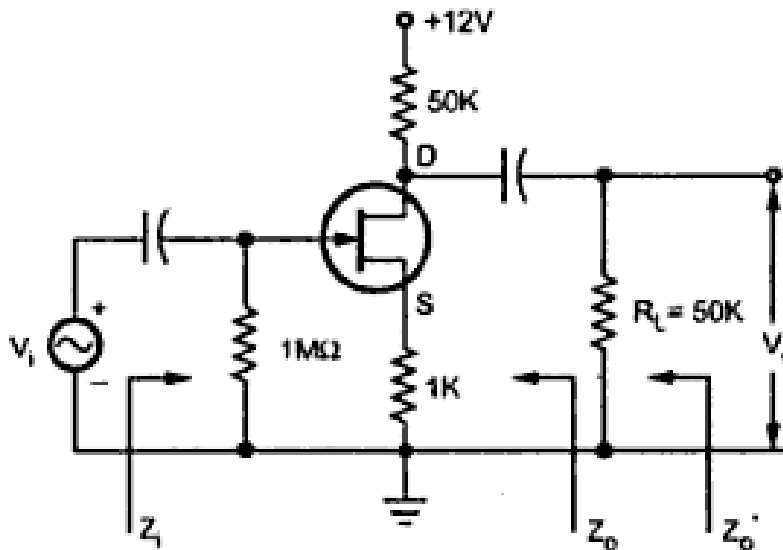


Figure 6