


Chapter 4 solved problem

1. In the circuit shown below if

$$v(t) = 56e^{-200t} \text{ V}, \quad t > 0$$

$$i(t) = 8e^{-200t} \text{ mA}, \quad t > 0$$

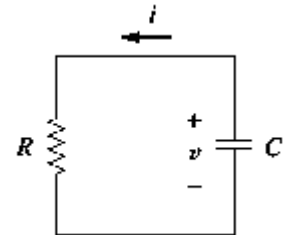- (a) Find the values of R and C .
- (b) Calculate the time constant
- (c) Determine the time required for the voltage to decay half its initial value at $t = 0$.



Solution

(a) $\tau = RC = 1/200$

For the resistor, $V = iR = 56e^{-200t} = 8Re^{-200t} \times 10^{-3} \longrightarrow R = \frac{56}{8} = 7 \text{ k}\Omega$

$$C = \frac{1}{200R} = \frac{1}{200 \times 7 \times 10^3} = 0.7143 \mu\text{F}$$


(b) $\tau = 1/200 = 5 \text{ ms}$

(c) If value of the voltage at $t = 0$ is 56.

$$\frac{1}{2} \times 56 = 56e^{-200t} \longrightarrow e^{200t} = 2$$


$$200t_o = \ln 2 \longrightarrow t_o = \frac{1}{200} \ln 2 = 3.466 \text{ ms}$$

2. Find $v_c(t)$, $t \geq 0$?

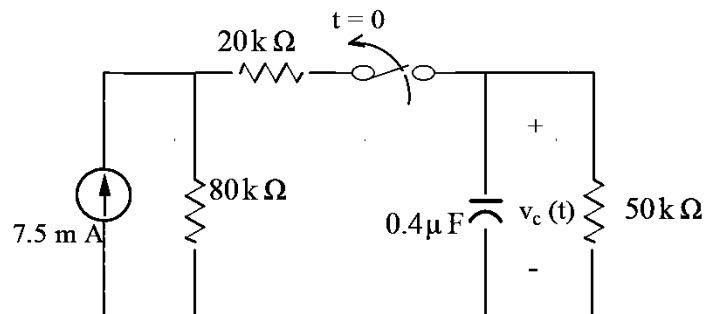


Solution:

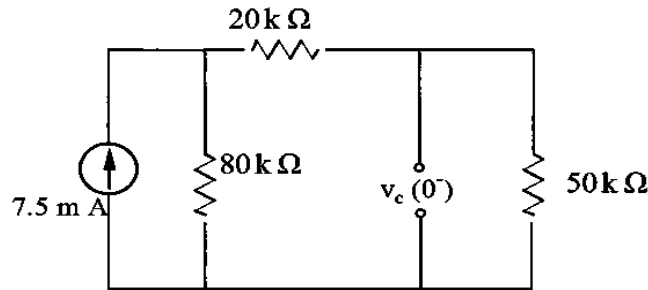- The switch has been closed for long time before switch move to new position.
- The capacitor behaves as open circuit.



$$v_c(0^-) = v_c(0) = v_c(0^+) = 50 \text{ k}\Omega \left[(7.5 \text{ mA}) \left(\frac{80 \text{ k}}{80 \text{ k} + 70 \text{ k}} \right) \right] = 50 \text{ k}\Omega \left[(7.5 \text{ mA}) \left(\frac{80 \text{ k}}{150 \text{ k}} \right) \right] = 200 \text{ V}$$

At $t = 0$, the switch is open

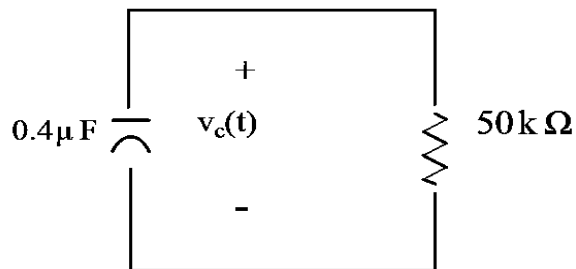

$$\frac{dv_c(t)}{dt} + 50 v_c(t) = 0$$

$$V_c(t) = 200 e^{-50t} \text{ V.}$$

KVL around the loop :


$$v_c(t) + 50 \text{ k} i_c(t) = 0$$

$$v_c(t) + 50 \text{ k} \left[C \frac{dv_c(t)}{dt} \right] = 0$$

Note From the voltage across the capacitor to find current through capacitor or resistance

$$I = C(dv/dt)$$

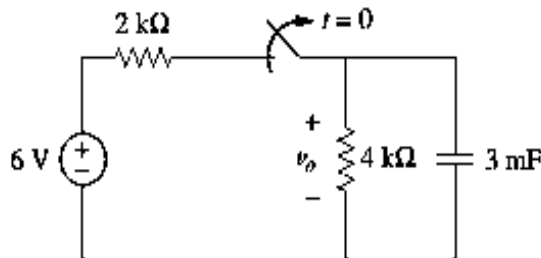3. The switch in figure below opens at $t=0$. Find for V_o for $t > 0$.



Solution For $t < 0$, the switch is closed so that


$$v_o(0) = \frac{4}{2+4}(6) = 4 \text{ V}$$

For $t > 0$, we have a source-free RC circuit.


$$\tau = RC = 3 \times 10^{-3} \times 4 \times 10^3 = 12 \text{ s}$$

$$v_o(t) = v_o(0)e^{-t/\tau} = 4e^{-t/12} \text{ V.}$$

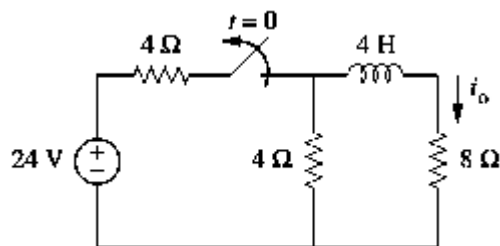4. For the circuit shown in figure below, find for i_o $t > 0$.



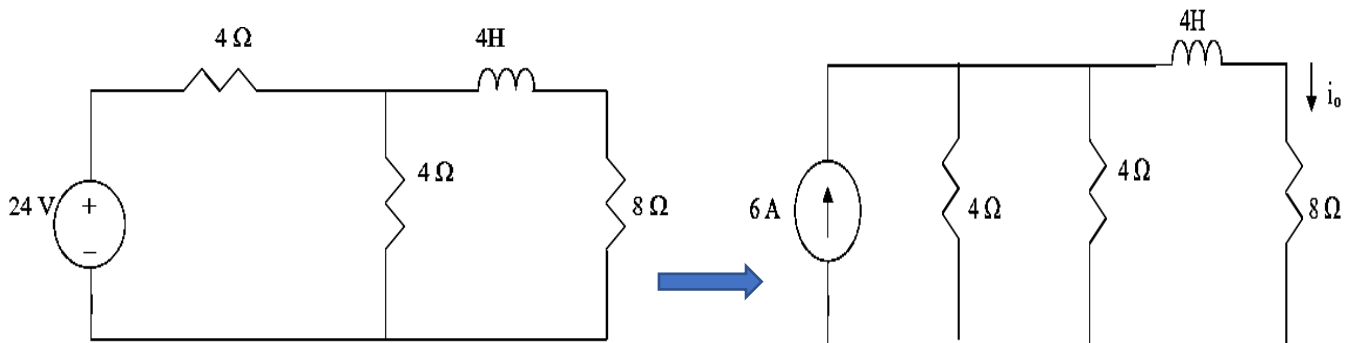Solution: For $t < 0$, we have the circuit shown below.



$$4 \parallel 4 = 4 \times 4 / 8 = 2$$

$$i_o(0^-) = [2 / (2 + 8)] 6 = 1.2 \text{ A}$$

For $t > 0$, we have a source-free RL circuit.

$$\tau = \frac{L}{R} = \frac{4}{4+8} = 1/3 \text{ thus,}$$


$$i_o(t) = 1.2e^{-3t} \text{ A.}$$

5. In the circuit shown below,

(a) Find R , L , and time constant.

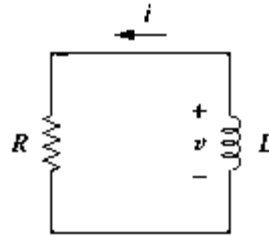(b) Calculate the energy dissipated in the resistance for $0 < t < .5 \text{ ms}$.

if $v(t) = 80e^{-10^3 t} \text{ V}, \quad t > 0$
 $i(t) = 5e^{-10^3 t} \text{ mA}, \quad t > 0$



solution:



(a) $\tau = \frac{1}{10^3} = \underline{1 \text{ ms}}$.

$v(t) = i(t)R = 80e^{-1000t} \text{ V} = R5e^{-1000t} \times 10^{-3}$ or $R = 80,000/5 = \mathbf{16 \text{ k}\Omega}$.

But $\tau = L/R = 1/10^3$ or $L = 16 \times 10^3 / 10^3 = \mathbf{16 \text{ H}}$.

(b). $E = \int_0^{0.05} V(t) * i(t) dt = 200(1 - e^{-1}) \times 10^{-6} = \mathbf{126.42 \text{ }\mu\text{J}}$.

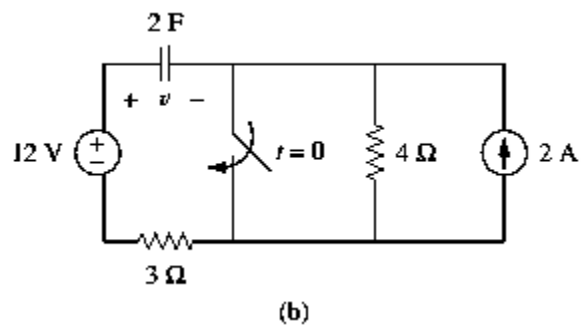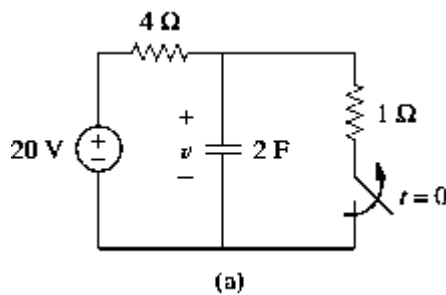6. Calculate the capacitor voltage for $t < 0$ and $t > 0$ for each of the circuits



Solution

(a) Before $t = 0$,

$$v(t) = \frac{1}{4+1} (20) = \mathbf{4 \text{ V}}$$

After $t = 0$,

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

$$\tau = RC = (4)(2) = 8, \quad v(0) = 4, \quad v(\infty) = 20$$

$$v(t) = 20 + (4 - 20) e^{-t/8}$$

$$v(t) = \mathbf{20 - 16 e^{-t/8} \text{ V}}$$

- (b) Before $t = 0$, $v = v_1 + v_2$, where v_1 is due to the 12-V source and v_2 is due to the 2-A source.

$$v_1 = 12 \text{ V}$$


To get v_2 , transform the current source as shown in Fig. (a).

$$v_2 = -8 \text{ V}$$


Thus,

$$v = 12 - 8 = 4 \text{ V}$$

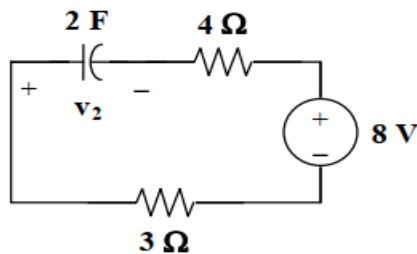After $t = 0$, the circuit becomes that shown in Fig. (b).



(a)

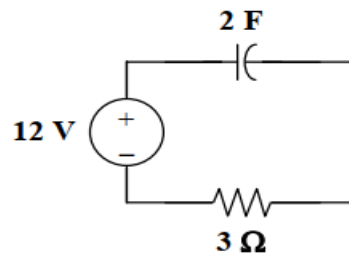

(b)


$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

$$v(\infty) = 12, \quad v(0) = 4, \quad \tau = RC = (2)(3) = 6$$

$$v(t) = 12 + (4 - 12)e^{-t/6}$$

$$v(t) = 12 - 8e^{-t/6} \text{ V}$$

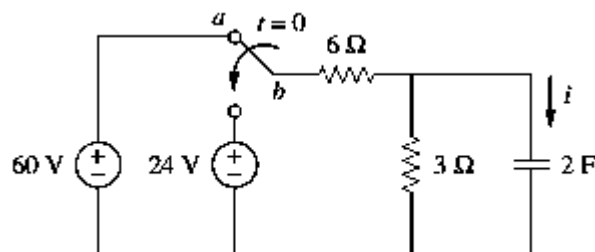7. The switch in Figure below has been in position a for a long time. At $t=0$ it moves to position b. Calculate $i(t)$ for all $t > 0$.



Solution:

$$R_{eq} = 6 \parallel 3 = 2 \Omega, \quad \tau = RC = 4$$

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

Using voltage division,


$$v(0) = \frac{3}{3+6} (60) = 20 \text{ V}, \quad v(\infty) = \frac{3}{3+6} (24) = 8 \text{ V}$$

Thus,

$$v(t) = 8 + (20 - 8) e^{-t/4} = 8 + 12 e^{-t/4}$$

$$i(t) = C \frac{dv}{dt} = (2)(12) \left(\frac{-1}{4} \right) e^{-t/4} = -6 e^{-0.25t} \text{ A}$$

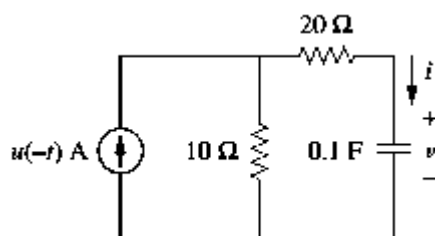8. Find $V(t)$ and $i(t)$ in the circuit if $u(-t) = 1$,



Solution For $t < 0$, $u(-t) = 1$,

For $t > 0$, $u(-t) = 0$, $v(\infty) = 0$


$$R_{th} = 20 + 10 = 30, \quad \tau = R_{th}C = (30)(0.1) = 3$$

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$


$$v(t) = 10 e^{-t/3} \text{ V}$$

$$i(t) = C \frac{dv}{dt} = (0.1) \left(\frac{-1}{3} \right) 10 e^{-t/3} \quad i(t) = \frac{-1}{3} e^{-t/3} \text{ A}$$

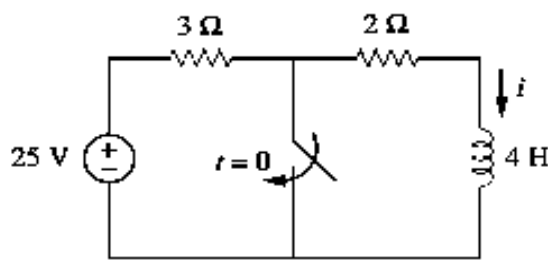9. Determine the inductor current for both $t < 0$ and $t > 0$ for each of the circuits shown below



(a)

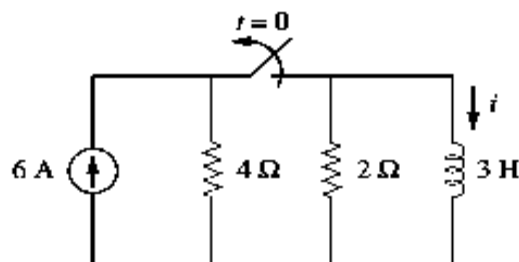

(b)

Solution:

(a) Before $t = 0$, $i = \frac{25}{3+2} = 5 \text{ A}$

After $t = 0$, $i(t) = i(0)e^{-t/\tau}$

$$\tau = \frac{L}{R} = \frac{4}{2} = 2, \quad i(0) = 5$$

$$i(t) = 5e^{-t/2} u(t) \text{ A}$$

- (b) Before $t = 0$, the inductor acts as a short circuit so that the 2Ω and 4Ω resistors are short-circuited.


$$i(t) = 6 \text{ A}$$

After $t = 0$, we have an RL circuit.

$$i(t) = i(0)e^{-t/\tau}, \quad \tau = \frac{L}{R} = \frac{3}{2}$$

$$i(t) = 6e^{-2t/3} u(t) \text{ A}$$

10. Obtain the inductor current for both $t < 0$ and $t > 0$ for the circuit shown below

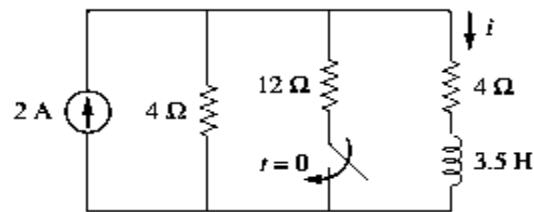**Solution**

Before $t = 0$, i is obtained by current division or

$$i(t) = \frac{4}{4+4} (2) = 1 \text{ A}$$

After $t = 0$,

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$\tau = \frac{L}{R_{eq}}, \quad R_{eq} = 4 + (4 \parallel 12) = 7 \Omega$$


$$\tau = \frac{3.5}{7} = \frac{1}{2}$$

$$i(0) = 1, \quad i(\infty) = \frac{(4 \parallel 12)}{4 + (4 \parallel 12)} (2) = \frac{3}{4+3} (2) = \frac{6}{7}$$

$$i(t) = \frac{6}{7} + \left(1 - \frac{6}{7}\right) e^{-2t}$$



$$i(t) = \frac{1}{7} (6 - e^{-2t}) \text{ A}$$

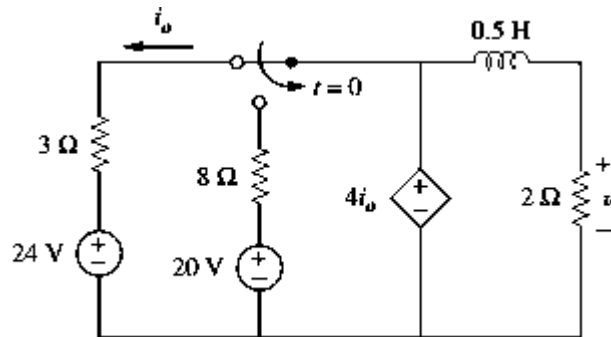11. Find $V(t)$ for $t < 0$ and $t > 0$ in the circuit shown below



Solution:

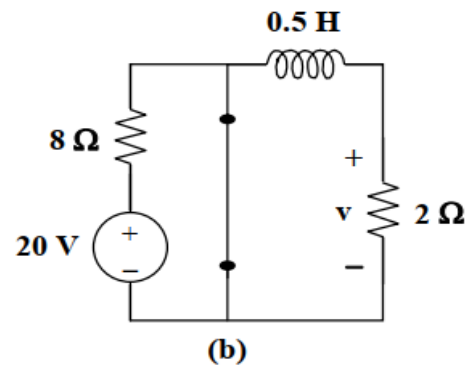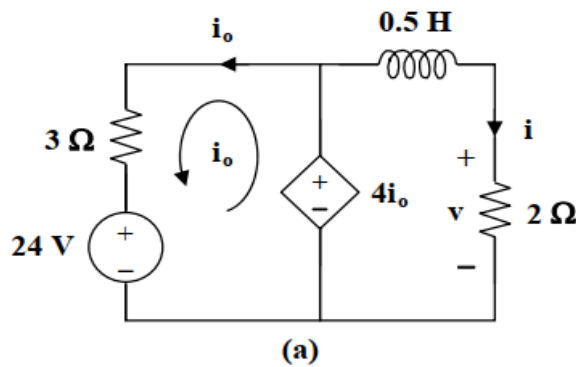For $t < 0$, consider the circuit shown in Fig. (a).



$$3i_o + 24 - 4i_o = 0 \longrightarrow i_o = 24$$

$$v(t) = 4i_o = \mathbf{96 \text{ V}} \qquad i = \frac{v}{2} = 48 \text{ A}$$

For $t > 0$, consider the circuit in Fig. (b).

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$


$$i(0) = 48, \quad i(\infty) = 0$$

$$R_{th} = 2 \Omega, \quad \tau = \frac{L}{R_{th}} = \frac{0.5}{2} = \frac{1}{4}$$

$$i(t) = (48) e^{-4t}$$

$$v(t) = 2i(t) = \mathbf{96 e^{-4t} u(t) V}$$

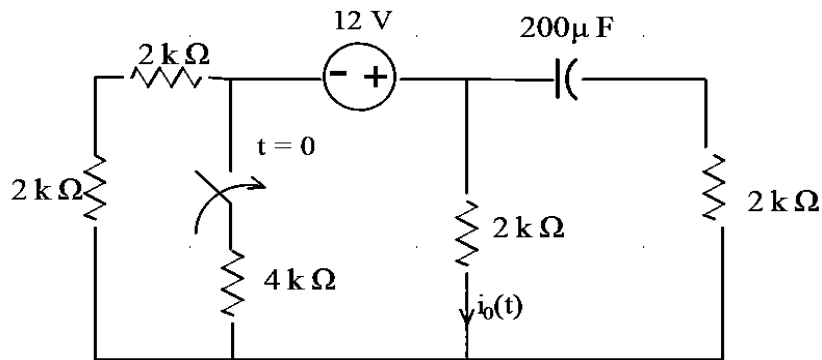
12. Find $i_0(t)$, $t > 0$ by using step by step methods.



Step (1) :

$$i_0(t) = k_1 + k_2 e^{\frac{-t}{\tau}}$$


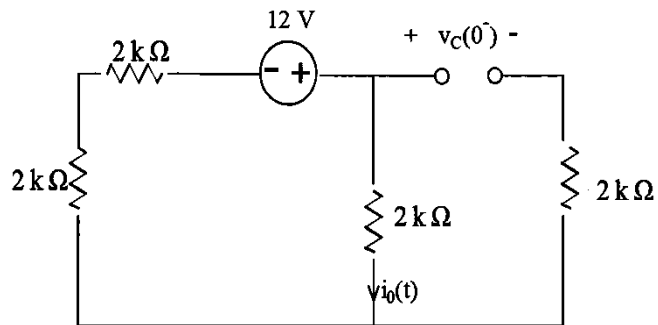
Step (2): assume steady state (for $t < 0$) replace capacitor by open circuit.




$$v_c(0^-) = (12) \frac{2k}{6k} = 4V$$

$$v_c(0^-) = v_c(0) = v_c(0^+) = 4V$$

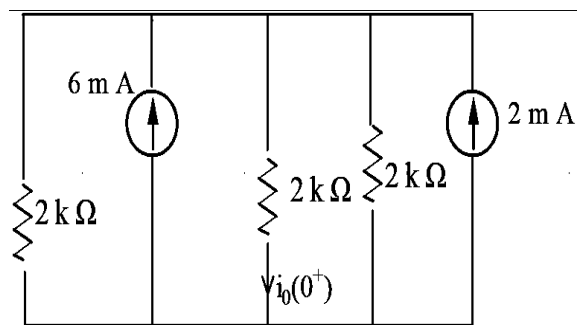
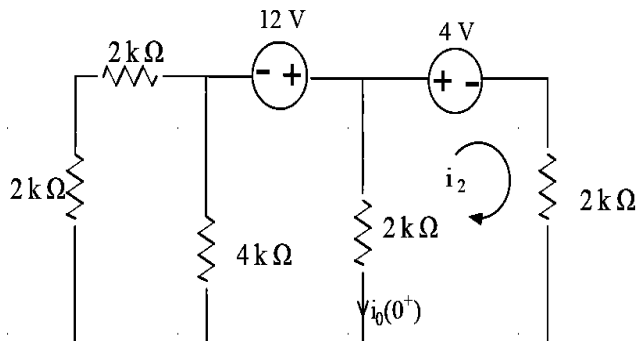
Step 3: now switch is moved, replace capacitor by voltage source = $v_c(0)$,
Now find $i_0(0)$



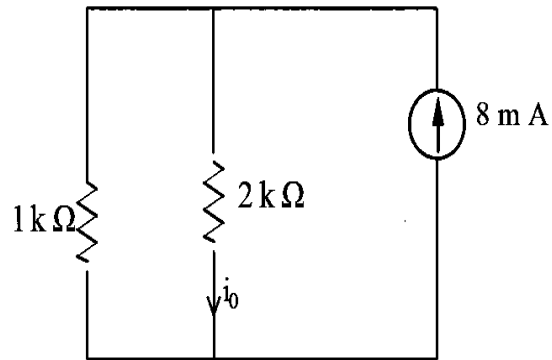


$$i_o(0) = 8 \text{ mA} \left(\frac{1\text{k}}{3\text{k}} \right) = 2.66 \text{ mA}$$

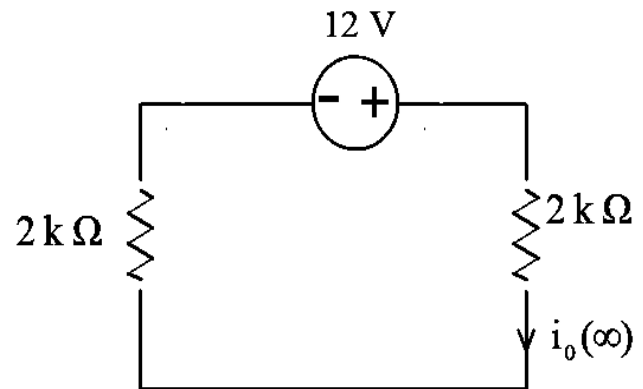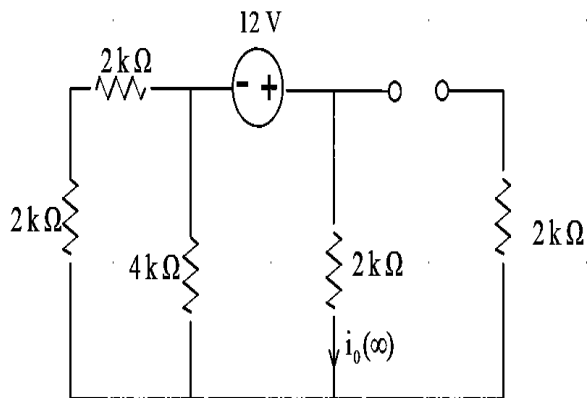Step 4: assume $t = \infty$, find $i_o(\infty)$. Steady state Replace capacitor by open circuit



$$i_o(\infty) = \frac{12}{4\text{k}} = 3 \text{ mA}$$

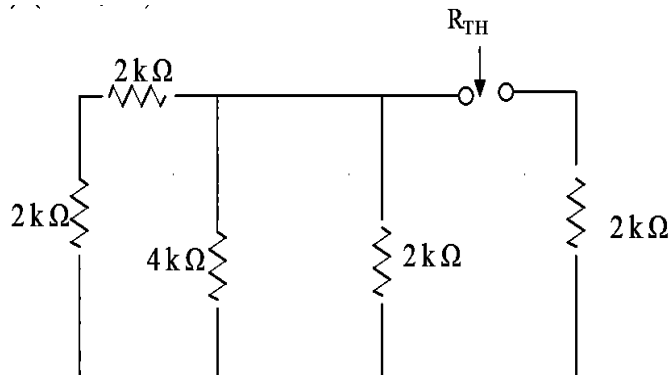Step 5: find time constant. First find R_{TH} at terminals of the capacitor



$$R_{TH} = (4\text{k} // 4\text{k} // 2\text{k}) + 2\text{k}$$

$$= 3\text{k}\Omega$$

$$\tau = R_{TH} C = (3\text{k}\Omega)(200\mu\text{F}) = 0.6 \text{ sec}$$

Step 6 : find the solution $i_o(t)$


$$i_o(t) = i_o(\infty) + [i_o(0) - i_o(\infty)] e^{\frac{-t}{\tau}}$$

$$= 3 + (2.66 - 3) e^{-t/0.6} \text{ mA}$$

$$i_o(t) = 3 - 0.33 e^{-t/0.6} \text{ mA}$$

13. For the circuit shown below find

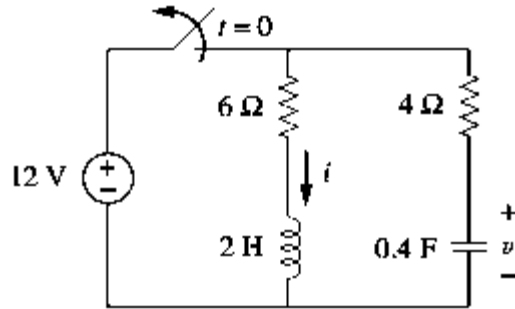- (a) $i(0^+)$ and $v(0^+)$,
- (b) $di(0^+)/dt$ and $dv(0^+)/dt$,
- (c) $i(\infty)$ and $v(\infty)$.




14. If what value of C will make an RLC series circuit:

- (a) overdamped,
- (b) critically damped,
- (c) underdamped?

Solution

- a. Overdamped when $C > 4L/(R_2) = 4 \times 1.5/2500 = 2.4 \times 10^{-3}$, or $C > \mathbf{2.4 \text{ mF}}$
- b. Critically damped when $C = \mathbf{2.4 \text{ mF}}$
- c. Underdamped when $C < \mathbf{2.4 \text{ mF}}$

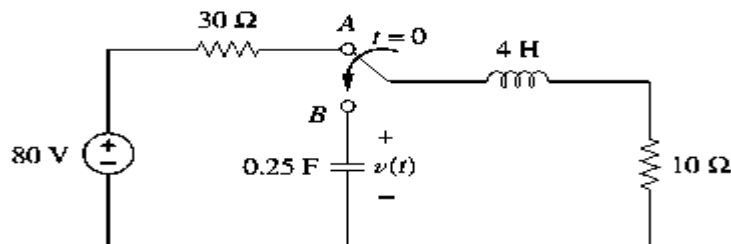15. The switch in figure below moves from position A to position B at (please note that the switch must connect to point B before it breaks the connection at A , a make-before-break switch). Let $v(0) = 0$, find $v(t)$ for $t > 0$.



Solution:

When the switch is in position A , $v(0^-) = 0$ and $i_L(0) = 80/40 = 2 \text{ A}$. When the switch is in position B , we have a source-free series RCL circuit.

$$\alpha = \frac{R}{2L} = \frac{10}{2 \times 4} = 1.25$$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{4} \times 4}} = 1$$

When the switch is in position A , $v(0^-) = 0$. When the switch is in position B , we have a source-free series RCL circuit.

$$\alpha = \frac{R}{2L} = \frac{10}{2 \times 4} = 1.25$$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{4} \times 4}} = 1$$

Since $\alpha > \omega_o$, we have overdamped case.

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} = -1.25 \pm \sqrt{1.5625} = -0.5 \text{ and } -2$$

$$v(t) = Ae^{-2t} + Be^{-0.5t}$$

$$v(0) = 0 = A + B$$

$$i_c(0) = C(dv(0)/dt) = -2 \text{ or } dv(0)/dt = -2/C = -8.$$


But $\frac{dv(t)}{dt} = -2Ae^{-2t} - 0.5Be^{-0.5t}$

$$\frac{dv(0)}{dt} = -2A - 0.5B = -8$$

Solving (2) and (3) gives $A = 1.3333$ and $B = -1.3333$

$$v(t) = 5.333e^{-2t} - 5.333e^{-0.5t} \text{ V.}$$

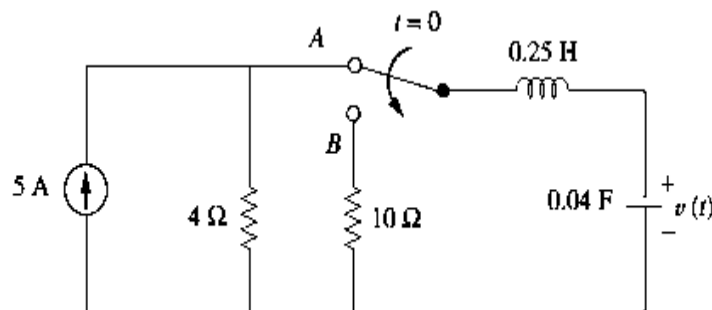16. In the circuit of Fig. 8.71, the switch instantaneously moves from position A to B at $t = 0$. Find for all $t > 0$.



Solution:

$$i(0) = I_0 = 0, \quad v(0) = V_0 = 4 \times 5 = 20$$

$$\frac{di(0)}{dt} = -\frac{1}{L}(RI_0 + V_0) = -4(0 + 20) = -80$$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{4} \times \frac{1}{25}}} = 10$$

$$\alpha = \frac{R}{2L} = \frac{10}{2 \times \frac{1}{4}} = 20, \text{ which is } > \omega_o.$$

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} = -20 \pm \sqrt{300} = -20 \pm 10\sqrt{3} = -2.679, -37.32$$

$$i(t) = A_1 e^{-2.679t} + A_2 e^{-37.32t}$$

$$i(0) = 0 = A_1 + A_2, \quad \frac{di(0)}{dt} = -2.679 A_1 - 37.32 A_2 = -80$$


This leads to $A_1 = -2.309 = -A_2$

$$i(t) = 2.309(e^{-37.32t} - e^{-2.679t})$$


Since, $v(t) = \frac{1}{C} \int_0^t i(t) dt + 20$, we get

$$v(t) = [21.55e^{-2.679t} - 1.55e^{-37.32t}] \text{ V}$$

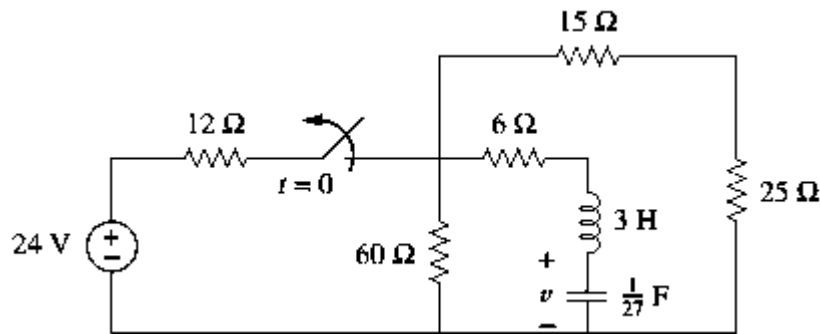17. Calculate for in the circuit of shown below



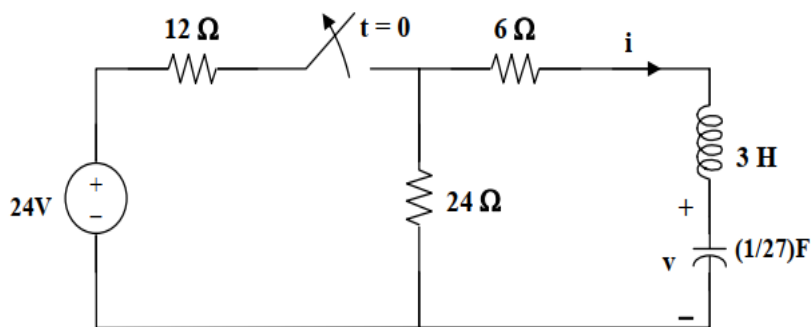Solution: By combining some resistors, the circuit is equivalent to that shown below.
 $60 \parallel (15 + 25) = 24 \text{ ohms.}$



At $t = 0^-$, $i(0) = 0$, $v(0) = 24 \times 24 / 36 = 16 \text{ V}$

For $t > 0$, we have a series RLC circuit. $R = 30 \text{ ohms}$, $L = 3 \text{ H}$, $C = (1/27) \text{ F}$

$$\alpha = R/(2L) = 30/6 = 5$$

$$\omega_o = 1/\sqrt{LC} = 1/\sqrt{3 \times 1/27} = 3, \text{ clearly } \alpha > \omega_o \text{ (overdamped response)}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} = -5 \pm \sqrt{5^2 - 3^2} = -9, -1$$

$$v(t) = [Ae^{-t} + Be^{-9t}], \quad v(0) = 16 = A + B \quad (1)$$


$$i = Cdv/dt = C[-Ae^{-t} - 9Be^{-9t}]$$

$$i(0) = 0 = C[-A - 9B] \text{ or } A = -9B \quad (2)$$

From (1) and (2), $B = -2$ and $A = 18$.

$$\text{Hence, } v(t) = (18e^{-t} - 2e^{-9t}) \text{ V}$$

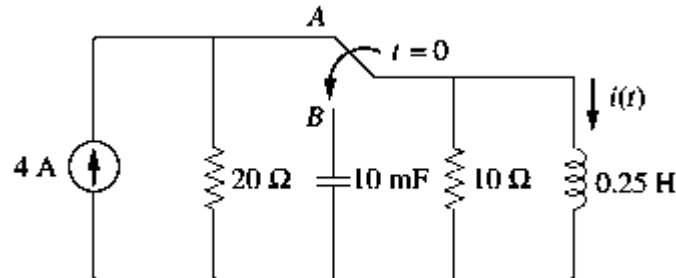18. The switch in Fig. below moves from position A to position B at (please note that the switch must connect to point B before it breaks the connection at A , a make-before-break switch). Determine $i(t)$ for $t > 0$.



Solution:

When the switch is in position A , the inductor acts like a short circuit so $i(0^-) = 4$

When the switch is in position B , we have a source-free parallel RCL circuit

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 10 \times 10 \times 10^{-3}} = 5$$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{4} \times 10 \times 10^{-3}}} = 20$$

Since $\alpha < \omega_o$, we have an underdamped case.

$$s_{1,2} = -5 \pm \sqrt{25 - 400} = -5 \pm j19.365$$

$$i(t) = e^{-5t} (A_1 \cos 19.365t + A_2 \sin 19.365t)$$

$$i(0) = 4 = A_1$$


$$v = L \frac{di}{dt} \longrightarrow \frac{di(0)}{dt} = \frac{v(0)}{L} = 0$$

$$\frac{di}{dt} = e^{-5t} (-5A_1 \cos 19.365t - 5A_2 \sin 19.365t - 19.365A_1 \sin 19.365t + 19.365A_2 \cos 19.365t)$$


$$0 = [di(0)/dt] = -5A_1 + 19.365A_2 \text{ or } A_2 = 20/19.365 = 1.0328$$

$$i(t) = e^{-5t} [4\cos(19.365t) + 1.0328\sin(19.365t)] \text{ A}$$

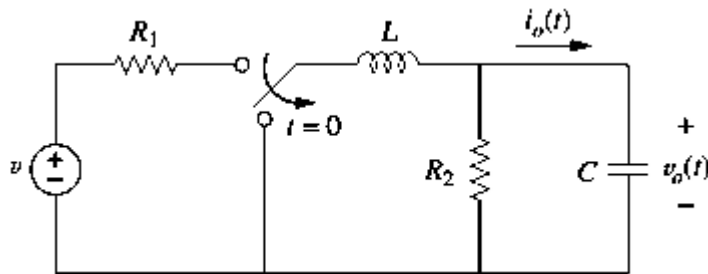19. Find $I_o(t)$ and $V_o(t)$ for the circuit shown below if $v = 30\text{V}$, $L = 1\text{H}$, $R_1 = 2\Omega$, $R_2 = 8\Omega$, $C = 0.25\text{ F}$



Solution:

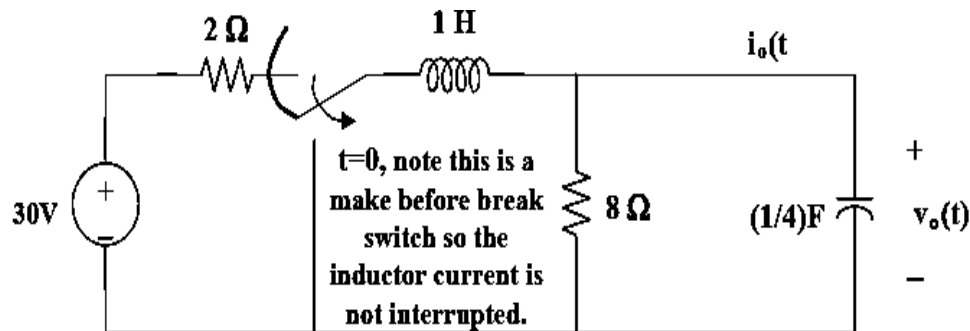

$$\text{At } t = 0^-, v_o(0) = (8/(2 + 8))(30) = 24$$

For $t > 0$, we have a source-free parallel RLC circuit.

$$\alpha = 1/(2RC) = 1/4 \quad \omega_o = 1/\sqrt{LC} = 1/\sqrt{1 \times 1/4} = 2$$

Since α is less than ω_o , we have an under-damped response.

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2} = \sqrt{4 - (1/16)} = 1.9843$$

$$v_o(t) = (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t}$$

$$v_o(0) = 30(8/(2+8)) = 24 = A_1 \text{ and } i_o(t) = C(dv_o/dt) = 0 \text{ when } t = 0.$$

$$dv_o/dt = -\alpha(A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} + (-\omega_d A_1 \sin \omega_d t + \omega_d A_2 \cos \omega_d t) e^{-\alpha t}$$


$$\text{at } t = 0, \text{ we get } dv_o(0)/dt = 0 = -\alpha A_1 + \omega_d A_2$$

$$\text{Thus, } A_2 = (\alpha/\omega_d) A_1 = (1/4)(24)/1.9843 = 3.024$$

$$v_o(t) = (24 \cos 1.9843t + 3.024 \sin 1.9843t) e^{-t/4} \text{ volts.}$$


$$\begin{aligned} i_o(t) &= C dv/dt = 0.25[-24(1.9843) \sin 1.9843t + 3.024(1.9843) \cos 1.9843t - \\ &0.25(24 \cos 1.9843t) - 0.25(3.024 \sin 1.9843t)] e^{-t/4} \\ &= [-12.095 \sin 1.9843t] e^{-t/4} \text{ A.} \end{aligned}$$

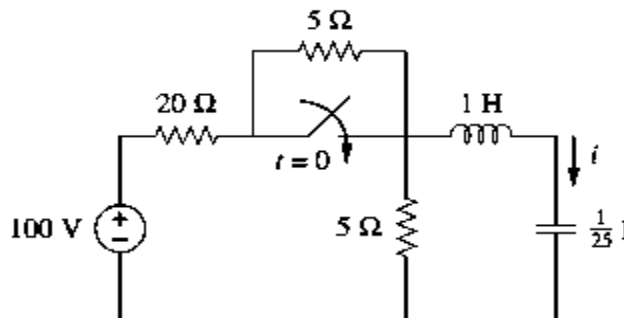20. Find $i(t)$ for $t > 0$ in the circuit of shown below



Solution: At $t = 0^-$, the switch is open. $i(0) = 0$, and
 $v(0) = 5 \times 100 / (20 + 5 + 5) = 50/3$

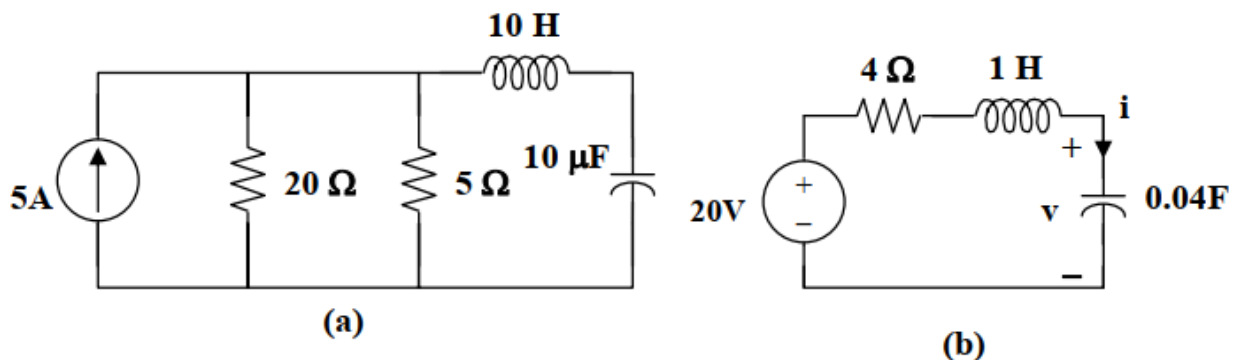For $t > 0$, we have a series RLC circuit shown in Figure (a). After source transformation, it becomes that shown in Figure (b).



$$\omega_o = 1/\sqrt{LC} = 1/\sqrt{1 \times 1/25} = 5$$

$$\alpha = R/(2L) = (4)/(2 \times 1) = 2$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} = -2 \pm j4.583$$

Thus,
$$v(t) = V_s + [(A \cos(\omega_d t) + B \sin(\omega_d t))e^{-2t}],$$

where $\omega_d = 4.583$ and $V_s = 20$

$$v(0) = 50/3 = 20 + A \text{ or } A = -10/3$$

$$i(t) = C dv/dt$$

$$= C(-2) [(A \cos(\omega_d t) + B \sin(\omega_d t))e^{-2t}] + C\omega_d [(-A \sin(\omega_d t) + B \cos(\omega_d t))e^{-2t}]$$

$$i(0) = 0 = -2A + \omega_d B$$


$$B = 2A/\omega_d = -20/(3 \times 4.583) = -1.455$$

$$i(t) = C \{ [(0 \cos(\omega_d t) + (-2B - \omega_d A) \sin(\omega_d t))] e^{-2t} \}$$

$$= (1/25) \{ [(2.91 + 15.2767) \sin(\omega_d t)] e^{-2t} \}$$

$$i(t) = 727.5 \sin(4.583t) e^{-2t} \text{ mA}$$

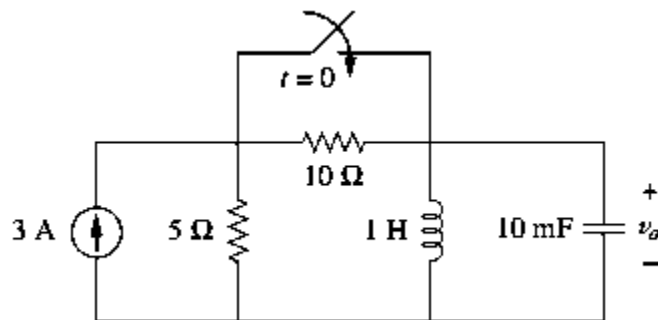21. Find the output voltage $V_o(t)$ in the circuits shown below



Solution: At $t = 0^-$, we obtain, $i_L(0) = 3 \times 5 / (10 + 5) = 1 \text{ A}$ and $v_o(0) = 0$.

For $t > 0$, the 10-ohm resistor is short-circuited and we have a parallel RLC circuit with a step input.

$$\alpha = 1/(2RC) = (1)/(2 \times 5 \times 0.01) = 10$$

$$\omega_o = 1/\sqrt{LC} = 1/\sqrt{1 \times 0.01} = 10$$

Since $\alpha = \omega_o$, we have a critically damped response.

$$s_{1,2} = -10$$

Thus, $i(t) = I_s + [(A + Bt)e^{-10t}]$, $I_s = 3$


$$i(0) = 1 = 3 + A \text{ or } A = -2$$

$$v_o = L di/dt = [Be^{-10t}] + [-10(A + Bt)e^{-10t}]$$

$$v_o(0) = 0 = B - 10A \text{ or } B = -20$$

$$\text{Thus, } v_o(t) = (200te^{-10t}) \text{ V}$$


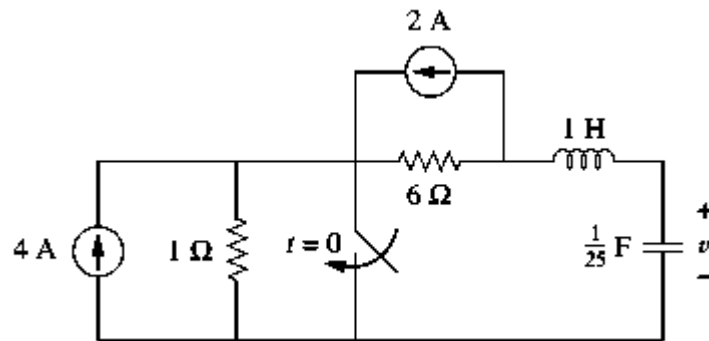
22. For the network given in figure below find $V(t) > 0$.



Solution:

For $t = 0^-$, we have the equivalent circuit as shown in Figure (a).

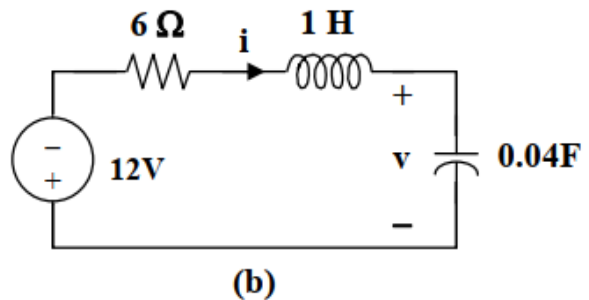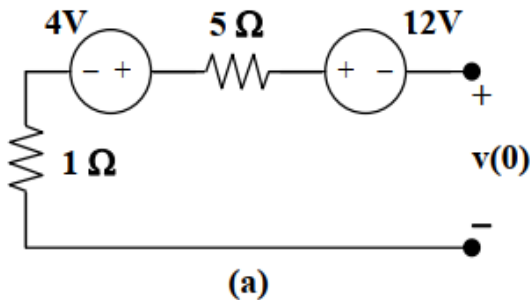$i(0) = i(0^-) = 0$, and $v(0) = 4 - 12 = -8\text{V}$



For $t > 0$, the circuit becomes that shown in Figure (b) after source transformation.

$$\omega_o = 1/\sqrt{LC} = 1/\sqrt{1 \times 1/25} = 5$$

$$\alpha = R/(2L) = (6)/(2) = 3$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} = -3 \pm j4$$

Thus,

$$v(t) = V_s + [(A \cos 4t + B \sin 4t)e^{-3t}], \quad V_s = -12$$


$$v(0) = -8 = -12 + A \quad \text{or} \quad A = 4$$

$$i = C dv/dt, \quad \text{or} \quad i/C = dv/dt = [-3(A \cos 4t + B \sin 4t)e^{-3t}] + [4(-A \sin 4t + B \cos 4t)e^{-3t}]$$

$$i(0) = -3A + 4B \quad \text{or} \quad B = 3$$


$$v(t) = \{-12 + [(4 \cos 4t + 3 \sin 4t)e^{-3t}]\} \text{ A}$$

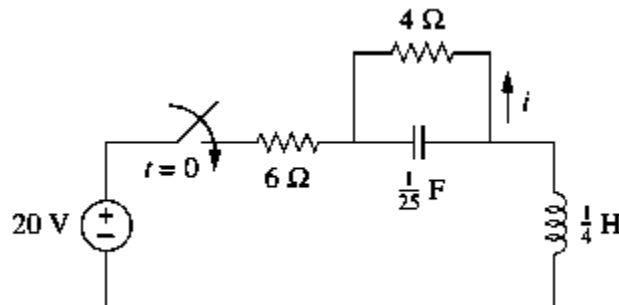23. In the circuit of Figure below, find for $i(t)$ for $t > 0$.



Solution: For $t < 0$, $i(0) = 0$ and $v(0) = 0$.

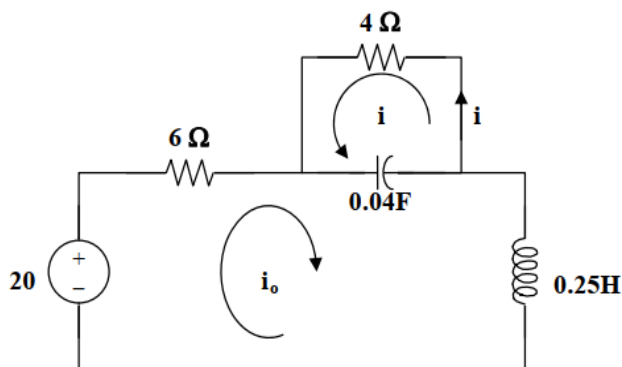For $t > 0$, the circuit is as shown below.



Applying KVL to the larger loop,

$$-20 + 6i_o + 0.25 di_o/dt + 25 \int (i_o + i) dt = 0$$

Taking the derivative,

$$6 di_o/dt + 0.25 d^2 i_o/dt^2 + 25(i_o + i) = 0 \quad 1$$

For the smaller loop, $4 + 25 \int (i + i_o) dt = 0$

Taking the derivative, $25(i + i_o) = 0$ or $i = -i_o$ (2)

From (1) and (2) $6di_o/dt + 0.25d^2i_o/dt^2 = 0$

This leads to, $0.25s^2 + 6s = 0$ or $s_{1,2} = 0, -24$


$$i_o(t) = (A + Be^{-24t}) \text{ and } i_o(0) = 0 = A + B \text{ or } B = -A$$

As t approaches infinity, $i_o(\infty) = 20/10 = 2 = A$, therefore $B = -2$

Thus, $i_o(t) = (2 - 2e^{-24t}) = -i(t)$ or

$$i(t) = (-2 + 2e^{-24t}) \text{ A}$$

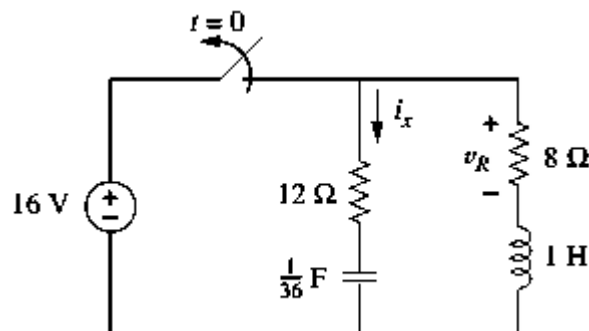24. If the switch in figure below has been closed for a long time before but is opened at determine:
- the characteristic equation of the circuit,
 - i_x and v_R for $t > 0$.



Solution: (a) Let v = capacitor voltage and i = inductor current. At $t = 0^-$, the switch is closed and the circuit has reached steady-state.

$$v(0^-) = 16\text{V and } i(0^-) = 16/8 = 2\text{A}$$

At $t = 0^+$, the switch is open but, $v(0^+) = 16$ and $i(0^+) = 2$.

We now have a source-free RLC circuit.

$$R = 8 + 12 = 20 \text{ ohms, } L = 1\text{H, } C = 4\text{mF}$$

$$\alpha = R/(2L) = (20)/(2 \times 1) = 10$$

Since $\alpha > \omega_o$, we have a overdamped response.


$$\omega_o = 1/\sqrt{LC} = 1/\sqrt{1 \times (1/36)} = 6$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} = -18, -2$$

Thus, the characteristic equation is $(s + 2)(s + 18) = 0$ or $s^2 + 20s + 36 = 0$.

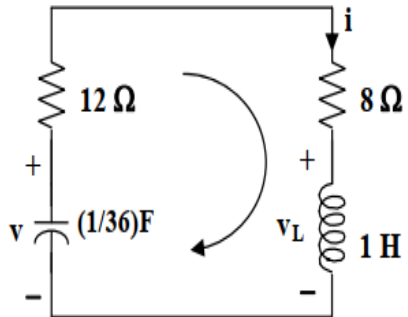(b) $i(t) = [Ae^{-2t} + Be^{-18t}]$ and $i(0) = 2 = A + B$ (1)

To get $di(0)/dt$, consider the circuit below at $t = 0^+$.



$-v(0) + 20i(0) + v_L(0) = 0$, which leads to,

$-16 + 20 \times 2 + v_L(0) = 0$ or $v_L(0) = -24$

$L di(0)/dt = v_L(0)$ which gives $di(0)/dt = v_L(0)/L = -24/1 = -24 \text{ A/s}$


Hence $-24 = -2A - 18B$ or $12 = A + 9B$ (2)

From (1) and (2), $B = 1.25$ and $A = 0.75$

$i(t) = [0.75e^{-2t} + 1.25e^{-18t}] = -i_x(t)$ or $i_x(t) = [-0.75e^{-2t} - 1.25e^{-18t}] \text{ A}$

$v(t) = 8i(t) = [6e^{-2t} + 10e^{-18t}] \text{ A}$

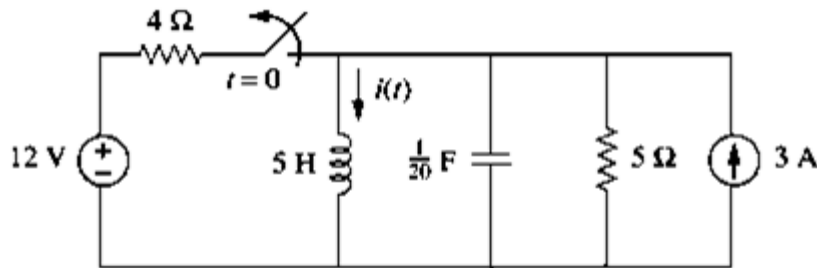25. Determine $i(t)$ for $t > 0$ in the circuit shown below



26. Find the output voltage $V_o(t)$ in the circuit of shown below for $t > 0$. If $V_1=8\text{v}$, $V_2=12\text{v}$, $R=2\Omega$, $L=1\text{H}$, $C= 1/5 \text{ F}$.

