

## WORK SHEET

1. A 60 W light bulb has a current of 0.5 A flowing through it. Calculate (i) the number of electrons passing through a cross-section of the filament (ii) the number of electrons that pass the cross-section in one hour.
2. Body *A* has a positive charge of  $0.6\ \mu\text{C}$  and body *B* has a charge of  $0.3\ \mu\text{C}$  (negative). If  $87 \times 10^{15}$  electrons are transferred from *A* to *B*, what are the charges in coulombs on *A* and on *B* after the transfer?
3. Three equal resistors are connected as shown in Fig 1 below. Find the equivalent resistance between points *A* and *B*.

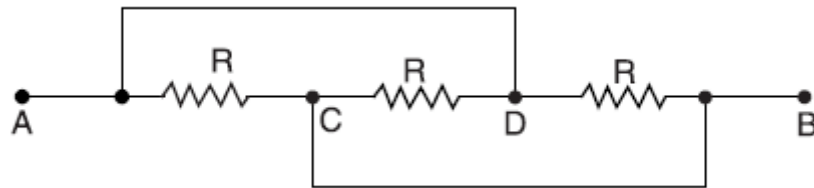


Fig .1

4. Find the current supplied by the d.c. source in the circuit shown in Figure 2 below

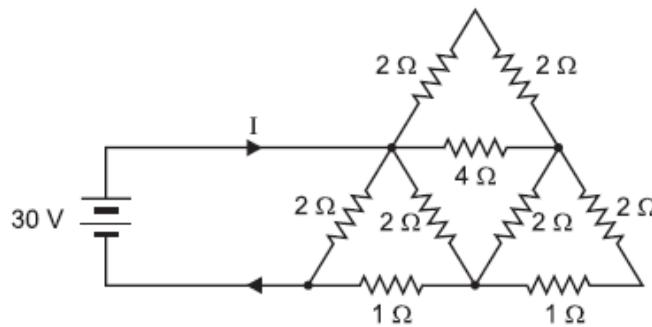


Fig.2

5. By using KCL and KVL, Determine the current in 4 ohms resistance of the circuit shown in Figure 3 below

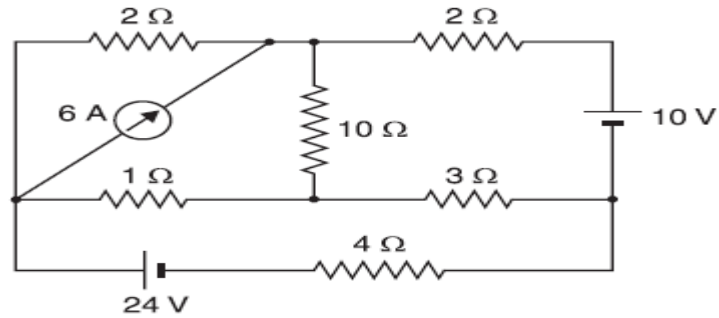


Fig.3

6. Use nodal analysis to find  $V_o$  in the circuit in fig.4

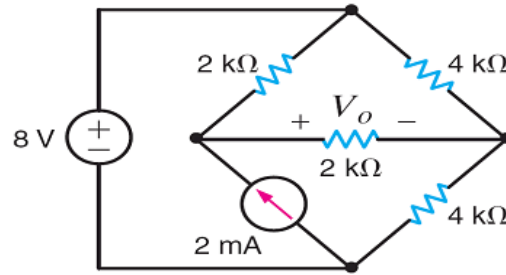


Fig.4

7. Find  $V_x$  using super position in fig. 5

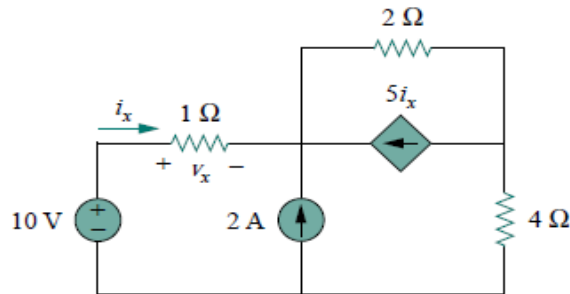


Fig.5

8. By using voltage divider rule, calculate the voltages  $v_x$  and  $v_y$  in the circuit shown in Figure 6 below.,

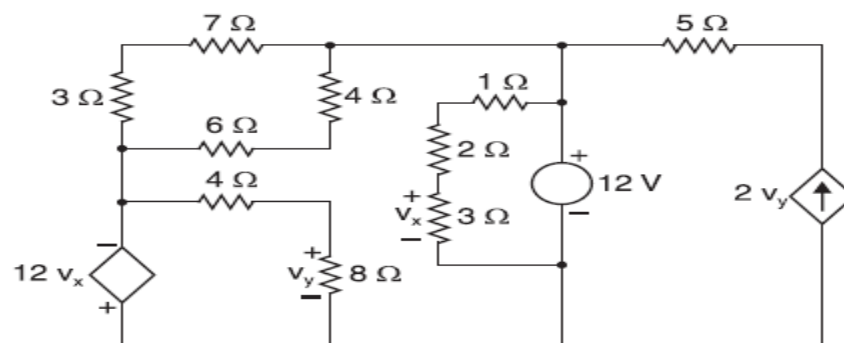


Fig.6

9. For the circuit in fig 7 obtain the Thevenin equivalent as seen from terminals:

a) a-b

b) a-c

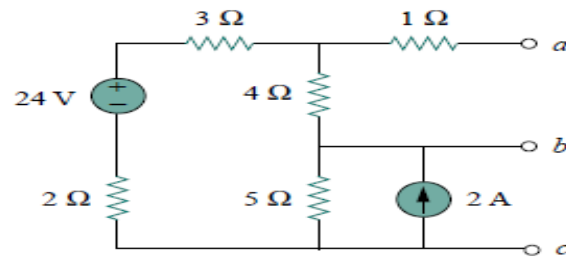


Fig.7

10. Obtain Norton equivalent at terminal a-b of the circuit in fig 8.

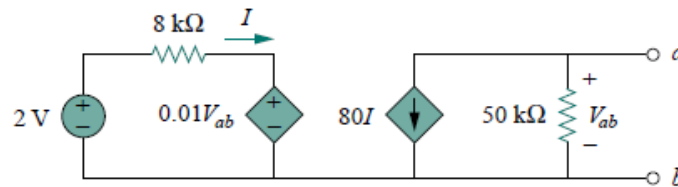


Fig. 8

11. Refer to fig 9. for what value of R is the power dissipated in R maximum? calculate the power

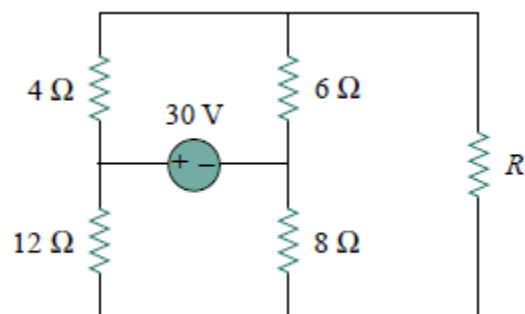


Fig.9