



ADAMA SCIENCE AND TECHNOLOGY UNIVERSITY

SCHOOL OF ELECTRICAL ENGINEERING&COMPUTING

DEPARTMENT OF ELECTRICAL POWER & CONTROL ENGINEERING

Course name: Fundamentals of Electrical Engineering

Group Assignment I: (5%)

Course no: EPCE 2101

Submission date:30/03/23

Instructions:

- Answer all of the following questions.
- Make your answers **Clear and Readable.**
- **Maximum number of students in one group:5**

1. The charge flowing through the element of electric circuit is plotted in figure1. If the current flowing through the element is given by

$$i(t) = \begin{cases} 3t\text{A}, & 0 \leq t < 6\text{ s} \\ 18\text{A}, & 6 \leq t < 10\text{ s} \\ -12\text{A}, & 10 \leq t < 15\text{ s} \\ 0, & t \geq 15\text{ s} \end{cases}$$

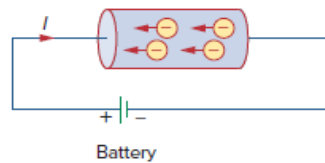


Figure 1

- a) Find the charge stored in the element at $t = 7\text{s}$.
- b) Plot the charge stored in the element over $0 < t < 20\text{ s}$.
2. From figure2 shown below determine the power loss in the 10Ω resistor by using mesh method.

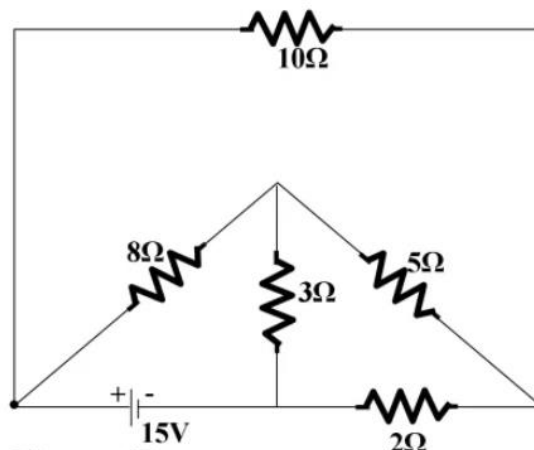


Figure 2

3. From the figure 3 shown below find the value of R by using superposition theorem. [$i=0.1\text{A}$]

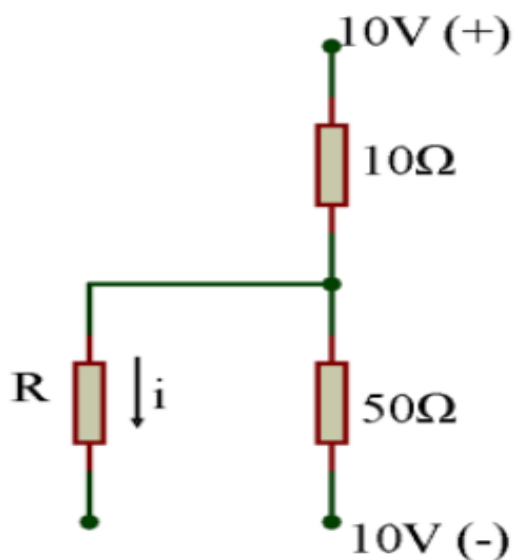


Figure 3

4. Consider the practical ammeter, diagrammed in figure 4 below, consisting of an ideal ammeter in series with a $2\text{-k}\Omega$ resistor. The meter sees a full-scale deflection when the current through it is $50\mu\text{A}$. If we wished to construct a multi range ammeter reading full-scale values of 1 mA , 10 mA , or 100 mA , depending on the setting of a rotary switch, what should R_1 , R_2 , and R_3 be?

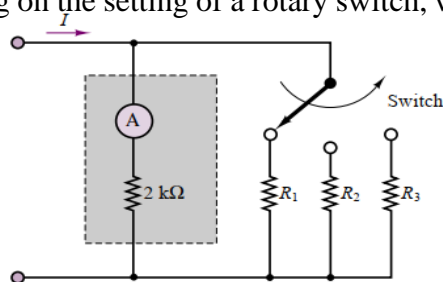


Figure 4

5. Find the maximum power transferred to resistor R in the circuit of figure 5 below.

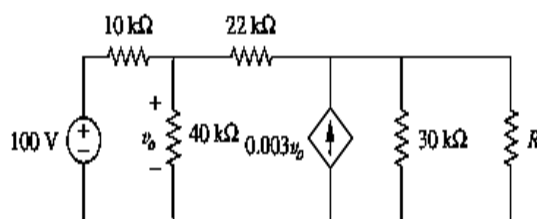


Figure 5

6. From an Automobile Ignition System, we consider the voltage generating system. The system is modeled by the circuit shown in the figure 6 below. The **12-V** source is due to the battery and alternator. The **4-Ω** resistor represents the resistance of the wiring. The ignition coil is modeled by the 8-mH inductor. The 1-μF capacitor (known as the condenser to auto-mechanics) is in parallel with the switch (known as the breaking points or electronic ignition which **opens at $t=0$ s**).

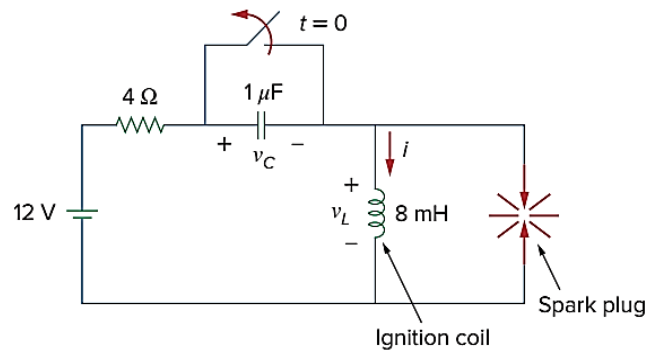


Figure 6

Thus,

- Determine the voltage drop $V_L(t)$ across the Ignition coil to create spark.
- Determine the voltage drop across the Capacitor $V_C(t)$ and Resistor model $V_R(t)$