

CH-5 Frequency Response of BJT and FET.

INTRODUCTION

The analysis so far has been limited to a particular range of frequencies by ignoring the effects of the capacitive elements and reducing the analysis to only resistive elements and sources of independent & controlled variety.

* In this chapter, we will investigate the frequency effects introduced by


1. the capacitive elements of the network (C_c , C_E & C_S) at low frequencies and
2. the smaller capacitive elements of the active device at high frequencies.

* The frequency response analysis of amplifiers extend ^{over} a wide range of frequencies, a logarithmic scale will be defined & used through out the analysis.


LOGARITHM: The use of logarithmic scale makes it comfortable plotting the frequency response of Amplifiers b/w wide limits.

- Advantages:-
1. The frequency response plot is compressed w/o loss of information.
Ex A frequency of $10,000 \text{ Hz}$ in linear scale becomes $\log_{10} 10^4 = 4$ in logarithmic scale.
Thus, the frequency plot is compressed
 2. The problem of dealing with huge numbers is overcome.

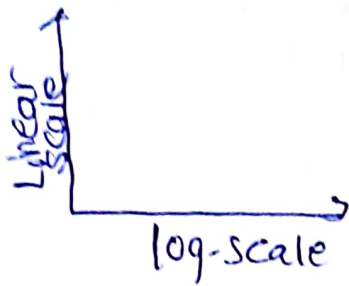- The use of log scales can significantly expand the range of variation of a particular variable on the graph.
- Most graph paper available is of the semilog or double-log variety



a) Semi-log graph

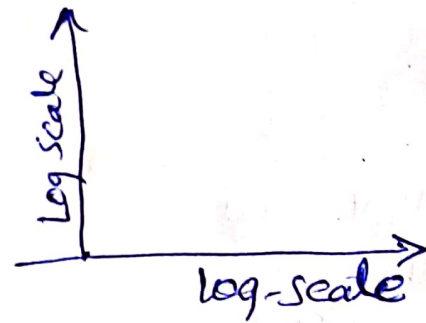

b) Double log graph

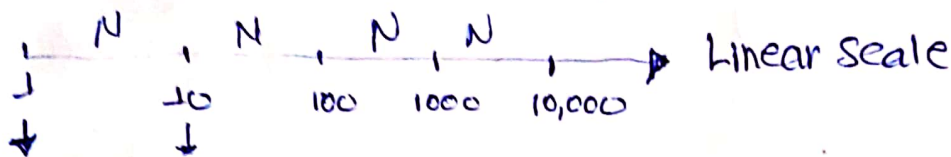


Fig: Conversion of linear scale to log scale

(2)

Decibels :- Decibel is used to compare two power levels on a logarithmic basis.

- The unit "bel" (B) is defined relating two power levels P_1 and P_2 as

$$G = \log_{10} (P_2/P_1) \text{ bel}$$

* As "bel" was found to be a large unit of measurement, the "decibel" (dB) is defined where 10 decibels = 1 bel

* Hence

$$G_{dB} = 10 \log_{10} (P_2/P_1) \text{ dB}$$

* $G_{dB} \rightarrow$ is a measure of difference in magnitude b/w two power levels, say o/p power level & input power level. Quite often the i/p power level (P_1) is taken as a reference power level ($P_1 = 1 \text{ mW}$, at $R_i = 600 \Omega$) in electronics


$$G_{dBm} = 10 \log_{10} \frac{P_2}{1 \text{ mW}} \text{ dBm}$$

In terms of voltage

$$G_{dB} = 10 \log_{10} \frac{P_2/P_1}{V_2^2/R_i / V_1^2/R_i} = 10 \log_{10} \frac{V_2^2/R_i}{V_1^2/R_i}$$

$$= 20 \log_{10} \frac{V_2}{V_1} \text{ dB, where } R_i - \text{i/p resistance}$$

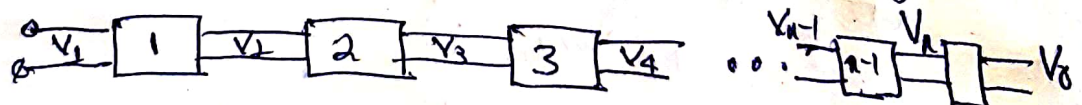The advantage of logarithmic r/ship is that the overall gain of a cascade s/s is simply the sum of individual gains.



The overall gain for "n" stage s/s is given by

$$G = G_1 \times G_2 \times G_3 \times \dots \times G_{n-1} \times G_n$$

$$\text{or } A_V = A_{V1} \times A_{V2} \times A_{V3} \times \dots \times A_{Vn-1} \times A_{Vn}$$

$$\frac{V_0}{V_1} = \frac{V_2}{V_1} \times \frac{V_3}{V_2} \times \frac{V_4}{V_3} \times \dots \times \frac{V_n}{V_{n-1}} \times \frac{V_0}{V_n}$$

In logarithmic r/ship

$$G_{dB} = 20 \log_{10} \frac{V_0}{V_1} = 20 \log_{10} \frac{V_2}{V_1} + 20 \log_{10} \frac{V_3}{V_2} + \dots + 20 \log_{10} \frac{V_0}{V_n}$$

(3)

where

$$G_{dB} = G_{V_1} + G_{V_2} + G_{V_3} + \dots + G_{V_n} \text{ dB}$$

Ex

Voltage gain V_o/V_i	dB-level
0.5	-6
0.707	-3
1	0
2	6
10	20
40	32
100	40
1000	60
10,000	80

Ex Find the magnitude gain corresponding to a voltage gain of

a) 100 dB

b) 200 dB

Soln (a) $G_{dB} = 20 \log \frac{V_o}{V_i} \Rightarrow 100 = 20 \log \frac{V_o}{V_i}$

$$\log \frac{V_o}{V_i} = \frac{100}{20} = 5$$

$$\Rightarrow \frac{V_o}{V_i} = 10^5$$

(b) $20 \log \frac{V_o}{V_i} = 200$

$$\log \frac{V_o}{V_i} = 10$$

$$\frac{V_o}{V_i} = 10^{10}$$

Ex A three-stage amplifier has a first-stage-voltage gain of 30; a second stage voltage gain of 200 & third stage gain of 400. Find the total voltage gain in dB

Soln 1st-stage: $G_1 = 20 \log 30 = 29.54 \text{ dB}$

2nd-stage: $G_2 = 20 \log 200 = 46 \text{ dB}$

3rd-stage: $G_3 = 20 \log 400 = 52 \text{ dB}$

(A)

Over gain

$$G_{dB} = G_1 + G_2 + G_3 = 29.54 + 46 + 52 = 127.54 \text{ dB}$$

Ex The input power to a device is 10,000W at a voltage of 1000V. The o/p power is 500W, while the o/p impedance is 20Ω.

- Find the power gain in dB
- Find the voltage gain in dB
- Explain why parts (a) & (b) agree or disagree

Soln

$$\text{a) } G_{dB} = 10 \log \frac{P_o}{P_i} = 10 \log \frac{500 \text{ W}}{10,000 \text{ W}} = 10 \log \frac{1}{20}$$
$$= -10 \log 20 = -10(1.301) = -13.01 \text{ dB}$$

$$\text{b) } G_V = 20 \log \frac{V_o}{V_i} = 20 \log \frac{\sqrt{P_o P_o}}{V_i} = 20 \log \frac{\sqrt{500 \times 20}}{1000}$$
$$= 20 \log \frac{100}{1000} = -20 \log 10 = -20 \text{ dB}$$

$$\text{c) } R_i = \frac{V_i^2}{P_i} = \frac{(1 \text{ kV})^2}{10 \text{ kW}} = \frac{10^6}{10^4} = 100 \Omega \neq R_o = 20 \Omega$$

Ex Determine G_{dBm} for an o/p power level of 25W

Soln

$$G_{dB} = 10 \log \frac{25 \text{ W}}{1 \text{ mW}} = 10 \log 25 \times 10^3$$
$$= 10 \log 25 + 30 = 13.98 + 30 = 43.98 \text{ dBm}$$

Ex The total dB gain of a 3-stage SLS is 120dB. Determine the dB gain each stage if the 2nd stage has twice the dB gain of the 1st & the third stage has 2.7 times the dB gain of the 1st.

② Determine the voltage gain of each stage

Soln ① $G_{dB} = G_1 + G_2 + G_3 = G_1 + 2G_1 + 2.7G_1 = 5.7G_1$

$$\Rightarrow 5.7G_1 = 120 \Rightarrow G_1 = 21.05 \text{ dB}$$

$$G_2 = 2 \times 21.05 = 42.1 \text{ dB}$$

$$G_3 = 2.7 \times 21.05 = 56.835 \text{ dB}$$

⑤

b) Stage-1

$$\frac{V_{o1}}{V_1} = \frac{V_2}{V_1} = 10^{\frac{AV}{20}} = 10^{\frac{21.05}{20}} = 10^{1.0526} \\ = 11.288$$

Stage-2

$$\frac{V_{o2}}{V_{i2}} = \frac{V_3}{V_2} = 10^{\frac{42.1}{20}} = 127.35$$

Stage-3

$$\frac{V_{o3}}{V_{i3}} = \frac{V_0}{V_3} = 10^{\frac{56.835}{20}} = 694.624$$

Q. An Amplifier has a voltage gain of 15 dB. If the o/p signal voltage is 0.8 V, determine the o/p voltage

Soln

$$GM = 20 \log \frac{V_0}{V_I}$$

$$15 \text{ dB} = 20 \log \frac{V_0}{V_I}$$

$$\frac{V_0}{V_I} = 10^{15/20} = 10^{0.75}$$

$$V_0 = V_I \cdot 10^{0.75} \\ = 0.8 \times 10^{0.75} = 4.5 \text{ V}$$

(6)

General Frequency considerations

All amplifier gain factors are functions of signal frequency. Up to this point, the analysis has been for the MID-band frequency spectrum. That is, we have assumed that the signal frequency is high enough that coupling & bypass capacitors can be treated as short ccts & at the same time, we have assumed that the signal frequency is low enough that parasitic capacitances can be treated as open ccts.

* In general, an amplifier gain factor versus frequency will resemble that shown below

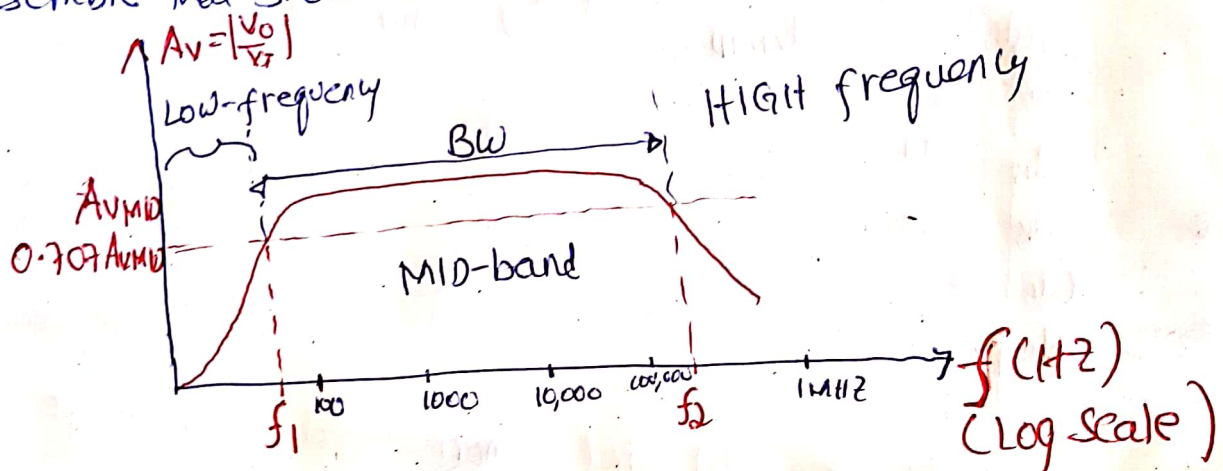


Fig: Gain Vs Frequency

* The frequencies f_1 & f_2 are generally called corner frequency, cut-off, band, break or half power frequencies.

$$P_{O_{MID}} = \frac{|V_o|^2}{R_o} = \frac{|A_{v_{MID}} V_i|^2}{R_o}$$

and at half power frequencies

$$P_{O_{HPF}} = \frac{|0.707 A_{v_{MID}} V_i|^2}{R_o} = 0.5 \frac{|A_{v_{MID}} V_i|^2}{R_o}$$

$$P_{O_{HPF}} = 0.5 P_{O_{MID}}$$

* The Bandwidth is given by

$$BW = f_2 - f_1$$

(7)

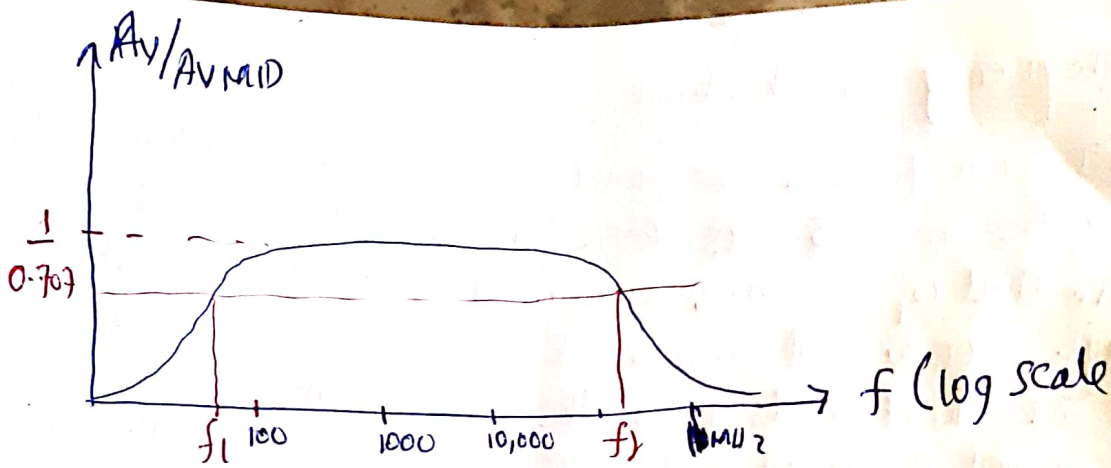


Fig: Normalized gain Vs frequency

* A decibel plot can be obtained as

$$\frac{A_v}{A_{vMID}} = 20 \log \left(\frac{A_v}{A_{vMID}} \right)$$

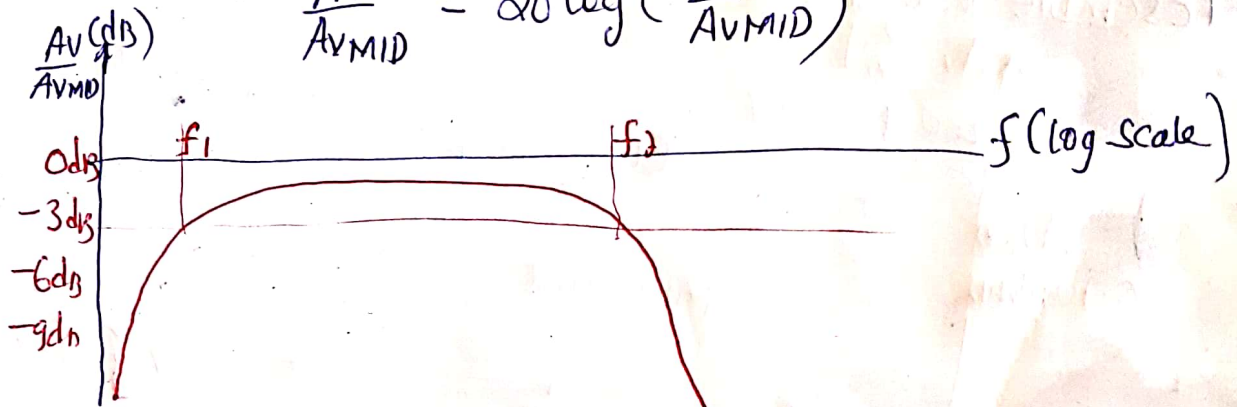


Fig: Decibel plot of normalized gain Vs frequency

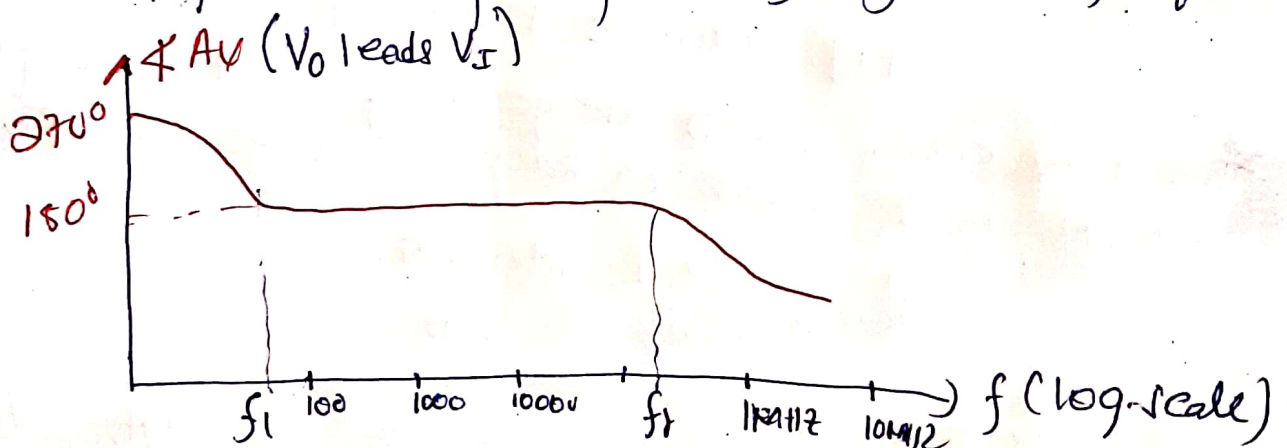


Fig: phase plot

(8)

Equivalent ccts

MIDBAND RANGE

- * Coupling & bypass capacitors are treated as short cct
- * Stray & transistor capacitors are treated as open cct

Low-frequency Range

- * Coupling and Bypass capacitors must be included in the Equivalent cct
- * The stray and transistor capacitance are treated as open cct

HIGH-Frequency Range

- * Coupling & Bypass capacitors are treated as short cct
- * The stray and transistor capacitance must be included in the analysis.

Low-Frequency Analysis

- * In this region, it is the R-C Combination formed by C_c , C_e and C_s and the n/w resistive parameters that determine the cut-off frequencies.
- * The Amp cct behaves as a simple High pass cct as shown below


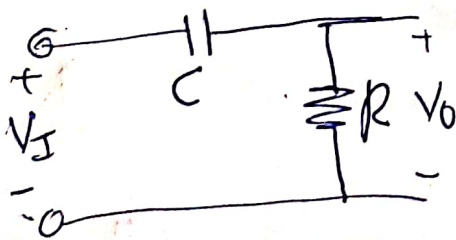


Fig: Equivalent cct for lower cut-off frequency

- * The capacitor behaves as short cct for very high frequency & open for a very low frequency


(9)

For HIGH Frequency

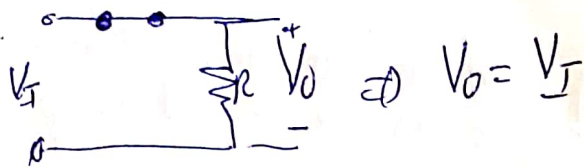


$$X_C = \frac{1}{2\pi f C} = 0 \Omega$$

For $f = 0$

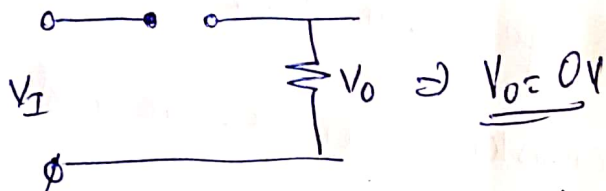

$$X_C = \frac{1}{2\pi f C} = \infty \Omega$$

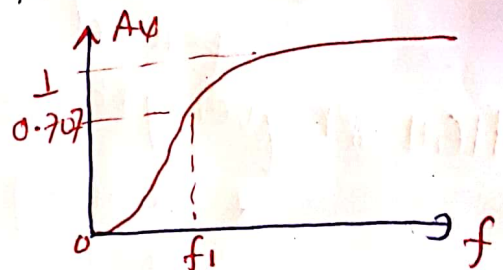* A typical frequency response b/w the two extremes is as shown below



* The o/p voltage is given by

$$V_O = \frac{R V_I}{R + jX_C} = \frac{R V_I}{R - jX_C}$$

* The magnitude of V_{out} is given by

$$|V_{out}| = \frac{R |V_{in}|}{\sqrt{R^2 + X_C^2}}$$

For the special case, when $X_C = R$

$$|V_{out}| = \frac{1}{\sqrt{2}} |V_{in}|$$

$$A_v = \left| \frac{V_O}{V_{in}} \right| = 0.707 \text{ at } X_C = R$$

$\Rightarrow$

$$f_1 = \frac{1}{2\pi RC} \rightarrow \text{corner frequency.}$$

In terms of log,

$$G_v = 20 \log A_v = 20 \log \frac{1}{\sqrt{2}} = -3 \text{ dB}$$

(10)

* The Voltage gain, A_v , can be written as

$$A_v = \frac{V_o}{V_i} = \frac{R}{R - jX_C} = \frac{R}{R - j\frac{1}{\omega C}} = \frac{1}{1 - j\frac{1}{\omega RC}}$$

$$= \frac{1}{1 - j(f_1/f)}$$

* The magnitude and phase of A_v are

$$A_v = \underbrace{\frac{1}{\sqrt{1 + (f_1/f)^2}}}_{\text{magnitude}} \angle \underbrace{\tan^{-1} f_1/f}_{\text{phase } \phi \text{ by which } V_o \text{ leads } V_i}$$

* In decibel the gain is given by

$$A_{v_{dB}} = 20 \log \frac{1}{\sqrt{1 + (f_1/f)^2}}$$

$$= -10 \log 1 + (f_1/f)^2$$

* For $f \ll f_1$

$$A_{v_{dB}} \approx -20 \log f_1/f$$

at $f = \frac{1}{2} f_1 \Rightarrow A_v = -6 \text{ dB}$

$f = \frac{1}{4} f_1 \Rightarrow A_v = -12 \text{ dB}$

$f = \frac{1}{10} f_1 \Rightarrow A_v = -20 \text{ dB}$

at $f = f_1, A_v = 0 \text{ dB}$

* The plot is shown below

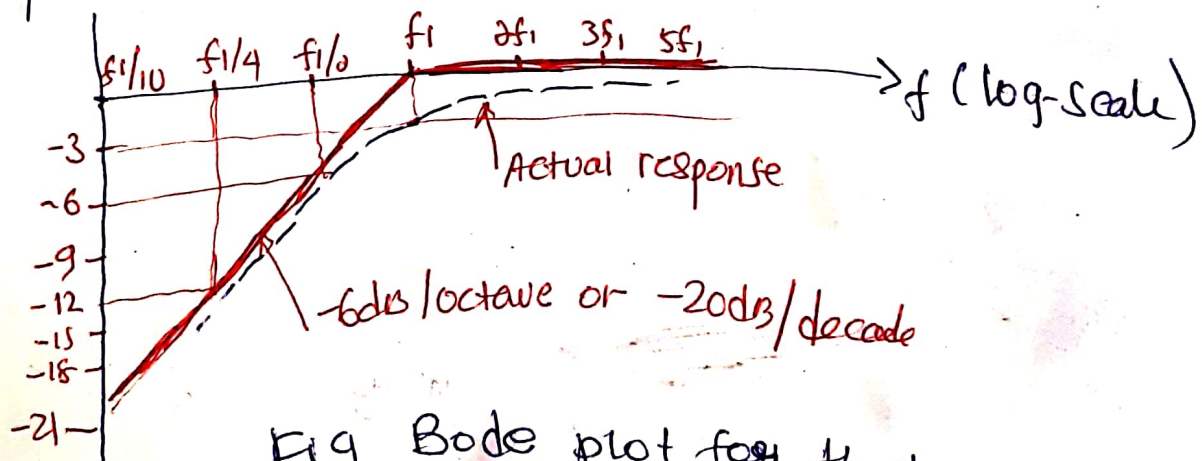


Fig Bode plot for the low-freq
vency region

(11)

* The piece-wise linear plot is called Bode plot of the magnitude Vs frequency

Remarks

- ① A change in frequency by a factor of 2, equivalent to 1 octave, results in a 6-dB change in the ratio
- ② For a 10:1 change in frequency, equivalent to 1 decade, there is a 20dB change in the ratio

The phase angle is determined by

$$\theta = \tan^{-1} f/f_1$$

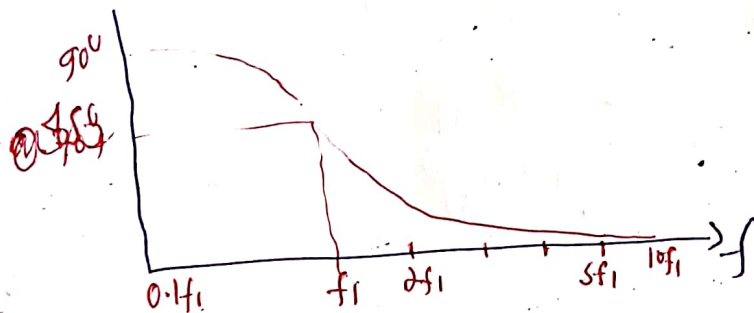



Fig :- phase plot vs frequency

⑫

$$V_i = \frac{1}{R_s + R_i - sX_C}$$

Low Frequency Response of BJT Amplifier

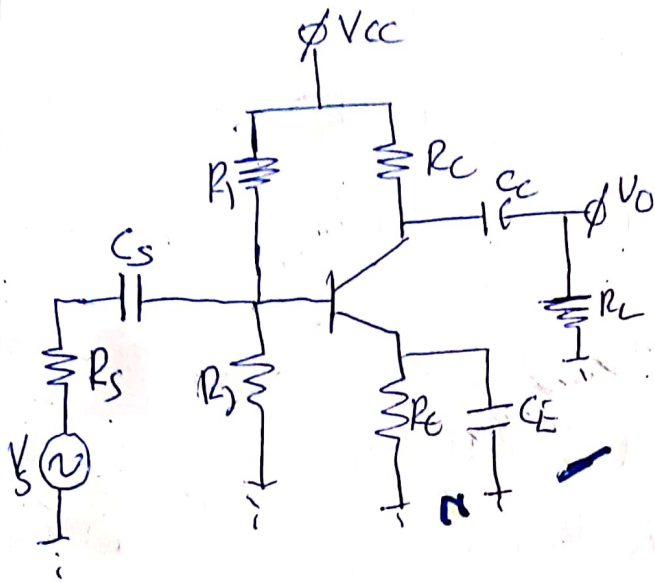Consider the voltage-divider BJT bias configuration.



Remark

- * The analysis can be extended to any BJT configuration.
- * C_s , C_E , C_C will no longer be considered as short circuit for low frequency analysis.
- * parasitic capacitance of the device can be considered as open circuit.

Analysis :- The effect of each capacitor is treated separately by considering the other two capacitors as a short circuit.

C_s :- C_C & C_E are considered as short circuit

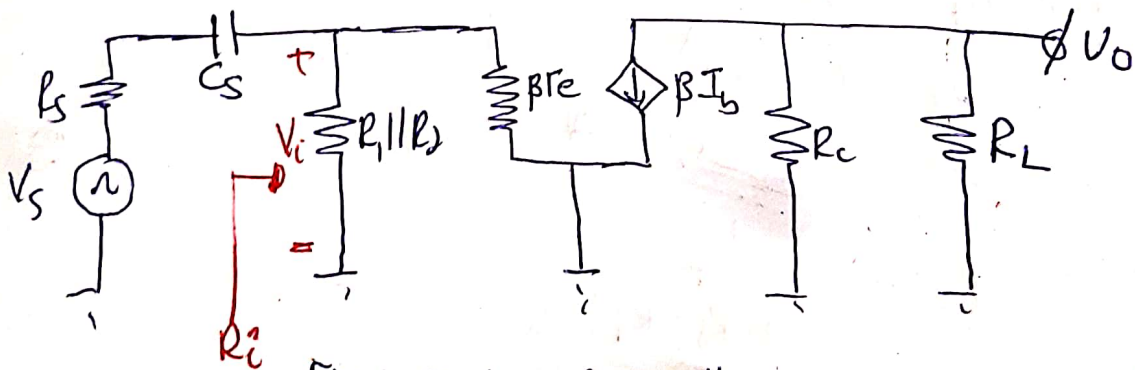


Fig: Determining the effect of C_s


$$R_i = (R_1 \parallel R_2) \parallel (\beta r_e)$$

and the o/p voltage, V_o , is given by

$$V_o = \frac{R_i V_s}{R_s + R_i - jX_{Cs}}$$

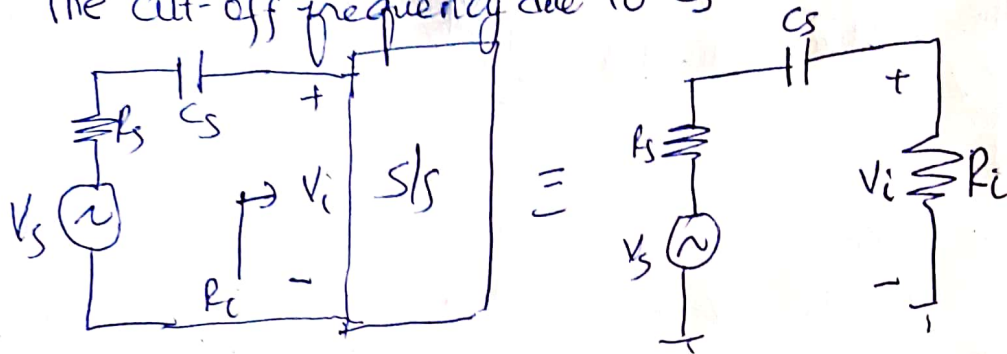(13)

The cut-off frequency due to C_S can be obtained as



$$\begin{aligned}\frac{V_i}{V_S} &= \frac{R_i}{R_S + R_i + \frac{1}{sC_S}} = \frac{R_i \{ sC_S \}}{1 + s(R_S + R_i)C_S} \\ &= \left(\frac{R_i}{R_S + R_i} \right) \left(\frac{s(R_S + R_i)C_S}{1 + s(R_S + R_i)C_S} \right) \\ &= \left(\frac{R_i}{R_S + R_i} \right) \left(\frac{1}{1 + \frac{1}{s(R_S + R_i)C_S}} \right)\end{aligned}$$

The frequency response is given by

$$\frac{V_i}{V_S} = \left(\frac{R_i}{R_S + R_i} \right) \left(\frac{1}{1 + j\left(\frac{f_0}{f}\right)} \right)$$

where $f_0 = \frac{1}{2\pi(R_S + R_i)C_S}$


The overall frequency response is given by

$$\frac{V_O}{V_S} = \underbrace{\left(\frac{R_{C1} \parallel R_L}{r_e} \right)}_{\text{Mid band Gain}} \underbrace{\left(\frac{R_i}{R_S + R_i} \right) \left(\frac{1}{1 + \frac{1}{s(R_S + R_i)C_S}} \right)}_{\text{the effect of } C_S}$$


(14)

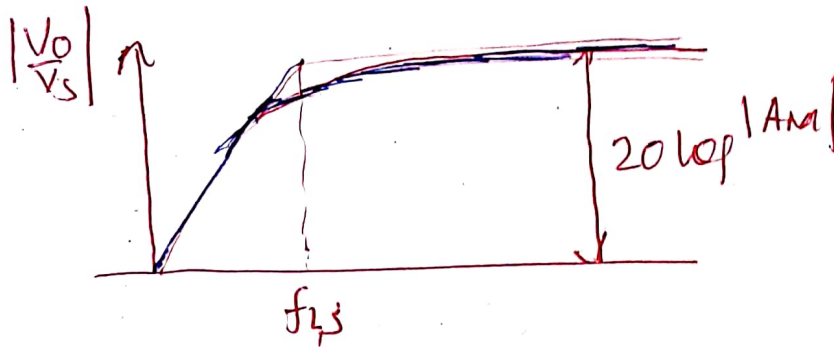(15)


$$f_{LS} = \frac{1}{2\pi(R_S + R_i)C_S}$$



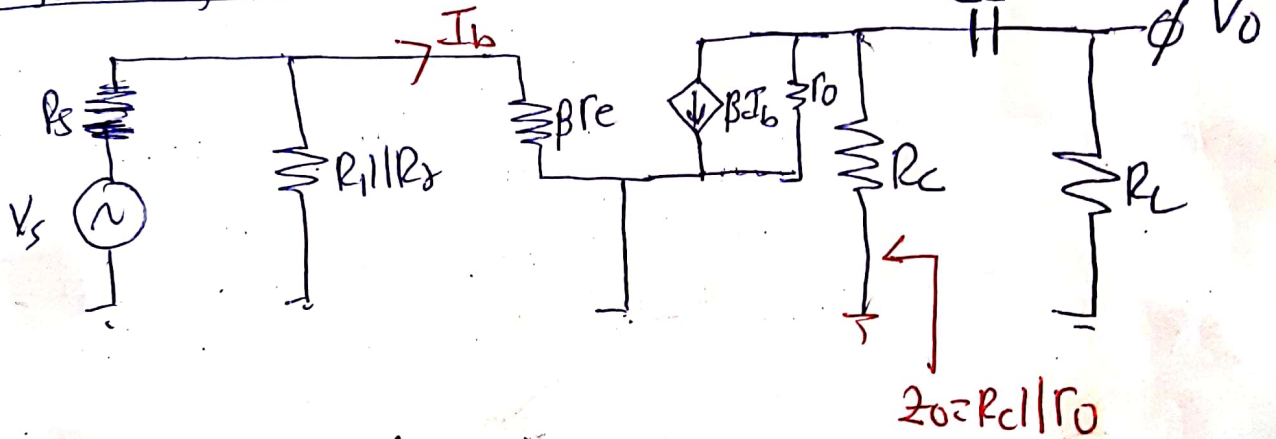The effect of C_C :- C_S & C_E are assumed ^{as} short ccted




The reduced equivalent cct becomes

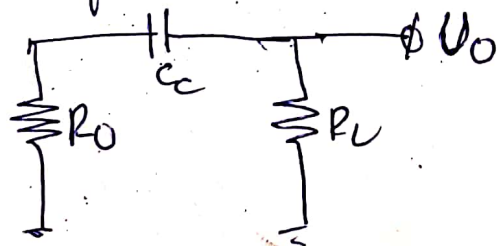

The required cut-off frequency is given by

$$f_{LC} = \frac{1}{2\pi(R_o + R_L)C_C}$$

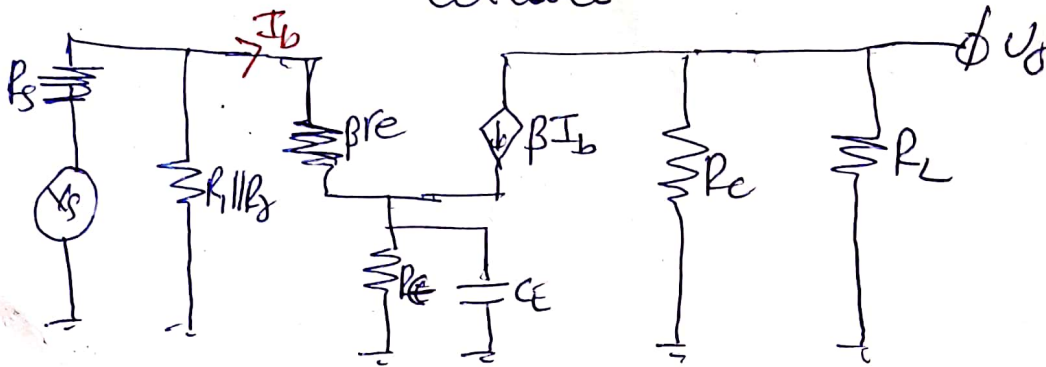The effect of CE :- C_s & C_c are considered as short circuit.



$$f_{LE} = \frac{1}{2\pi R_e C_e}$$

where $R_e = R_e \parallel \left(\frac{R_s'}{\beta} + r_e \right)$

$$R_s' = R_s \parallel R_1 \parallel R_2$$

Q. Determine the cut-off frequencies for the network shown using the following parameters


$$C_s = 10\text{ nF}, \quad C_e = 20\text{ nF}, \quad C_c = 1\text{ nF}$$

$$R_1 = 40\text{ k}\Omega, \quad R_2 = 10\text{ k}\Omega, \quad R_e = 2\text{ k}\Omega, \quad R_c = 4\text{ k}\Omega$$

$$R_L = 2.2\text{ k}\Omega$$

$$\beta = 100, \quad r_o = \infty, \quad V_{CC} = 20\text{ V}$$

Solu

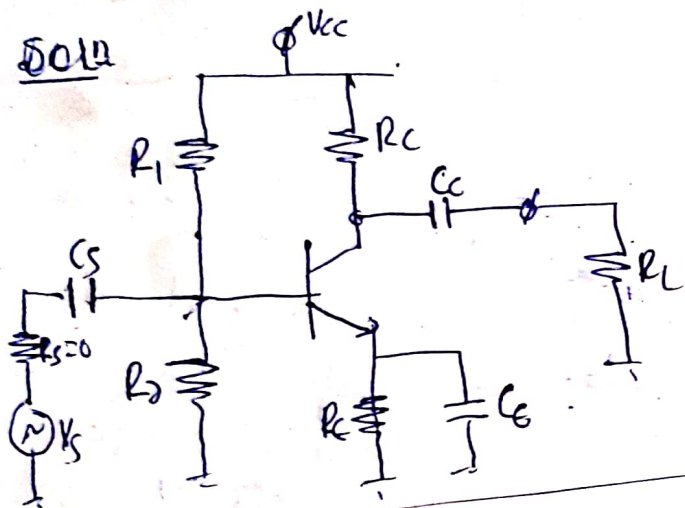

Solu

Test condition

$$\beta R_e \geq 100 \times 2\text{ k}\Omega = 200\text{ k}\Omega$$

$$10 R_2 = 100\text{ k}\Omega$$

$$\beta R_e > 10 R_2 \quad \checkmark \text{ Condition met}$$

x we use approximate method

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{10\text{ k}\Omega \times 20\text{ V}}{40\text{ k}\Omega + 10\text{ k}\Omega} = 4\text{ V}$$

$$V_E = V_B - V_{BE} = 4\text{ V} - 0.7\text{ V} = 3.3\text{ V}$$

$$I_E = \frac{V_E}{R_e} = \frac{3.3\text{ V}}{2\text{ k}\Omega} = 1.65\text{ mA}$$

$$r_e = \frac{V_T}{I_E} = \frac{26\text{ mV}}{1.65\text{ mA}} = 15.76\text{ }\Omega$$

$$\beta R_e = 100 \times 15.76\text{ }\Omega = 1.576\text{ k}\Omega$$

$$\text{Midband gain, } A_m = \frac{V_o}{V_i} = -\frac{R_c \parallel R_L}{r_e} = -\frac{(4\text{ k}\Omega) \parallel (2.2\text{ k}\Omega)}{15.76\text{ }\Omega} \approx -90$$

$$C_s \quad R_i = R_1 \parallel R_2 \parallel \beta R_e = 40\text{ k}\Omega \parallel 10\text{ k}\Omega \parallel 1.576\text{ k}\Omega \approx 1.32\text{ k}\Omega$$

$$f_{LS} = \frac{1}{2\pi R_i C_s} = \frac{1}{2\pi \times 1.32 \times 10^3 \times 10 \times 10^{-6}} = 12.06\text{ Hz}$$

(17)

$$C_c \quad R_o = R_c \parallel R_o \approx R_c = 4k\Omega$$

$$f_{LC} = \frac{1}{2\pi(R_o + R_c)C_c} = \frac{1}{6.28(4k\Omega + 2.2k\Omega)1nF}$$

$$= 25.68 \text{ Hz}$$

$$C_E \quad R_e = R_E \parallel \left(\frac{R_1 \parallel R_2}{\beta} + r_e \right)$$

$$= 2k\Omega \parallel \left(\frac{8k\Omega}{100} + 15.76\Omega \right)$$

$$= 91.38\Omega$$

$$f_{LE} = \frac{1}{2\pi R_e C_E} = \frac{1}{6.28 \times 91.38 \times 20nF} = 87.13 \text{ Hz}$$

Since $f_{LE} \gg f_{LC}$ or f_{LS} , the bypass capacitor C_E determines the lower cut-off frequency of the Amplifier.

Ex Repeat the above Example with a source resistance $R_S = 1k\Omega$

(b) Sketch the frequency response using a bode plot

Soln a) The dc-condition remains the same

$$r_e = 15.76\Omega$$

$$\beta r_e = 1.576k\Omega$$

$$\text{Mid band gain, } A_M = \frac{V_o}{V_i} = \frac{-R_c \parallel R_L}{r_e} = -90$$

$$R_i = R_1 \parallel R_2 \parallel \beta r_e = 1.32k\Omega$$

$$\text{Overall gain} = A_v = A_M \times \frac{R_i}{R_S + R_i}$$

$$= -90 \times \frac{1.32k\Omega}{2.32k\Omega} = -51.21$$

$$C_S : f_{LS} = \frac{1}{2\pi(R_S + R_i)C_S} = \frac{1}{2\pi(2.32k\Omega) \times 10nF}$$

$$= \frac{10.0}{6.28 \times 2.32} \approx 6.86 \text{ Hz}$$

(18)

$$C_c \quad f_{LC} = \frac{1}{2\pi(R_c + R_L)C_c} = \frac{1}{6.28(6.2k\Omega) \times 10^{-6}F}$$

$$= 25.68 \text{ Hz as before}$$

$$C_E: \quad R_e = R_e \parallel \left(\frac{R_s \parallel R_1 \parallel R_2}{\beta} + r_e \right)$$


$$= 2k\Omega \parallel \left(\frac{0.889k\Omega}{100} + 15.76\Omega \right)$$

$$= 24.35\Omega$$

$$f_{LE} = \frac{1}{2\pi R_e C_E} = \frac{1}{6.28 \times 24.35 \times 20 \times 10^{-6}}$$

$$\approx 327 \text{ Hz} \quad \text{vs } 87.13 \text{ Hz w/o } R_s$$

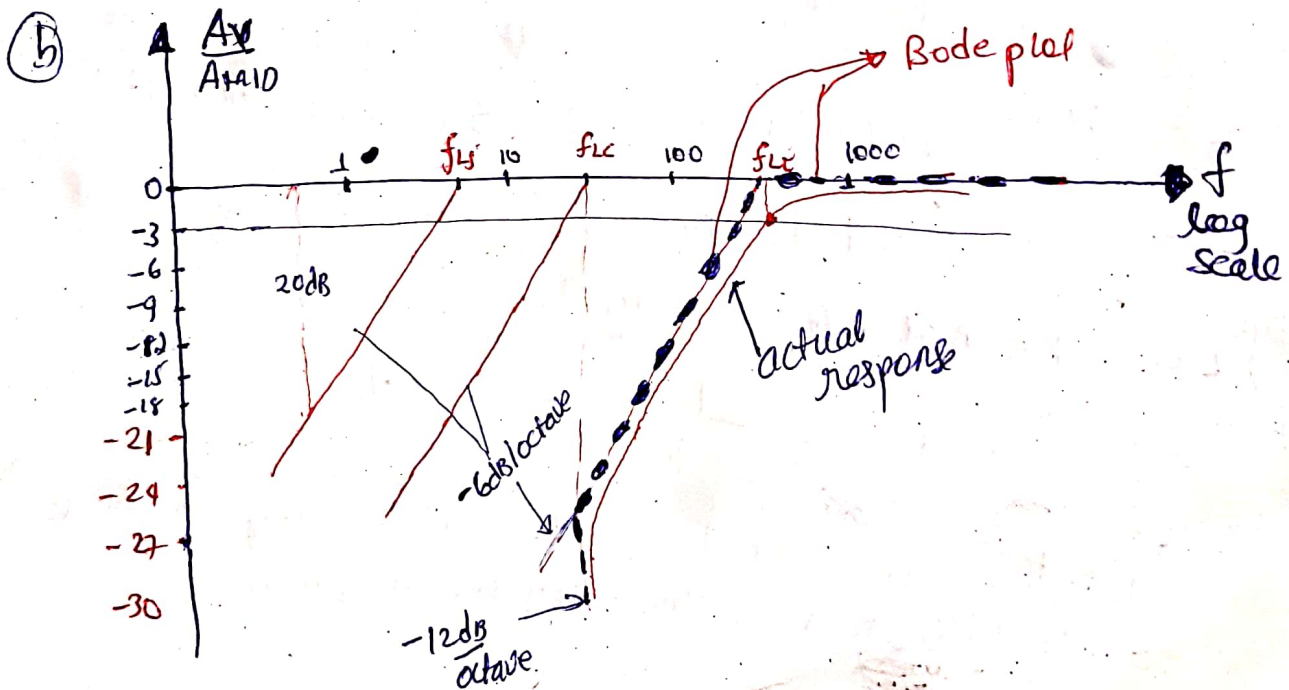The result is a severe reduction in overall gain, but a corresponding reduction in the lower cut-off frequency.



19

Ex: Repeat the analysis of the above example with $r_o = 40k\Omega$.

Soln

$$r_e = 15.76\Omega$$

$$A_{v_{mid}} = -\frac{R_c \parallel R_L \parallel r_o}{r_e} = -\frac{4k\Omega \parallel 2.2k\Omega \parallel 40k\Omega}{15.76\Omega}$$

$$= -86.97$$

C_s : f_{Ls} : r_o do not affect R_o

Since $\therefore f_{Ls} = \frac{1}{2\pi(R_s + R_i)C_s}$

$$f_{Ls} = \frac{1}{2\pi(2.32k\Omega)10\mu F} = 6.86 \text{ Hz}$$

C_c : Now $R_o = R_c \parallel r_o = 4k\Omega \parallel 40k\Omega = 3.636k\Omega$

$$f_{Lc} = \frac{1}{2\pi(R_o + R_L)C_c} = \frac{1}{2\pi(3.636k\Omega + 2.2k\Omega)1\mu F}$$
$$= 27.28 \text{ Hz}$$

f_{Le} : R_e not affected by r_o

$$f_{Le} = \frac{1}{2\pi R_e C_e} = 327 \text{ Hz}$$


In total the effect of r_o on the frequency response is to slightly reduce the mid band gain.

(2e)


(21)

Low-frequency Response - FET Amplifier

Consider the self bias configuration

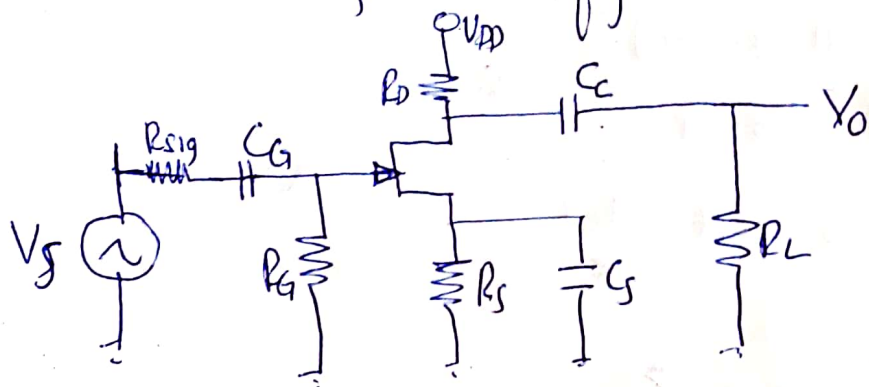

The ac-equivalent ckt is shown below

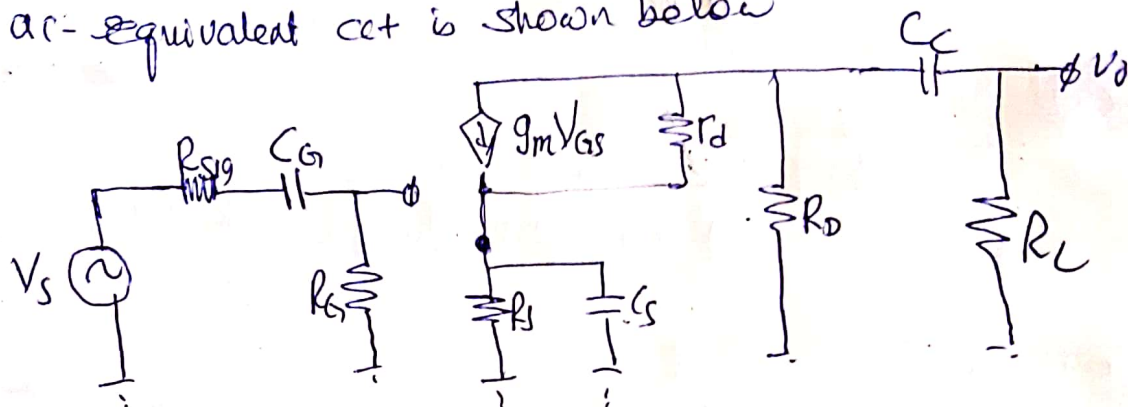

C_G :- C_S & C_C are considered short-cct

$$f_{LG} = \frac{1}{2\pi(R_{sig} + R_i)C_G}$$

where $R_i = R_G$

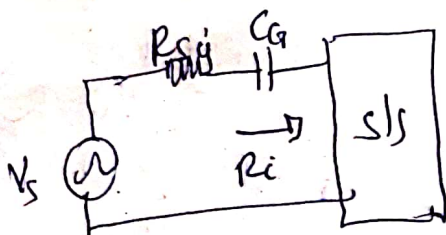



Fig: Determining the effect of C_G

(21)

C_c :- C_G & C_S are short ccted

$$f_{Lc} = \frac{1}{2\pi (R_o + R_L) C_c}$$

where $R_o = R_D || r_d$

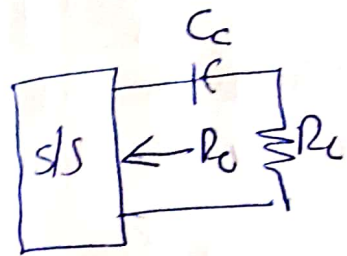

C_s :- C_c & C_G are short ccted


$$f_{Ls} = \frac{1}{2\pi R_{eq} C_s}$$

where

$$R_{eq} = \frac{R_s}{1 + R_s (1 + g_m r_d) / (r_d + R_D || R_L)}$$

for $r_d = \infty$, R_{eq} becomes
 $R_{eq} = R_s || \frac{1}{g_m}$

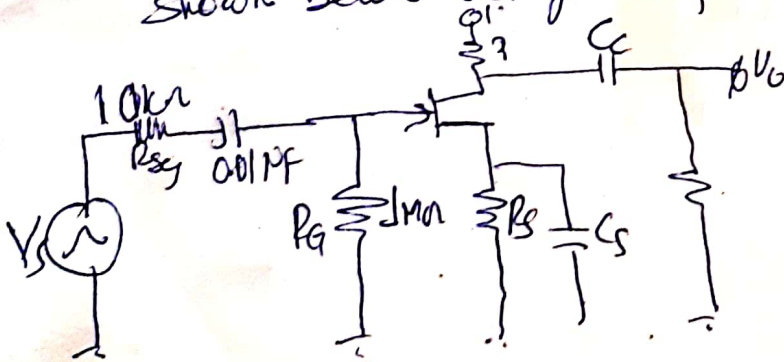Q. a) Determine the lower cut-off frequency for the n/w shown below using the following parameters



$$C_G = 0.01 \mu F$$

$$C_S = 2 nF$$

$$C_c = 0.5 \mu F$$

$$R_{sg} = 10 k\Omega$$

$$R_G = 1 M\Omega$$

$$R_D = 4.7 k\Omega$$

$$R_S = 1 k\Omega$$

$$R_L = 2.2 k\Omega$$

$$I_{DSS} = 8 mA$$

$$V_P = -4 V$$

$$V_{DD} = 20 V$$

$$r_d = \infty$$

b) Sketch the frequency response using Bode-plot

(22)

$$2\pi R_{eq} C_s = 2\pi (333.33 \mu) 2 nF = 238.73 Hz$$

Soln

DC - Analysis

$$I_D = I_{DSS} (1 - V_{GS}/V_p)^2 = 8 (1 + V_{GS}/4)^2$$

$$V_{GS} = -I_D R_s = -I_D$$

$$I_D = 8 \left(1 - \frac{I_D}{4}\right)^2 = 8 \left(1 - \frac{I_D}{2} + \frac{I_D^2}{16}\right)$$

$$I_D = 8 - 4I_D + \frac{I_D^2}{2}$$

Solving the quadratic equation

$$V_{GS} = -2V \quad I_{DQ} = 2mA$$

$$g_{m0} = \frac{2I_{DSS}}{|V_p|} = \frac{2 \times 8mA}{-4V} = 4mS$$

$$g_m = g_{m0} \left(1 - \frac{V_{GSQ}}{V_p}\right) = 4mS \left(1 - \frac{2}{4}\right) = 2mS$$

C_G

$$f_L = \frac{1}{2\pi (R_{sig} + R_i) C_G} = \frac{1}{2\pi (10k\Omega + 1M\Omega) (0.01\mu F)} \\ = 15.8 Hz$$

C_C

$$f_{LC} = \frac{1}{2\pi (R_o + R_L) C_C} = \frac{1}{2\pi (4.7k\Omega + 2.2k\Omega) (0.5\mu F)} \\ = 46.13 Hz$$

C_S


$$R_{eq} = R_s \parallel \frac{1}{g_m} = 1k\Omega \parallel \frac{1}{2mS} = 1k\Omega \parallel 0.5k\Omega \\ = 333.33\Omega$$

$$f_{LS} = \frac{1}{2\pi R_{eq} C_S} = \frac{1}{2\pi (333.33\Omega) (2\mu F)} \\ = 238.73 Hz$$

(23)

b) The mid band gain

$$\begin{aligned} A_{V_{MID}} &= -g_m(R_D || R_L) \\ &= -2mS(4.7k\Omega || 2.2k\Omega) \\ &= -2mS \times 1.499k\Omega \\ &\approx -3 \end{aligned}$$

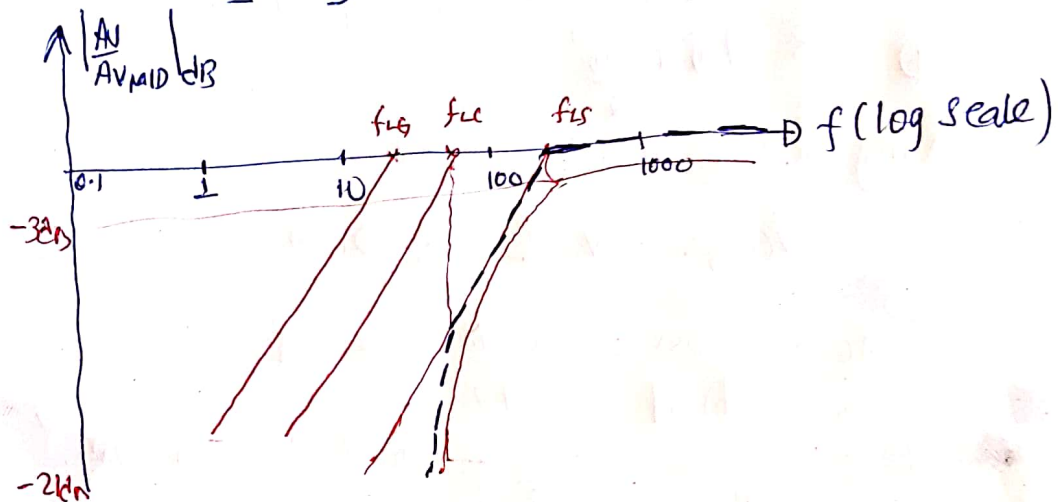


24

capacitor

MILLER EFFECT CAPACITANCE

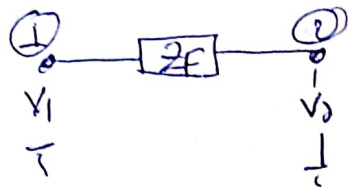* Consider the general ckt shown in the figure, where the floating impedance, Z_F , appears b/n node 1 & 2. We wish transform Z_F to two grounded impedances on the inp & output sides, while ensuring all the currents and voltages in the ckt remains unchanged.




- * To determine Z_1 & Z_2 , we make two observations.
- 1) The current drawn by Z_F from node 1 must be equal to that drawn by Z_1
 - 2) The current injected to node 2 must be equal to that injected by Z_2

The requirements are

$$\frac{V_1 - V_2}{Z_F} = \frac{V_1}{Z_1}$$
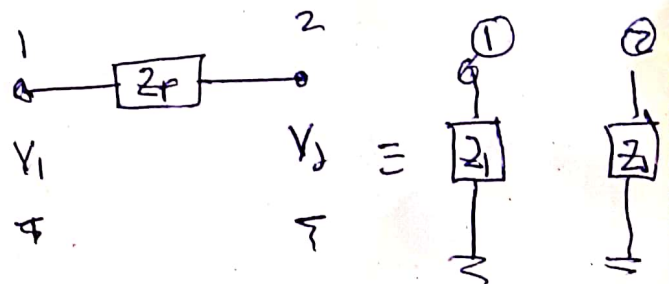
$$\frac{V_1 - V_2}{Z_F} = \frac{-V_2}{Z_2}$$



* Denoting the voltage gain from node 1 to node 2 by A_0 , we obtain

$$Z_1 = \frac{Z_F}{1 - A_0} \quad \& \quad Z_2 = \frac{A_0 Z_F}{A_0 - 1} = \frac{Z_F}{1 - \frac{1}{A_0}}$$

Called Miller's theorem,

* Now consider Z_F is a single capacitor, C_F , tied b/n the inp & op of an inverting Amplifier as shown below

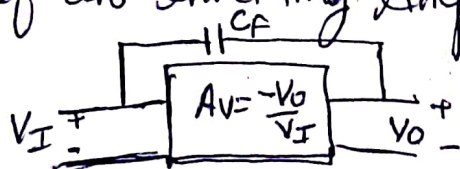


Fig: Inverting Amplifier with floating capacitor

25

Miller's theorem : It states that if an impedance Z is connected b/w the o/p and o/p terminals of a n/w which provides a voltage gain of A , an equivalent ckt that gives the same effect can be drawn by removing Z & connecting an impedance $Z_i = \frac{Z}{1-A}$ across the input & $Z_o = \frac{ZA}{A-1}$ across the o/p as shown below

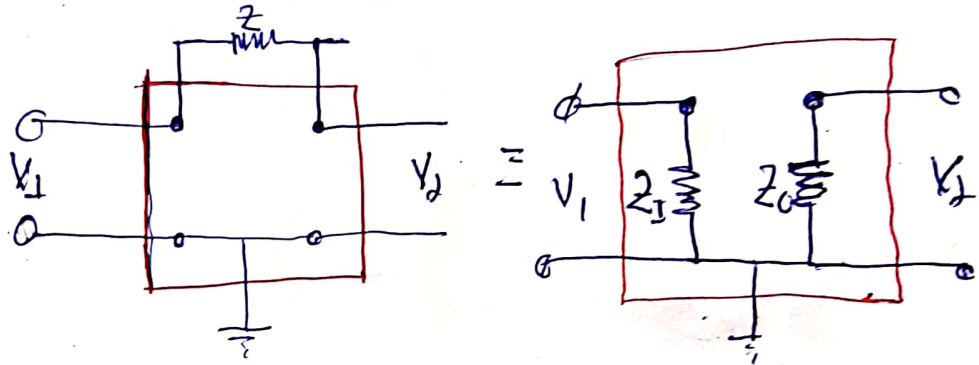


Fig Miller's theorem

26

$$Z_1 = \frac{Z_F}{1 - A_0} = \frac{Z_F}{1 - A_v} = \frac{1}{(1 - A_v) C_F s}$$

$\Rightarrow$ The o/p has a capacitor value $(1 - A_v) C_F$, as if " C_F " is amplified by a factor of $(1 - A_v)$

- The effect of C_F at the o/p can be obtained as

$$Z_2 = \frac{Z_F}{1 - \frac{1}{A_0}} = \frac{Z_F}{1 - \frac{1}{A_v}} = \frac{1}{(1 - \frac{1}{A_v}) C_F s}$$

$\Rightarrow$ The o/p has a capacitor of value $(1 - \frac{1}{A_v}) C_F$

* In general, the Miller effect input capacitance is defined by

$$C_{M_i} = (1 - A_v) C_F$$

& the Miller output capacitance is defined by

$$C_{M_o} = (1 - \frac{1}{A_v}) C_F$$

27

Fig Bode plot for the op-amp

HIGH - Frequency Analysis

- In this region, it is the R-C combination formed by the various parasitic capacitances of the transistor (C_{be} , C_{bc} , C_{ce}) and wiring capacitances (C_{wi} , C_{wo}) and the n/w resistive parameters that determine the cut-off frequencies
- The Amplifier circuit behaves as a simple low pass ckt as shown below

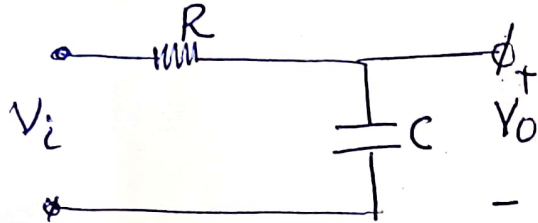


Fig:- RC-combination that will define a high-cut-off frequency.

* The voltage gain, A_v , can be written as

$$A_v = \frac{V_o}{V_i} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$

$$= \frac{1}{1 + j(f/f_d)} \quad ; \quad \text{where } f_d = \frac{1}{2\pi RC}$$

* The magnitude, $|A_v|$:

$$|A_v| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} = \frac{1}{\sqrt{1 + (f/f_d)^2}}$$

$$|A_v|_{dB} = -10 \log 1 + (f/f_d)^2$$

The bode-plot of $|A_v|_{dB}$ is shown below


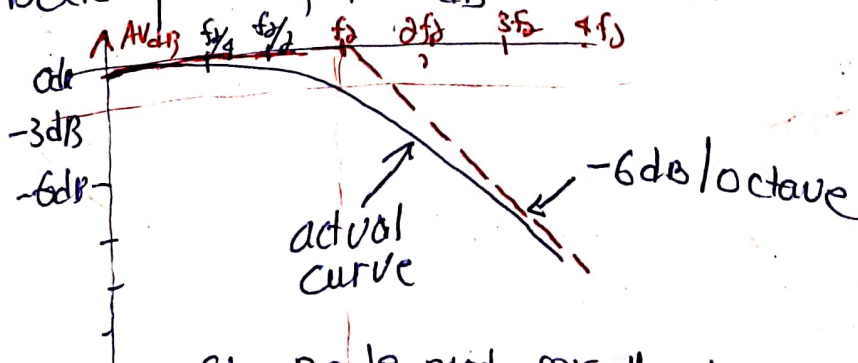


Fig Bode plot for the high frequency region


HIGH FREQUENCY RESPONSE OF BJT

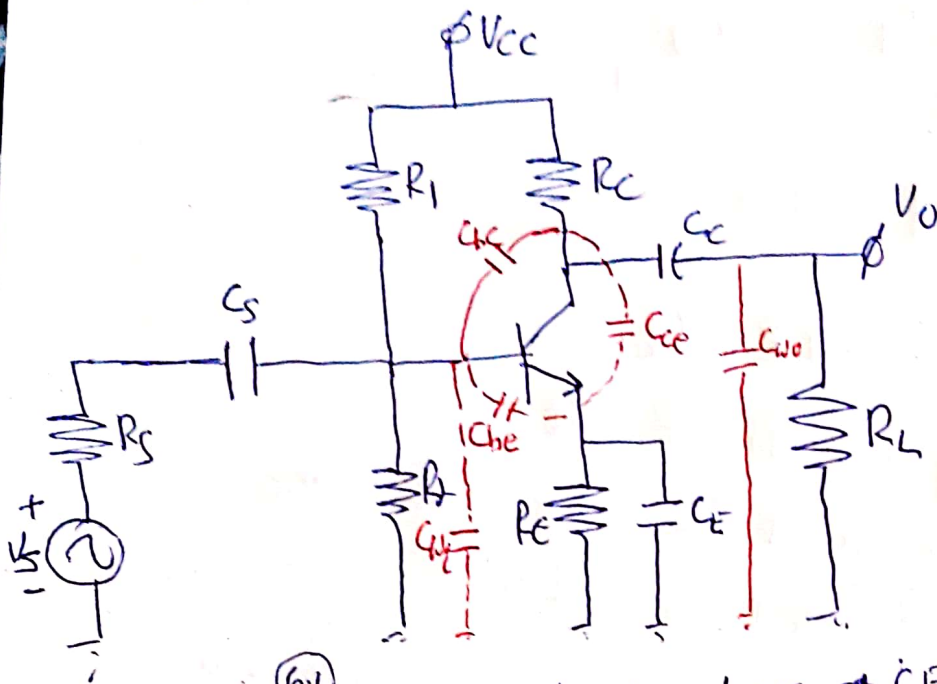A high frequency ac equivalent model for the network of Fig 6.1 appears in Fig 6.2 a & b



* parasitic capacitance
 C_{be}, C_{bc}, C_{ce}
 * wiring capacitances
 C_{wi} - inp side
 C_{wo} - out side

Fig. (6.1) Voltage-dividing bias at CE-configuration at high frequency

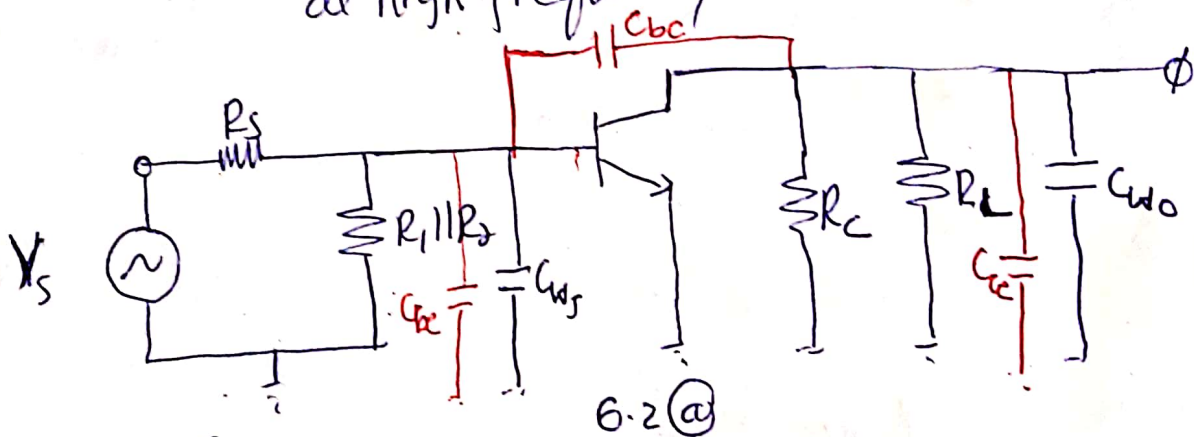

6.2(a)

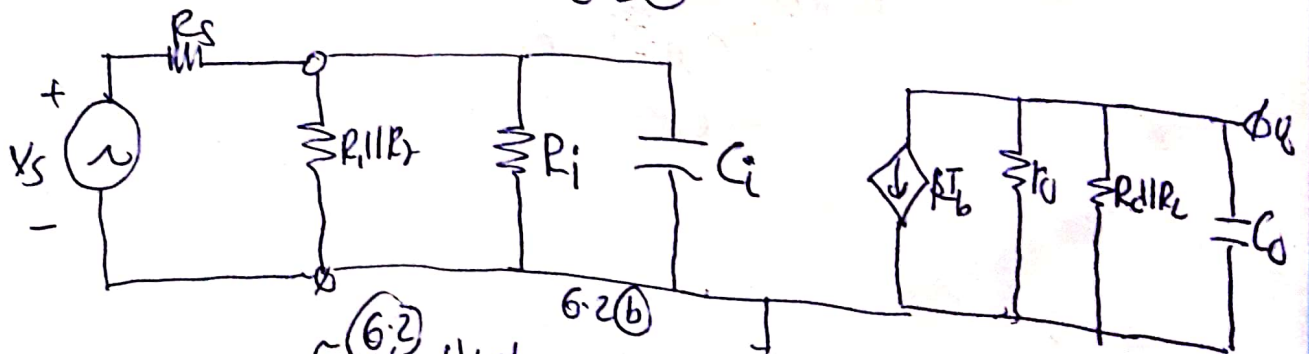



Fig. (6.2) High frequency ac-equivalent model

$$C_i = C_{wi} + C_{be} + C_{mi}$$

$$C_o = C_{wo} + C_{ce} + C_{mo}$$



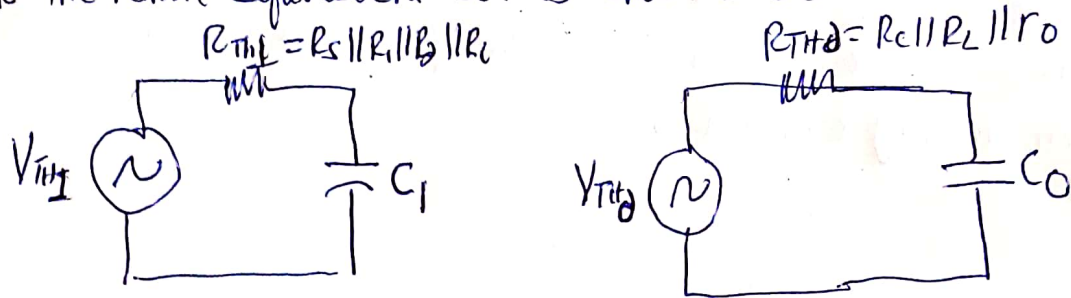The Thevenin equivalent ckt is shown below



The 3dB cut-off frequency is defined by

$$f_{H1} = \frac{1}{2\pi R_{TH1} C_i}$$

with

$$R_{TH1} = R_s \parallel R_1 \parallel R_2 \parallel \beta R_e$$

$$C_i = C_{xLi} + C_{be} + C_{mi} = C_{xLi} + C_{be} \\ = C_{wLi} + C_{be} + (1 - A_v) C_{bc}$$

The effect of C_i is

* * to reduce the total impedance of the parallel combination of R_1, R_2, R_i

* * The result is a reduced level of voltage across C_i and a reduction in I_b , & a gain for the s/s

For the o/p network

$$f_{H0} = \frac{1}{2\pi R_{TH2} C_o}$$

with

$$R_{TH2} = R_c \parallel R_L \parallel R_o$$

$$C_o = C_{wLo} + C_{ce} + C_{mo} \\ = C_{wLo} + C_{ce} + (1 - \frac{1}{A_v}) C_{bc}$$

30

Ex For the n/w shown with parameters

$$R_s = 1k\Omega, R_1 = 40k\Omega, R_2 = 10k\Omega, R_E = 2k\Omega, R_C = 4k\Omega$$

$$R_L = 2.2k\Omega, C_S = 10\mu F, C_C = 1\mu F, C_E = 20\mu F$$

$$\beta = 100, r_o = \infty\Omega, V_{CC} = 20V$$

$$\text{with } C_{be} = 36pF, C_{bc} = 4pF, C_{ce} = 1pF, C_{wC} = 6pF, C_{wE} = 8pF$$

a) Determine f_{H_i} & f_{H_o}

b) Find f_B & f_T

c) Sketch the frequency response for the high-frequency region using a Bode plot & determine the cut-off frequency

d) ~~what~~ Sketch the overall frequency response

Soln using Approximate method ($\beta R_E \gg 10 R_2$)

DC-Analysis

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = 4V$$

$$V_E = V_B - V_{BE} = 4V - 0.7V = 3.3V$$

$$I_E = \frac{V_E}{R_E} = \frac{3.3V}{2k\Omega} = 1.65mA$$

$$r_e = \frac{V_T}{I_E} = \frac{25mV}{1.65mA}$$

$$I_E = 1.65mA$$

$$r_e = 15.76\Omega$$

$$\beta r_e = 100 \times 15.76 = 1.576k\Omega$$

MID-BAND GAIN (A_{MID})

$$A_{MID} = \frac{V_o}{V_i} = \frac{-R_C \parallel R_L}{r_e} = -90$$

$$R_i = R_1 \parallel R_2 \parallel \beta r_e = 1.32k\Omega$$

AC-Analysis

$$R_{TH} = R_s \parallel R_1 \parallel R_2 \parallel R_i = 1k\Omega \parallel 40k\Omega \parallel 10k\Omega \parallel 1.32k\Omega$$

$$= 0.531k\Omega \quad 531\Omega$$

$$1.576k\Omega$$

$$1.576k\Omega$$

$$C_i = C_{wC} + C_{be} + (1 - A_v) C_{bc}$$

$$= 6pF + 36pF + (1 + 90) 4pF$$

$$= 406pF$$

$$f_{H_S} = \frac{1}{2\pi R_{TH} C_i} = \frac{1}{2\pi (0.531k\Omega) (406pF)} = 738.24kHz$$

~~20~~ 21

$$R_{TH2} = R_C \parallel R_L = 4k\Omega \parallel 2.2k\Omega = 1.419k\Omega$$

$$C_0 = C_{W0} + C_{ce} + C_{M0}$$

$$= 8pF + 1pF + \left(1 + \frac{1}{90}\right) 4pF$$

$$= 13.04pF$$

$$f_{H0} = \frac{1}{2\pi R_{TH0} C_0} = \frac{1}{2\pi \times 1.419k\Omega \times 13.04pF}$$

$$= \underline{\underline{8.6MHz}}$$

b)

$$f_\beta = \frac{1}{2\pi \beta_{mid} r_e (C_{ce} + C_{bc})}$$


$$= \frac{1}{2\pi \times 100 \times 15.76 \times (36pF + 4pF)}$$

$$= \underline{\underline{2.52MHz}}$$

$$f_T = \beta_{mid} f_\beta = 100 \times 2.52MHz$$

$$= \underline{\underline{252MHz}}$$

c)

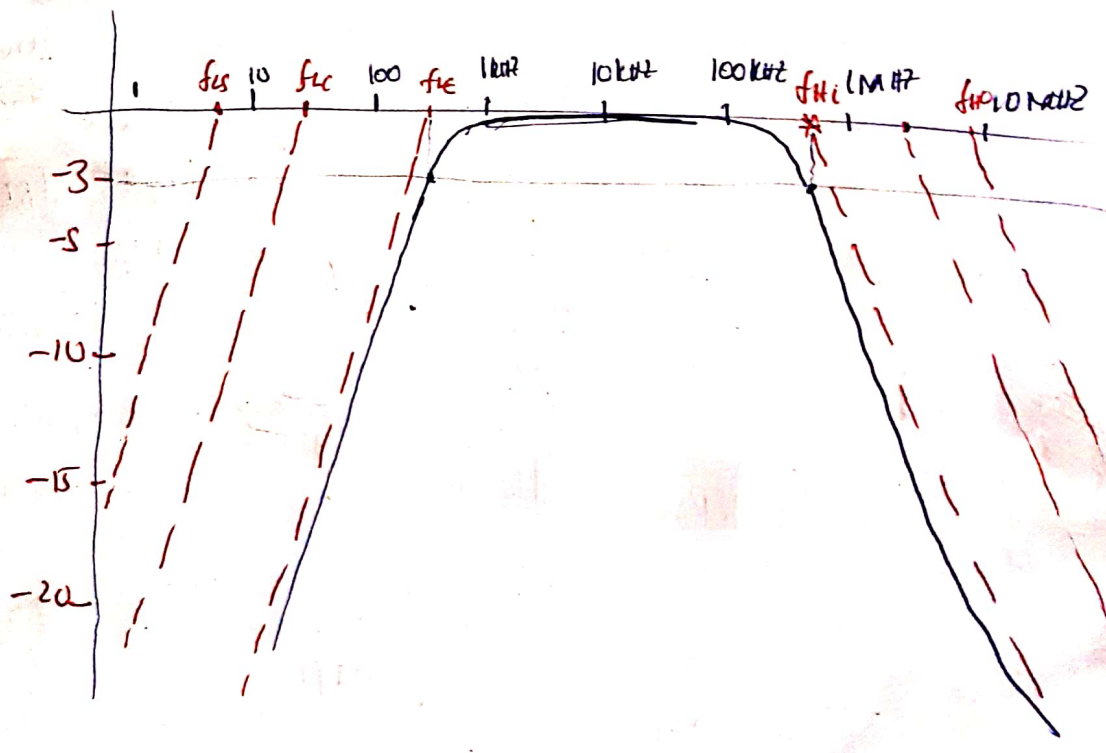

HIGH-Frequency Response - JFET Amplifier

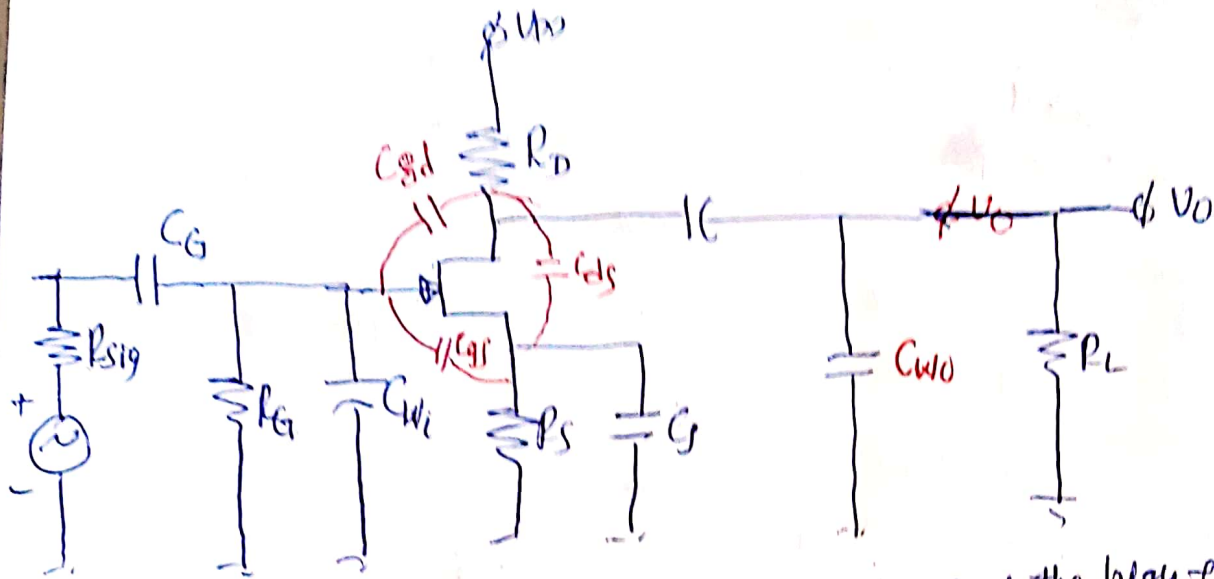


Fig: Capacitive elements that affect the high-frequency response of JFET Amplifier

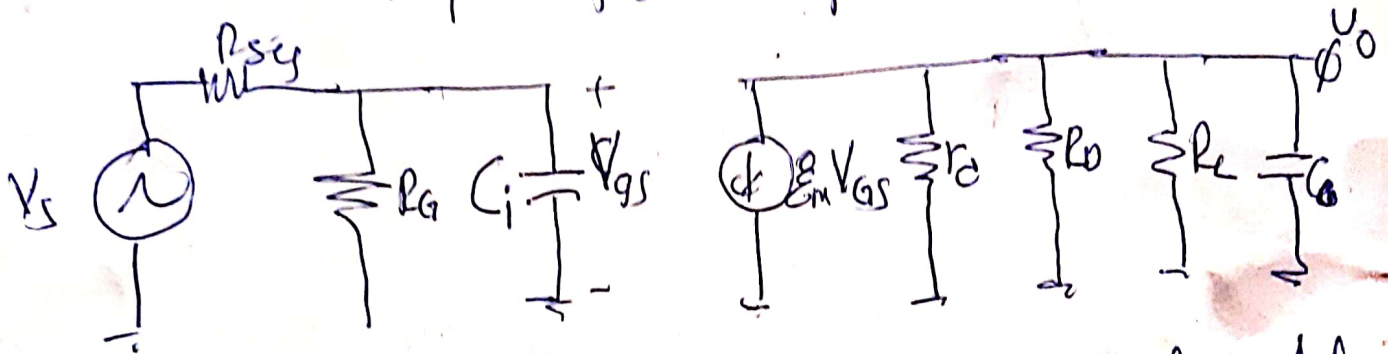


Fig: High frequency ac-Equivalent model

$$f_{H1} = \frac{1}{2\pi R_{TH1} C_i}$$

$$R_{TH1} = R_{sig} \parallel R_G$$

$$C_i = C_{Wi} + C_{gs} + C_{mi}$$

$$= C_{Wi} + C_{gs} + (1 - A_v) C_{gd}$$

$$f_{H0} = \frac{1}{2\pi R_{TH0} C_o}$$

$$R_{TH0} = R_D \parallel R_L \parallel r_d$$

$$C_o = C_{Wo} + C_{ds} + C_{mo}$$

$$= C_{Wo} + C_{ds} + (1 - \frac{1}{A_v}) C_{gd}$$

Ex-2 Determine the high cutoff frequencies of ex-2 using the same parameters

$$C_G = 0.01 \mu F, C_C = 0.5 \mu F, C_S = 2 \mu F$$

$$R_{sig} = 10 k\Omega, R_G = 1 M\Omega, R_D = 4.7 k\Omega, R_S = 1 k\Omega$$

$$R_L = 2.2 k\Omega, I_{DSS} = 8 mA, V_p = -4V, r_d = \infty$$

$$V_{DD} = 20V$$

$$C_{gd} = 2 pF, C_{GS} = 4 pF, C_{DS} = 0.5 pF, C_{wi} = 5 pF$$

$$C_{wo} = 6 pF$$

(b) Sketch the Bode plot

Sol: $R_{TH1} = R_{sig} \parallel R_G = 10 k\Omega \parallel 1 M\Omega = 9.9 k\Omega$

$$A_v = -3$$

$$C_i = C_{wi} + C_{GS} + (1 - A_v) C_{gd}$$

$$= 5 pF + 4 pF + (1 + 3) 2 pF$$

$$= 17 pF$$

$$f_{H1} = \frac{1}{2\pi R_{TH1} C_i} = \frac{1}{2\pi \times 9.9 k\Omega \times 17 pF}$$

$$= 945.67 kHz$$

$$R_{TH2} = R_D \parallel R_L = 4.7 k\Omega \parallel 2.2 k\Omega$$

$$= 1.5 k\Omega$$

$$C_o = C_{wo} + C_{DS} + C_{wo}$$


$$= 6 pF + 0.5 pF + (1 - \frac{1}{-3}) 2 pF$$

$$= 9.17 pF$$

$$f_{H2} = \frac{1}{2\pi (1.5 k\Omega) (9.17 pF)} = 11.57 MHz$$

39

6

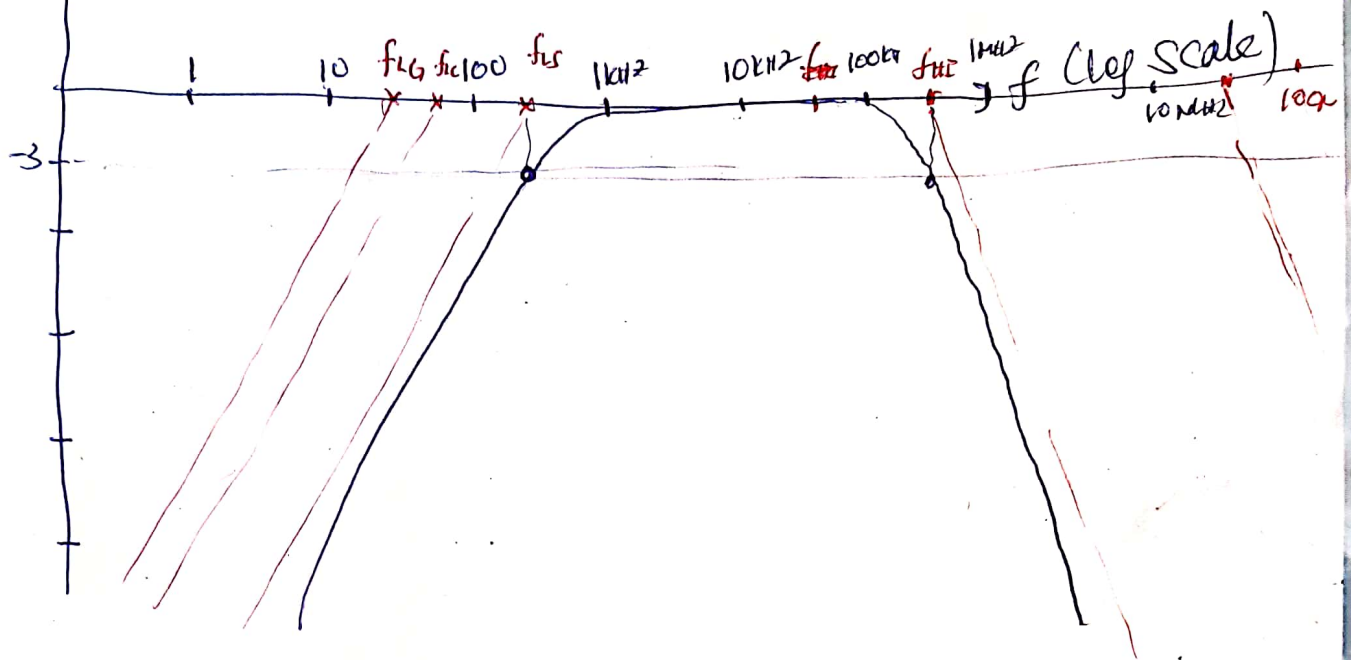

35