



# አዳማ ሳይንስ እና ቴክኖሎጂ ዩኒቨርሲቲ

## Adama Science and Technology University



[www.astu.edu.et](http://www.astu.edu.et)

We are dedicated to innovative knowledge!



# ASTU



## **School of Electrical Engineering and Computing**

**Department of Electrical Power and Control Engineering**

**Fundamentals of Electrical Engineering (EPCE 2101)**

### **Chapter – 5**

### **AC Steady State Analysis**



# Outlines

1

Sinusoids' features

2

Phasors

3

Phasor relationships for circuit elements

4


Impedance and admittance

5

Kirchhoff's laws in the frequency domain



# AC

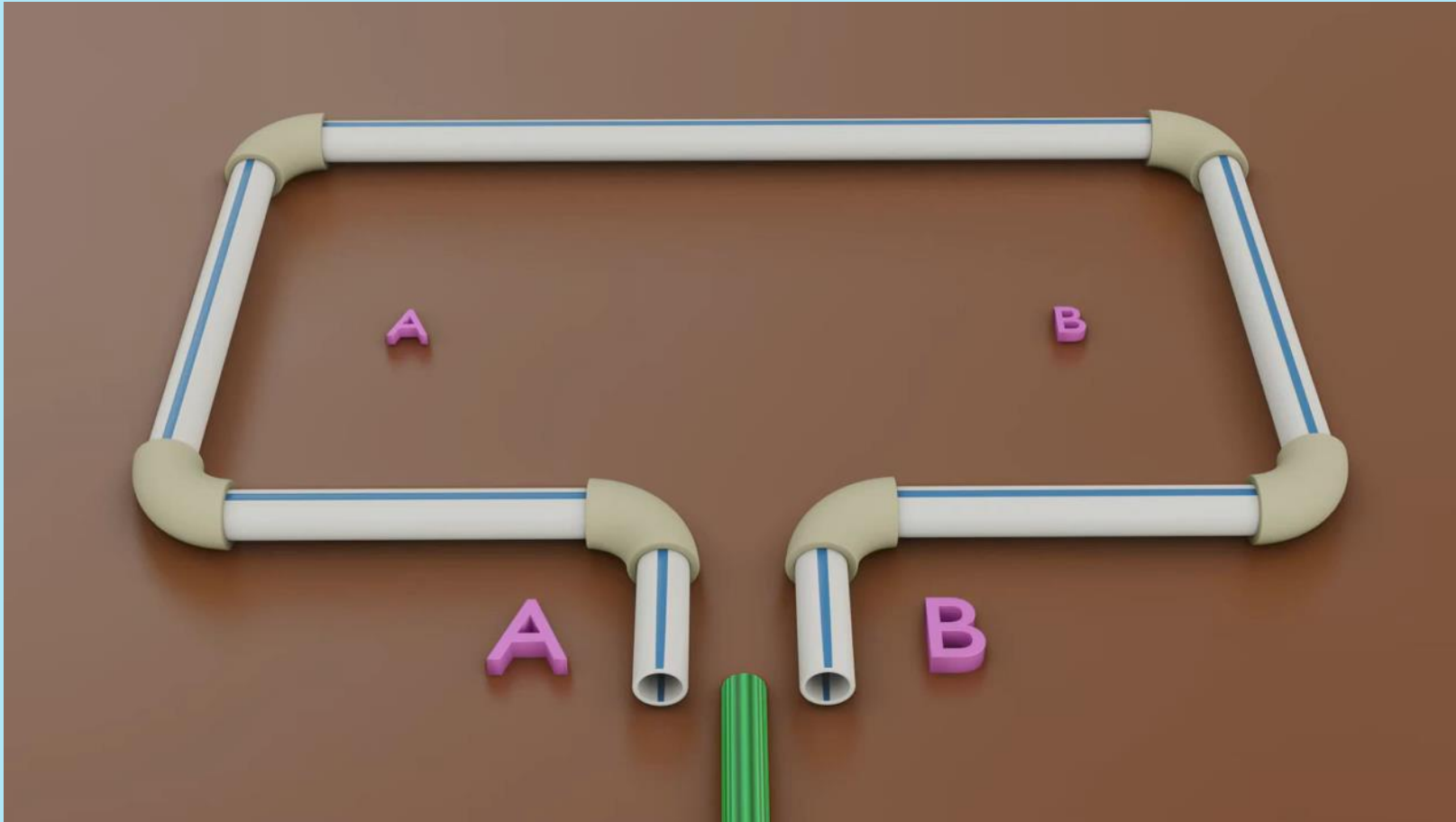



## 5.1 Introduction to Sinusoids

- **A sinusoid** is a signal that has the form of the **sine or cosine function**.
- A sinusoidal current is usually referred to as **ac**.
- Such a current reverses at regular time intervals and has alternately **positive and negative values**.
- **Circuits driven by sinusoidal current or voltage sources are called ac circuits.**



## 5.2. Sinusoidal and complex forcing functions

➤ Sinusoids are easily expressed in *terms of phasors*,

**A phasor is a complex number that** represents the **amplitude** and **phase of a sinusoid**.

➤ **A general expression for the sinusoid,**

$$v(t) = V_m \sin(\omega t + \phi)$$

**Where**

$V_m$  = **Amplitude** of the sinusoid

$\omega$  = **Angular frequency** in radians/s

$\phi$  = **Phase**


$\omega t$  = **Argument of the sinusoid**


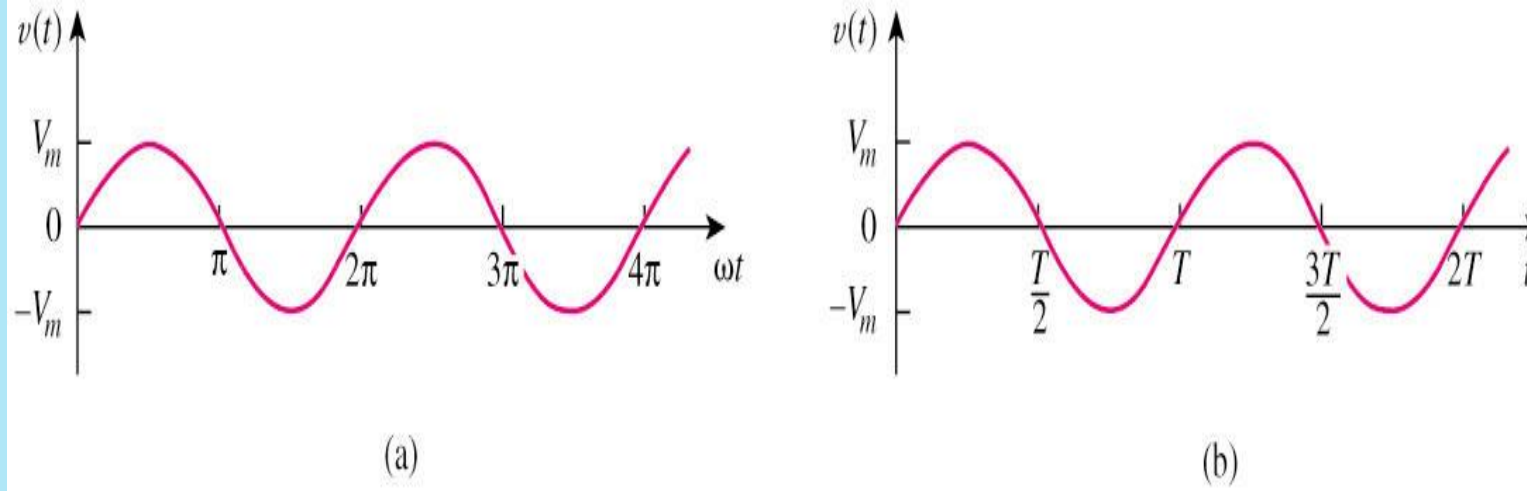
## 5.2. Sinusoidal and complex forcing functions

➤ The sinusoid is shown in


- Fig. 5.1(a) as a **function of its argument** and
- Fig. 5.1(b) as a **function of time**.



A sketch of  $V_m \sin \omega t$ : (a) as a function of  $\omega t$ , (b) as a function of  $t$ .


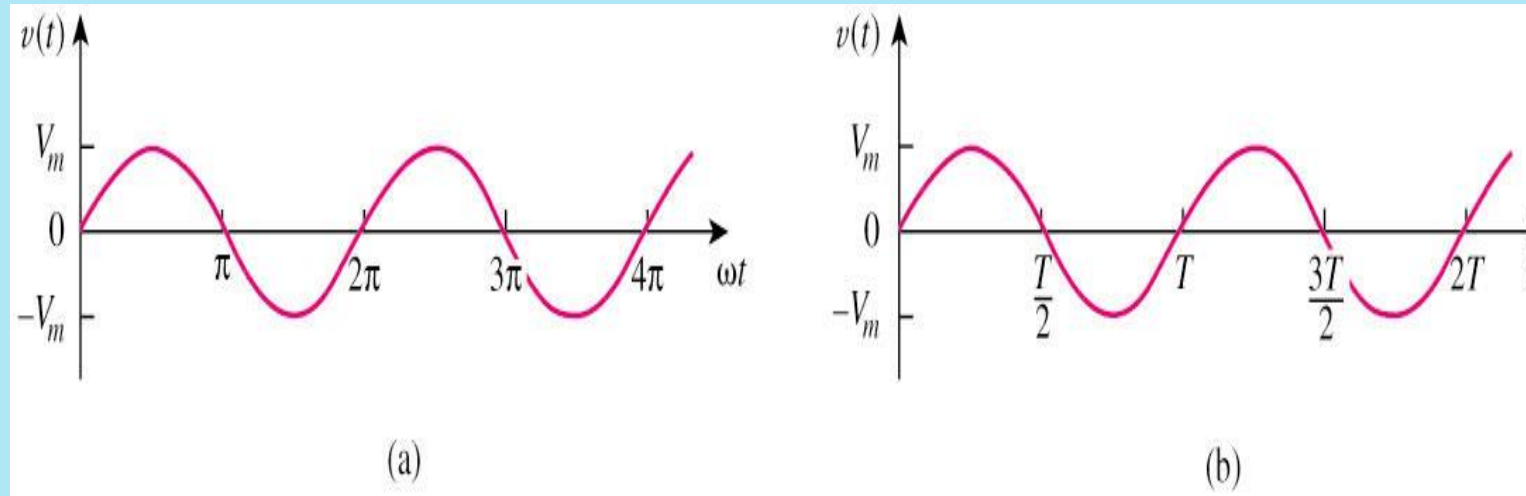
## 5.2. Sinusoidal and complex forcing functions



A sketch of  $V_m \sin \omega t$ : (a) as a function of  $\omega t$ , (b) as a function of  $t$ .

- The sinusoid repeats itself every  $T$  second; thus,  $T$  is called the period of the sinusoid.

$$\omega T = 2\pi,$$



$$T = \frac{2\pi}{\omega}$$

$$\omega = 2\pi f$$



## 5.2. Sinusoidal and complex forcing functions

- A *periodic function* is one that satisfies  $f(t) = f(t + nT)$ , for all  $t$  and for all integers  $n$ .

$$v(t + T) = V_m \sin \omega(t + \frac{2\pi}{\omega}) = V_m \sin \omega(t + \frac{2\pi}{\omega})$$

- The *period*  $T$  of the periodic function is the time of one complete cycle or the number of seconds per cycle.




## 5.2. Sinusoidal and complex forcing functions

$$\omega = 2\pi f$$

$$f = \frac{1}{T} \text{ Hz}$$

$$v_1(t) = V_m \sin \omega t \text{ and } v_2(t) = V_m \sin (\omega t + \phi)$$

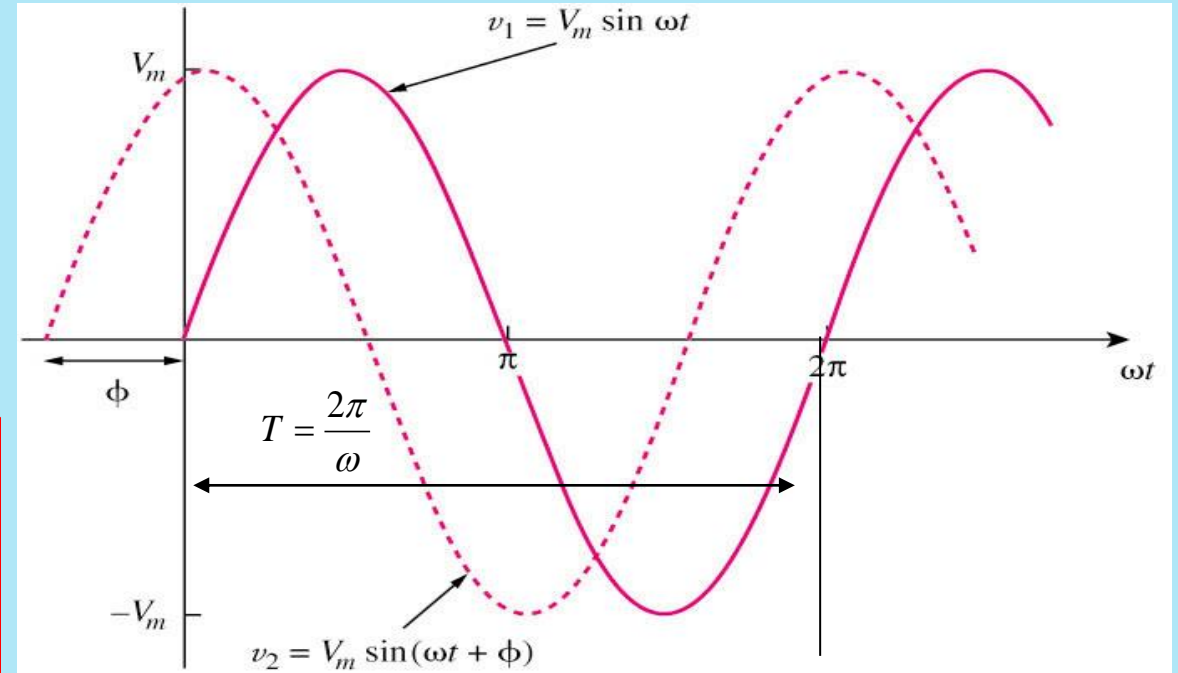- $v_2$  leads  $v_1$  by  $\phi$  or that  $v_1$  lags  $v_2$  by  $\phi$ .
- If  $\phi \neq 0$ , we also say that  $v_1$  and  $v_2$  are out of phase.
- If  $\phi = 0$ , then  $v_1$  and  $v_2$  are said to be in phase.




Two sinusoids with different phases.


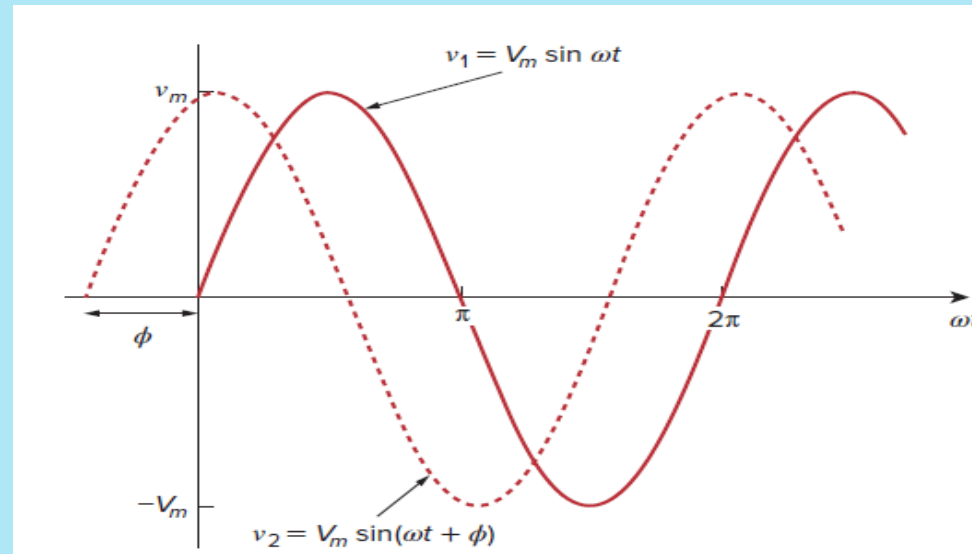
## 5.2. Sinusoidal and complex forcing functions

- Their *minima and maxima at exactly the same time*.
- We can compare  $v_1$  and  $v_2$  in this manner because *they operate at the same frequency; they do not need to have the same amplitude.*



Two sinusoids with different phases.



## 5.2. Sinusoidal and complex forcing functions

- A **sinusoid** can be expressed in either sine or cosine form.
- When **comparing two sinusoids**, it is convenient to express both as either sine or cosine with **positive amplitudes**.

$$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$



## 5.2. Sinusoidal and complex forcing functions

Using these relationships, we can **transform a sinusoid from sine form to cosine form or vice versa.**

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

$$\cos(\omega t - 90^\circ) = \sin \omega t, \quad \sin(\omega t + 180^\circ) = -\sin \omega t$$



## 5.2. Sinusoidal and complex forcing functions

*We can add two sinusoids of the same frequency* when

- One is in sine form and
- The other is in cosine form

To add  **$A \cos \omega t$**  and  **$B \sin \omega t$** , we note that  **$A$  is the magnitude of  $\cos \omega t$**  while  **$B$  is the magnitude of  $\sin \omega t$** ,

$$A \cos \omega t + B \sin \omega t = C \cos(\omega t - \theta)$$

$$C = \sqrt{A^2 + B^2}$$

$$\theta = \tan^{-1} \frac{B}{A}$$




## Example

1. Add  $3 \cos \omega t$  and  $-4 \sin \omega t$  as shown in Fig. and obtain

$$3 \cos \omega t - 4 \sin \omega t = 5 \cos (\omega t + 53.1^\circ)$$

$$C = \sqrt{A^2 + B^2}$$

$$\theta = \tan^{-1} \frac{B}{A}$$

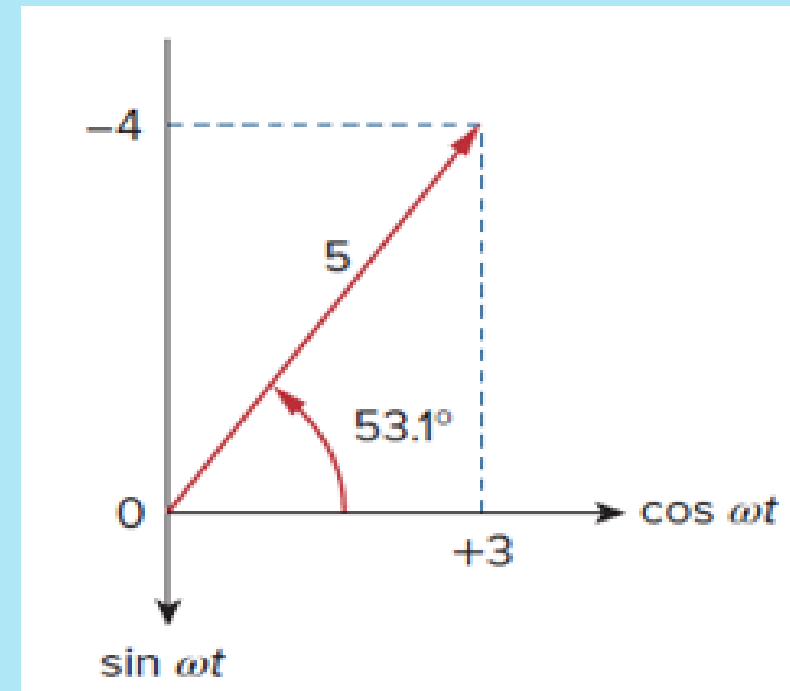



# Example

1. Find the amplitude, phase, period, and frequency of the sinusoid

$$V(t) = 12\cos(50t + 10^\circ) \text{ V.}$$

## Solution:


- ❖ The amplitude is  $V_m = 12 \text{ V}$ .
- ❖ The phase is  $\phi = 10^\circ$ .
- ❖ The angular frequency is  $\omega = 50 \text{ rad/s}$ .
- ❖ The period  $T = \frac{2\pi}{\omega} = \frac{2\pi}{50} = 0.1257 \text{ s}$ .
- ❖ The frequency is  $f = 1/T = 7.958 \text{ Hz}$ .



# Activity

1. Two sources have frequencies  $f_1$  and  $f_2$  respectively.  
If  $f_2 = 2f_1$  and  $T_2$  is 20ms, determine  $f_1$ ,  $f_2$ , and  $T_1$ ?

$$f_2 = \frac{1}{T_2} = \frac{1}{20ms} = 50Hz$$


$$f_1 = \frac{f_2}{2} = \frac{50Hz}{2} = 25Hz$$

$$T_1 = \frac{1}{f_1} = \frac{1}{25Hz} = 40ms$$



# Homework

1. Given the sinusoid  **$45 \cos(5\pi t + 36^\circ)$** , calculate its amplitude, phase, angular frequency, period, and frequency.

## **Solution:**

- ❖ The amplitude is  **$V_m = 45 \text{ V}$** .
- ❖ The phase is  **$\phi = 36^\circ$** .
- ❖ The angular frequency is  **$\omega = 15.708 \text{ rad/s}$** .
- ❖ The period  **$T = \frac{2\pi}{\omega} = \frac{2\pi}{15.708} = 400\text{ms}$** .
- ❖ The frequency is  **$f = 1/T = 2.5\text{Hz}$** .



# Example

1. Calculate the **phase angle between**  $v_1 = -10 \cos(\omega t + 50^\circ)$  and  $v_2 = 12 \sin(\omega t - 10^\circ)$ . State which sinusoid is leading.

**Solution** In order to compare  $v_1$  and  $v_2$ , ***we must express***


- ❑ ***In the same form.***
- ❑ ***In positive amplitudes,***

$$\begin{aligned}
 \cos \omega t &= \sin(\omega t + 90^\circ) \\
 -\cos \omega t &= \sin(\omega t - 90^\circ) \\
 \sin \omega t &= \cos(\omega t - 90^\circ) \\
 -\sin \omega t &= \cos(\omega t + 90^\circ)
 \end{aligned}$$



# Example

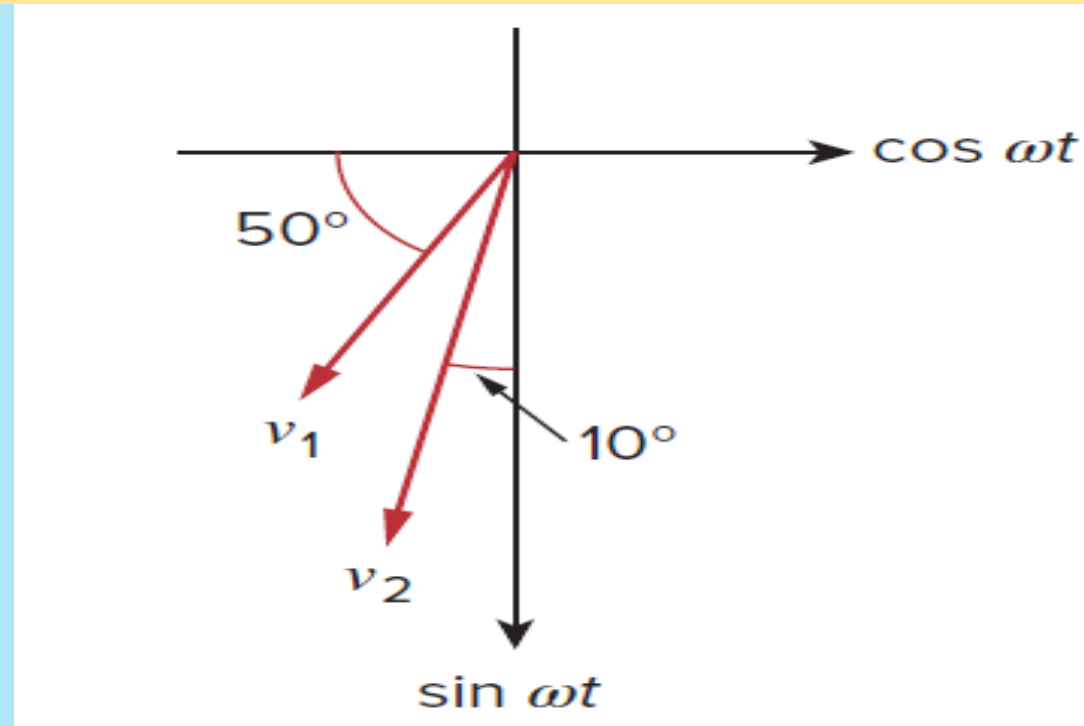***Phase difference between  $v_1$  and  $v_2$  is  $30^\circ$ .***



**$v_2$  leads  $v_1$  by  $30^\circ$**



# Homework

Does  $i_1$  lead or lag  $i_2$ ?

$$i_1 = -4 \sin(377t + 55^\circ) \text{ and } i_2 = 5 \cos(377t - 65^\circ)$$


**$210^\circ$ ,  $i_1$  leads  $i_2$ .**



# AC Phase
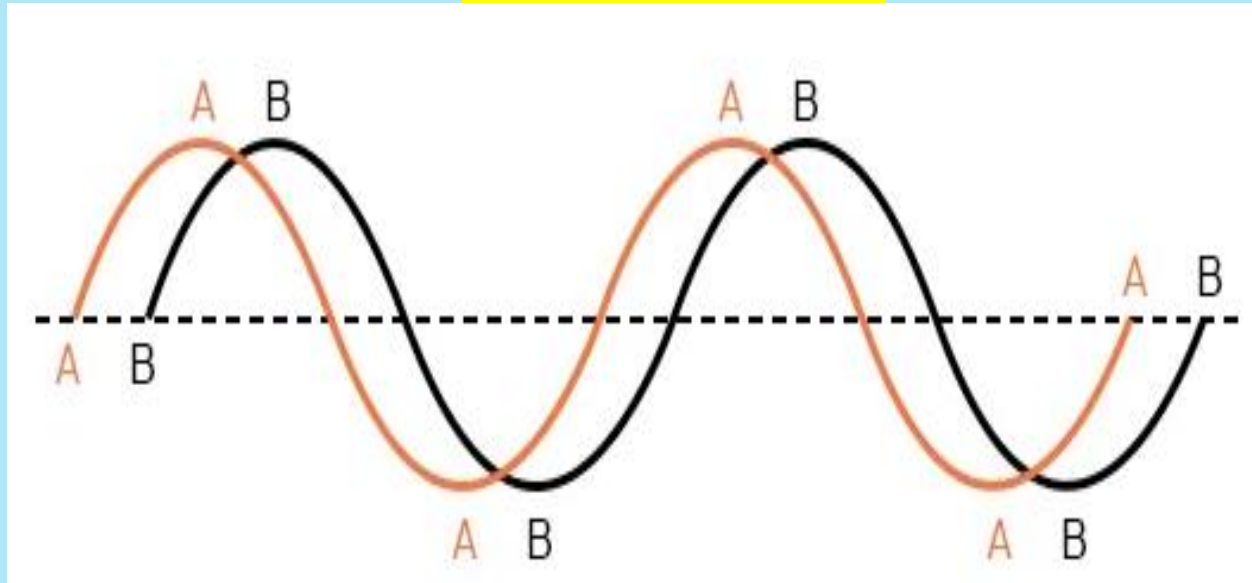
## 1. Out of phase:

- By “out of step,” I mean that the two waveforms are not synchronized.
- Their **peaks and zero points** do not match up at the same points in time



***Out of phase waveforms.***

**We are dedicated to innovative knowledge!**



## Using a graphical approach to relate/compare sinusoids




- We can also **compare sinusoids** that are expressed as **sines and cosines** with a **graphical approach**.
- ❖ **With this method,**
- The **horizontal axis represents the magnitude of cosine** and the **vertical axis represents the magnitude of sine**.



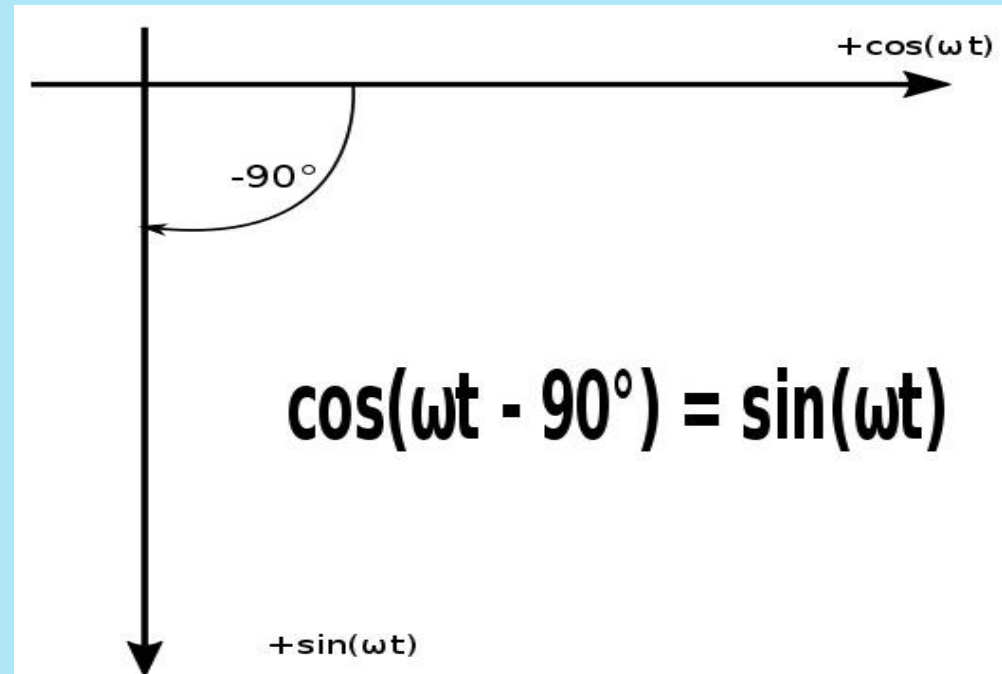
# Using a graphical approach

- The positive direction of sine is denoted as pointing "downwards". **Angles are measured positively in a counter-clockwise** direction from the **horizontal axis**.




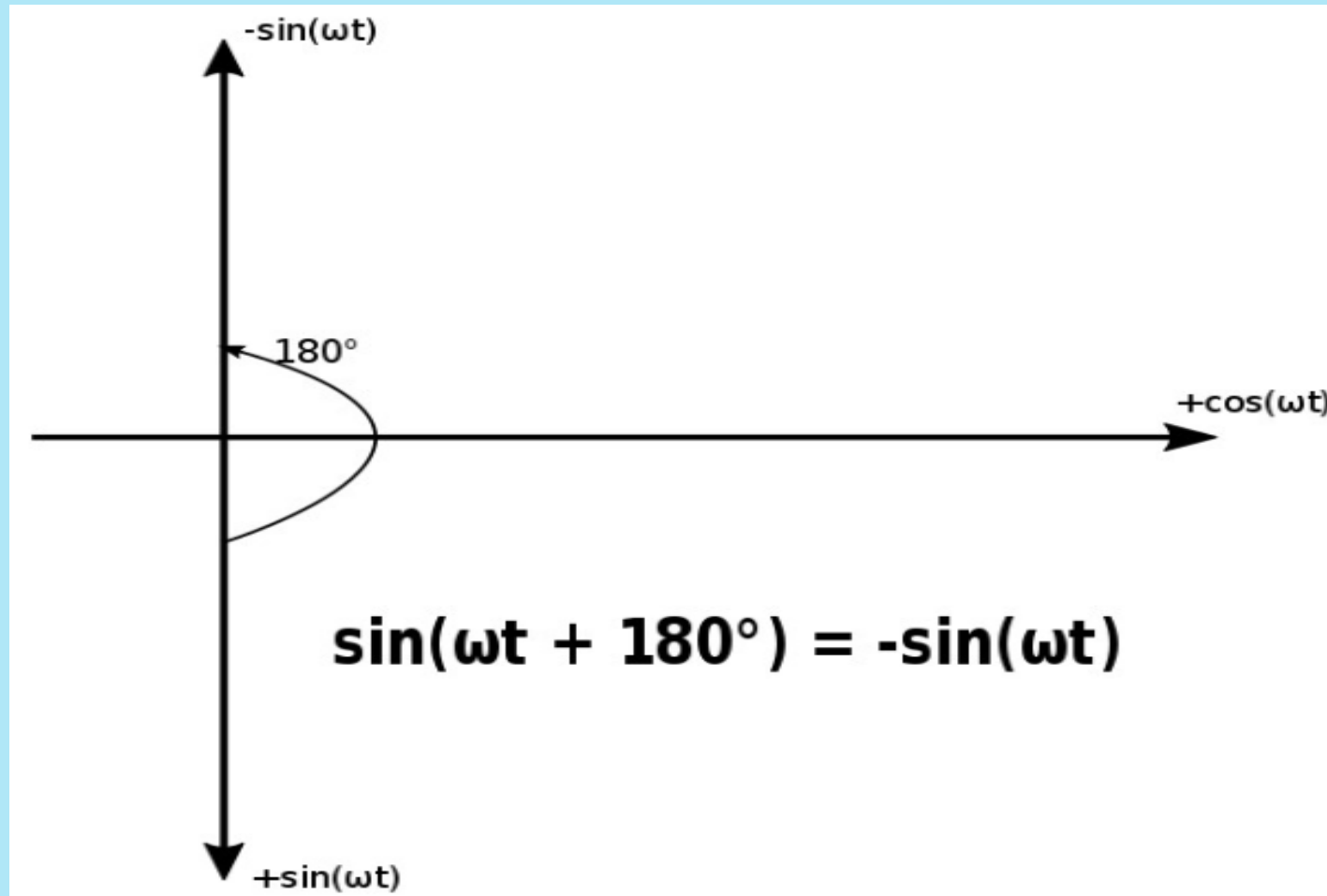
# Another illustration of the graphical approach





# Graphical Method to Add/Subtract Sinusoids of the Same Frequency



- Add the following two sinusoids ( $v_1$  and  $v_2$ ):

$$v_1(t) = A \cos(\omega t)$$

$$v_2(t) = B \sin(\omega t)$$




# Graphical Method to Add/Subtract Sinusoids

- The **magnitude and argument** of the resulting sinusoid can be obtained from the following triangle:

$$v_1(t) = A \cos(\omega t)$$

$$v_2(t) = B \sin(\omega t)$$

$C$  = magnitude of resultant sinusoid

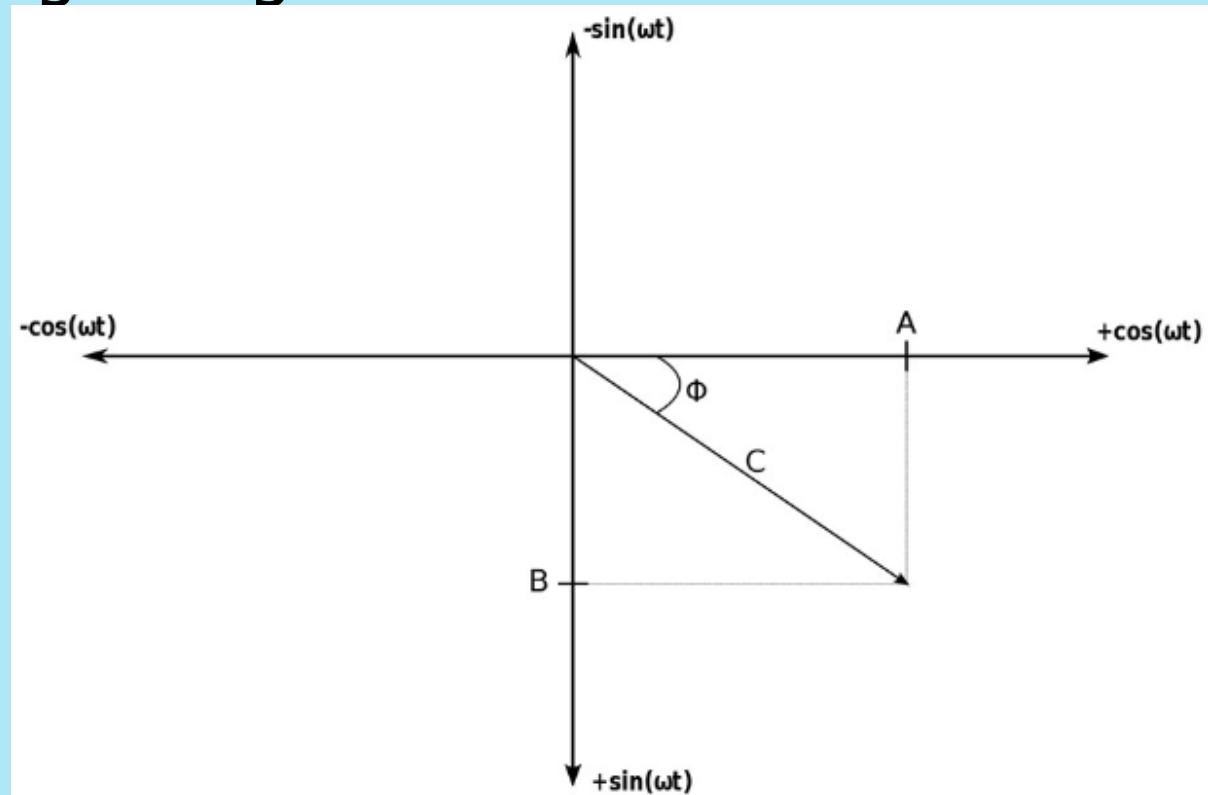



# Graphical Method to Add/Subtract Sinusoids

- The **phase angle** can be determined by the **definition of tangent**

$$\tan(\phi) = \frac{B}{A}$$
$$\phi = \tan^{-1}\left(\frac{B}{A}\right)$$


- For the phase angle, **don't forget** the difference between a reference angle (relative to the horizontal axis) and the actual angle.
- The **sign of A and B** will tell you **what quadrant of the plane the angle lies.**


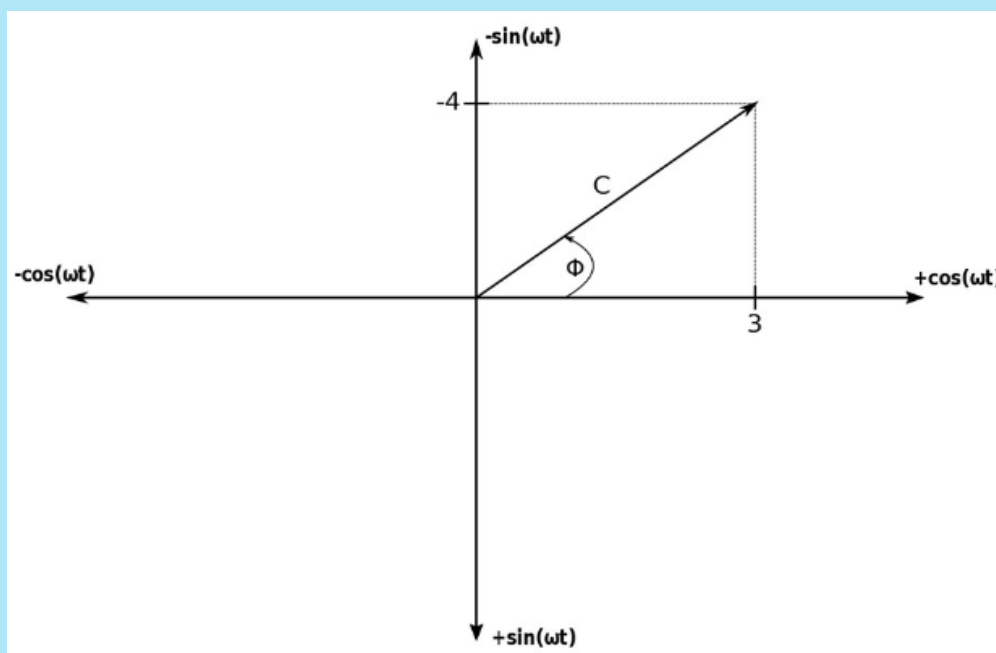
# Sum the following sinusoids

$$3\cos(\omega t) - 4\sin(\omega t)$$

✓ Start by using the graphical approach to plot the sinusoids:





# Phasors (Sinusoid Example Problems)

- Calculate the phase angle between:

$$v_1 = -10\cos(\omega t + 50^\circ)$$

$$v_2 = 12\sin(\omega t - 10^\circ)$$

Using both the method of trig identities and the graphical approach. Determine which sinusoid is leading.



## Method #2 (Graphical Approach)


- plotting  $v_1$  and  $v_2$  on our "improvised" coordinate system:

$$v_1 = -10\cos(\omega t + 50^\circ)$$

$$v_2 = 12\sin(\omega t - 10^\circ)$$

$$\phi = 30^\circ$$

HW

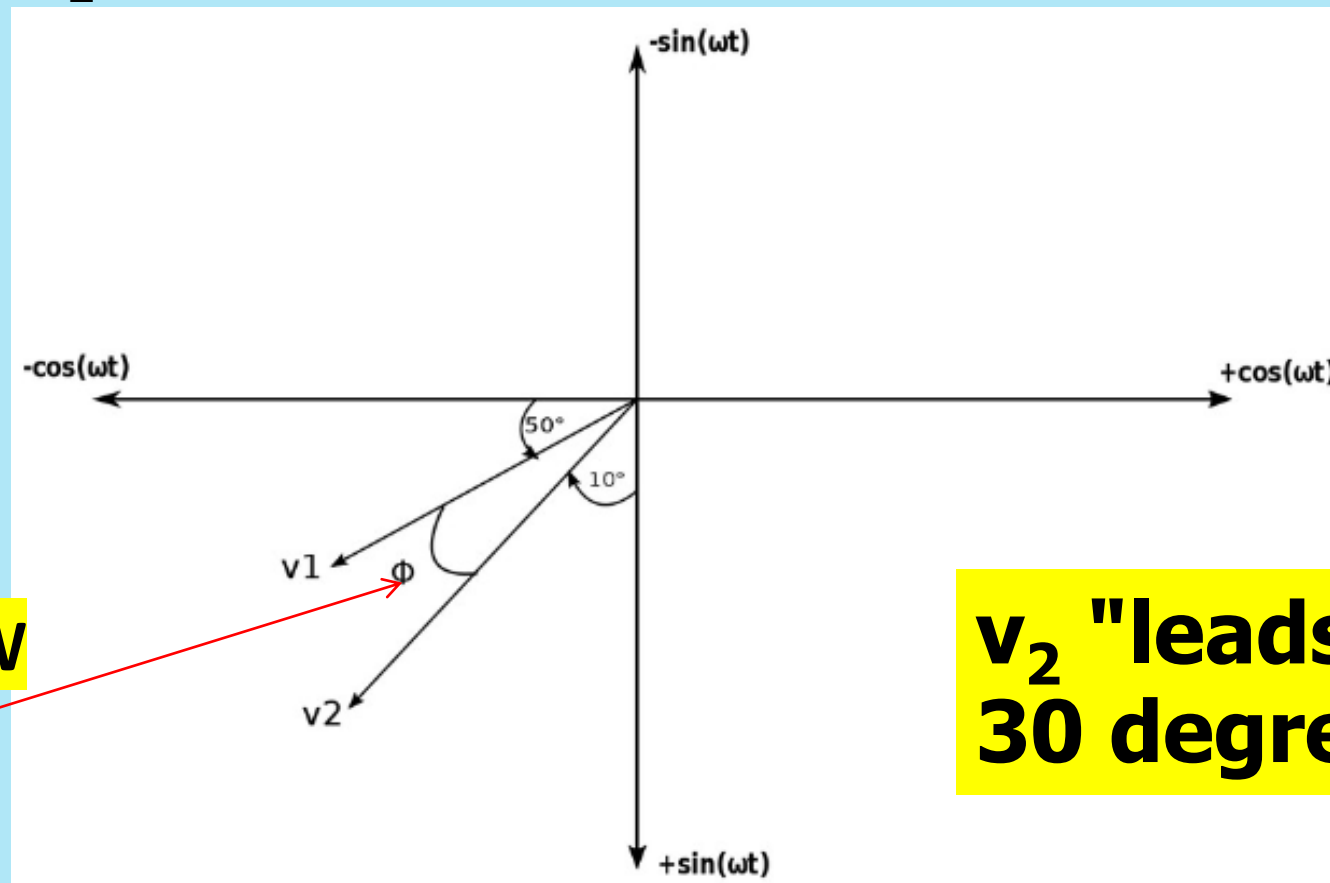

$v_2$  "leads"  $v_1$  by 30 degrees.



# Phasor

- **A phasor** is a complex number that represents the **amplitude** and **phase** of a sinusoid.
- Phasors provide a simple means of analyzing linear circuits excited by sinusoidal sources.



# Phasor

- A complex number  **$\mathbf{Z}$**  can be written in **rectangular form** as

$$\mathbf{z} = \mathbf{x} + j\mathbf{y}$$

Where

- $j = \sqrt{-1}$
- $\mathbf{x}$  is the real part of  $\mathbf{z}$ ;
- $\mathbf{y}$  is the imaginary part of  $\mathbf{z}$ .



# Phasor

- The complex number  $z$  can also be written in polar or exponential form as

$$z = r \angle \phi = re^{j\phi}$$

Where

- $r$  is the magnitude of  $z$ , and
- $\phi$  is the phase of  $z$ .



# Phasor

- **Generally  $\mathbf{Z}$**  can be represented in three ways:

a. Rectangular  $z = x + jy = r(\cos \phi + j \sin \phi)$

b. Polar  $z = r \angle \phi$

c. Exponential  $z = re^{j\phi}$

Where

$$r = \sqrt{x^2 + y^2}$$

$$\phi = \tan^{-1} \frac{y}{x}$$


**$\mathbf{Z}$**  may be written as

$$z = x + jy = r \angle \phi = r(\cos \phi + j \sin \phi)$$


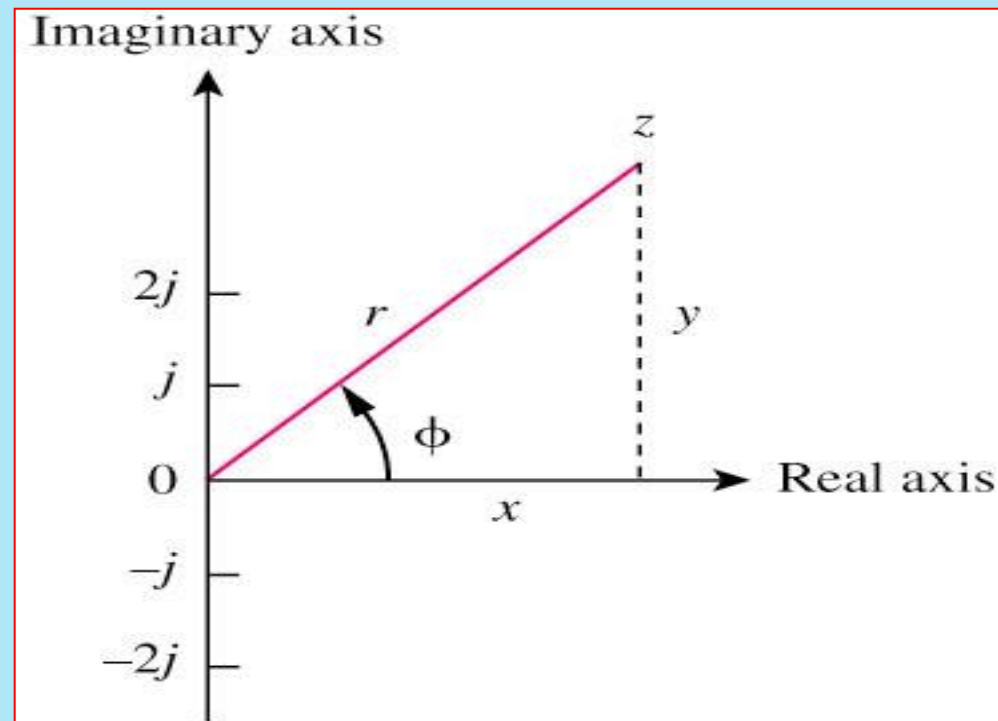
# Phasor

A complex number "z" graphed in the **complex plane** is shown below:



Representation of a complex number  $z = x + jy$



# Converting from rectangular to polar form

- We notice that "r" is the magnitude of the complex number "z".

$$r = \sqrt{x^2 + y^2}$$

- Also, by the definition of the tangent of an angle:

$$\phi = \tan^{-1}\left(\frac{y}{x}\right)$$



# Converting from polar to rectangular form

- Using the definition of sine and cosine of an angle gives us:

$$x = r \cos \phi$$

$$y = r \sin \phi$$

When working with complex numbers, it is useful to keep in mind the basic properties of mathematical operations performed on them:



# Properties of Complex Numbers

Mathematic operation of complex number:

1. Addition

$$z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

2. Subtraction

$$z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

3. Multiplication

$$z_1 z_2 = r_1 r_2 \angle \phi_1 + \phi_2$$

4. Division

$$\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$$

5. Reciprocal

$$\frac{1}{z} = \frac{1}{r} \angle -\phi$$

6. Square root

$$\sqrt{z} = \sqrt{r} \angle \phi/2$$

7. Complex conjugate

$$z^* = x - jy = r \angle -\phi = re^{-j\phi}$$

8. Euler's identity

$$e^{\pm j\phi} = \cos \phi \pm j \sin \phi$$



# Phasor

- Transform a sinusoid to and from the time domain to the phasor domain:

$$v(t) = V_m \cos(\omega t + \phi) \longleftrightarrow V = V_m \angle \phi$$

(Time domain)

(Phasor domain)



## Example Problems Involving Complex Numbers

**Ex1)** Evaluate the following **complex number** and **express the result in polar notation**.

$$(40\angle 50^\circ + 20\angle (-30^\circ))^{\frac{1}{2}}$$

### **Solution**

Converting **to rectangular form**:

$$= \left[ 40\cos 50^\circ + j40\sin 50^\circ + 20\cos(-30^\circ) + j20\sin(-30^\circ) \right]^{\frac{1}{2}}$$



## Example Problems Involving Complex Numbers

❖ Numerically evaluating the trig terms:

$$= [43.03 + j20.64]^{\frac{1}{2}}$$

➤ Recall that to convert to polar form:

$$r = \sqrt{x^2 + y^2}$$

$$\phi = \tan^{-1}\left(\frac{y}{x}\right)$$

Therefore  
we get:



$$= \left[ \sqrt{43.03^2 + 20.64^2} \angle \left( \tan^{-1}\left(\frac{20.64}{43.03}\right) \right) \right]^{\frac{1}{2}}$$

$$= [47.72 \angle 25.63^\circ]^{\frac{1}{2}}$$



## Example Problems Involving Complex Numbers

- Using the rule for complex numbers that involves square roots:

$$= \sqrt{47.72} \angle \left( \frac{25.63}{2} \right)$$

$$= 6.91 \angle 12.82^\circ$$



# Phasor Notation

- Phasor Notation/Representation is based on **Euhler's Identity** which states the following:

$$e^{\pm j\phi} = \cos(\phi) \pm j\sin(\phi)$$

- Notice that **cosine(phi)** and **sine(phi)** are the **real** and **imaginary** parts of the complex number:

$$\cos(\phi) = \text{Re}\{e^{j\phi}\} \quad (\text{eqn 1})$$

$$\sin(\phi) = \text{Im}\{e^{j\phi}\} \quad (\text{eqn 2})$$



# Phasor Notation

- ❑ Either equation 1 or equation 2 can be used to develop a phasor, but
- ❑ **Standard convention** is to use equation #1 (**the cosine term**).

$$\cos(\phi) = \text{Re}\{e^{j\phi}\} \quad (\text{eqn 1})$$

$$\sin(\phi) = \text{Im}\{e^{j\phi}\} \quad (\text{eqn 2})$$



# Developing the phasor notation

- Given the following sinusoid:

$$v(t) = V_m \cos(\omega t + \phi)$$

- By equation #1 we can rewrite this as:

$$v(t) = \text{Re}\{V_m e^{j(\omega t + \phi)}\}$$

and by rules of exponentials:

$$= \text{Re}\{V_m e^{j\omega t} e^{j\phi}\} \quad (\text{Eqn3})$$



# Developing the phasor notation

- Now let us define the following expression:

$$V = V_m e^{j\phi} \quad (\text{expression 4})$$

- and recall the following expression for converting a complex number "z" from exponential form to polar form:

$$z = r e^{j\phi} = r \angle \phi$$

- ...which means that expression #4 can be expanded in the following manner:

$$V = V_m e^{j\phi} = V_m \angle \phi \quad (\text{expression 5})$$



# Developing the phasor notation

- Using expression #5, we can now rewrite equation #3 as the following:

$$v(t) = \text{Re}\{\mathbb{V}e^{j\omega t}\} \quad (\text{expression 6})$$

where the term "sinor" is defined as the following:

$$\mathbb{V}e^{j\omega t} = V_m e^{j(\omega t + \phi)}$$



# Developing the phasor notation

- **To get the phasor that corresponds to a sinusoid:**

1. Express the sinusoid in cosine form so that it can be written as the real part of a complex number.
2. Remove the following time factor:

$$e^{j\omega t}$$

and whatever is left is the phasor.



# Developing the phasor notation

- By suppressing the time factor,  $e^{(j\omega t)}$ , the sinusoid is transformed from the time domain to the phasor domain.

$$v(t) = V_m \cos(\omega t + \phi), (time\ domain)$$

when transformed to the phasor domain is equivalent to


$$\mathbb{V} = V_m \angle \phi, (phasor\ domain)$$


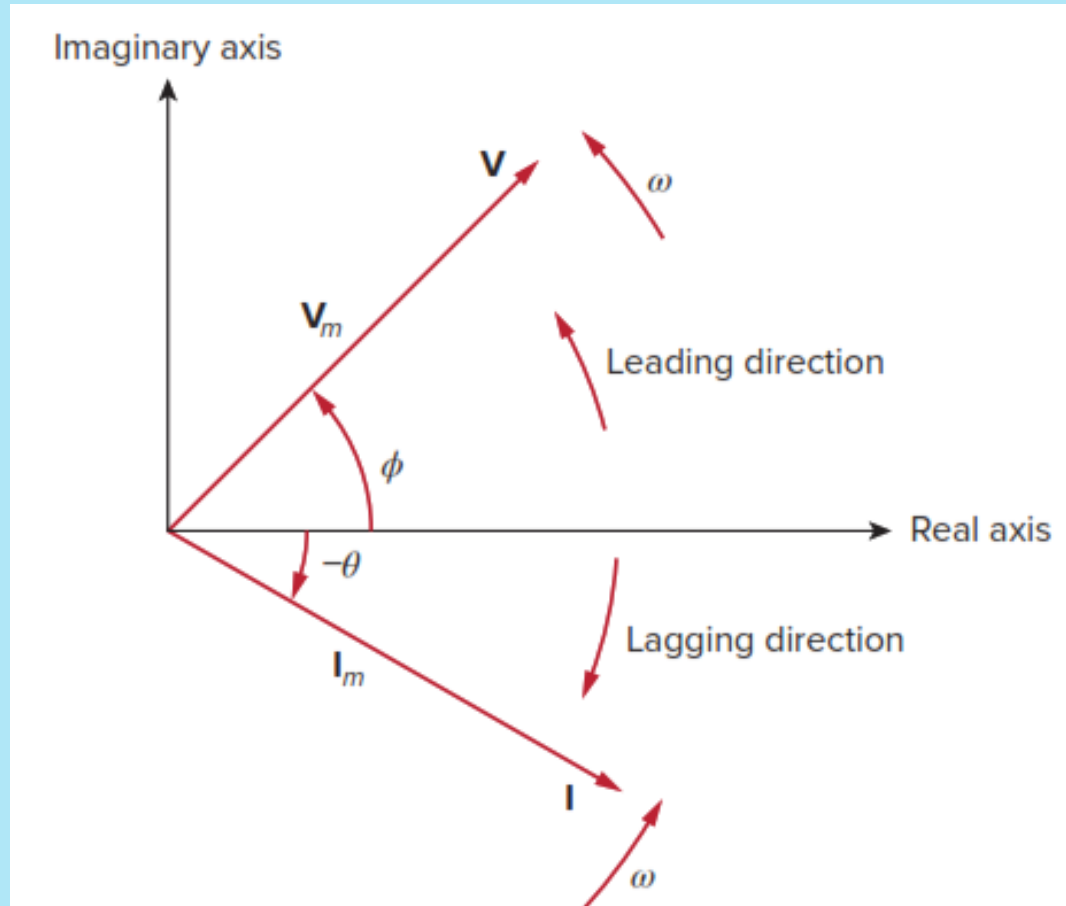
# Phasor

A phasor diagram showing

$$V = V_m \angle \phi$$
$$I = I_m \angle -\theta$$





# Sinusoid-phasor transformation

## Time domain representation

$$V_m \cos(\omega t + \phi)$$

$$V_m \sin(\omega t + \phi)$$

$$I_m \cos(\omega t + \theta)$$

$$I_m \sin(\omega t + \theta)$$

## Phasor domain representation

$$V_m \angle \phi$$

$$V_m \angle \phi - 90^\circ$$

$$I_m \angle \theta$$

$$I_m \angle \theta - 90^\circ$$

The phasor domain is also known as the frequency domain.



# Phasor

- **$v(t)$**  is transformed to the phasor domain  **$j\omega V$**

$$\begin{array}{ccc} \frac{dv}{dt} & \Leftrightarrow & j\omega V \\ \text{(Time domain)} & & \text{(Phasor domain)} \end{array}$$

- The integral of  **$v(t)$**  is transformed to the phasor domain as  **$V/j\omega$**

$$\begin{array}{ccc} \int v dt & \Leftrightarrow & \frac{V}{j\omega} \\ \text{(Time domain)} & & \text{(Phasor domain)} \end{array}$$



# Phasor

The differences between  $\mathbf{v(t)}$  and  $\mathbf{V}$  should be emphasized:

1.  $\mathbf{V(t)}$  is time domain representation, while  $\mathbf{V}$  is the frequency or phasor domain representation.
2.  $\mathbf{V(t)}$  is time dependent, while  $\mathbf{V}$  is not.
3.  $\mathbf{V(t)}$  is always real with no complex term, while  $\mathbf{V}$  is generally complex.



# Example

1. Transform these **sinusoids to phasors**:

(a)  $i = 6 \cos(50t - 40^\circ)$  A

(b)  $v = -4 \sin(30t + 50^\circ)$  V

**Solution:**

(a)  $i = 6 \cos(50t - 40^\circ)$  has the phasor

$$I = 6 \angle -40^\circ \text{ A}$$

(b) Since  $-\sin A = \cos(A + 90^\circ)$ ,

$$\begin{aligned} v &= -4 \sin(30t + 50^\circ) = 4 \cos(30t + 50^\circ + 90^\circ) \\ &= 4 \cos(30t + 140^\circ) \text{ V} \end{aligned}$$

The phasor form of  $v$  is

$$V = 4 \angle 140^\circ \text{ V}$$



# Example

Evaluate these **complex numbers**:

$$(a) (40/\underline{50^\circ} + 20/\underline{-30^\circ})^{1/2}$$

For addition, convert to Rectangular

$$= (25.71 + j30.64 + 17.32 - j10)^{1/2}$$

$$= (43.03 + j20.64)^{1/2}$$

$$= (47.72/\underline{25.63^\circ})^{1/2}$$

$$= (47.72)^{1/2} \underline{\frac{25.63^\circ}{2}}$$

$$= 6.91/\underline{12.81^\circ}$$

$$\sqrt{z} = \sqrt{r} \underline{\phi/2}$$



# Class work

$$(b) \frac{10 \angle -30^\circ + (3 - j4)}{(2 + j4)(3 - j5)^*}$$

Using polar-rectangular transformation, addition, multiplication, and division,

$$(b) \frac{10 \angle -30^\circ + (3 - j4)}{(2 + j4)(3 - j5)^*}$$

For addition, convert to Rectangular

$$\frac{10 \angle -30^\circ + (3 - j4)}{(2 + j4)(3 - j5)^*} = \frac{8.66 - j5 + (3 - j4)}{(2 + j4)(3 - j5)^*} = \frac{11.66 - j9}{(2 + j4)(3 - j5)^*}$$

Taking care of Conjugate

$$= \frac{11.66 - j9}{(2 + j4)(3 + j5)}$$

For multiplication, convert to Polar

$$= \frac{11.66 - j9}{(4.47 \angle 63.43^\circ)(5.83 \angle 59^\circ)} = \frac{14.73 \angle -37.66^\circ}{26.08 \angle 122.47^\circ} = 0.565 \angle -160.13^\circ$$



# Home work

Evaluate the following complex number

$$(a) [(5 + j2)(-1 + j4) - 5\angle 60^\circ]^*$$

$$(b) \frac{10 + j5 + 3\angle 40^\circ}{-3 + j4} + 10\angle 30^\circ + j5$$



# Homework solution

**Solution:**

$$(a) [(5 + j2)(-1 + j4) - 5\angle 60^\circ]^*$$

$$= [(5.385\angle 21.8)(4.123\angle 104) - 5\angle 60] ^*$$

$$= [22.2\angle 125.8 - 5\angle 60] ^*$$

$$= [-12.986 + j18 - (2.5 + j4.33)] ^*$$

$$= [-15.5 + j13.67] ^*$$

$$= [-15.5 - j13.67]$$

$$(b) \frac{10 + j5 + 3\angle 40^\circ}{-3 + j4} + 10\angle 30^\circ + j5$$

$$= \frac{10 + j5 + 2.298 + j1.93}{-3 + j4} + 8.66 + j5 + j5$$

$$= \frac{12.298 + j6.928}{-3 + j4} + 8.66 + j10$$

$$= \frac{14.12\angle 29.39}{5\angle 126.86} + 8.66 + j10$$

$$= 2.83\angle -97.47 + 8.66 + j10$$

$$= 2.83\angle -97.47 + 8.66 + j10$$

$$= -0.367 - j2.799 + 8.66 + j10$$


$$= 8.293 + j7.2$$



# Impedance , Admittance and Phasor diagrams
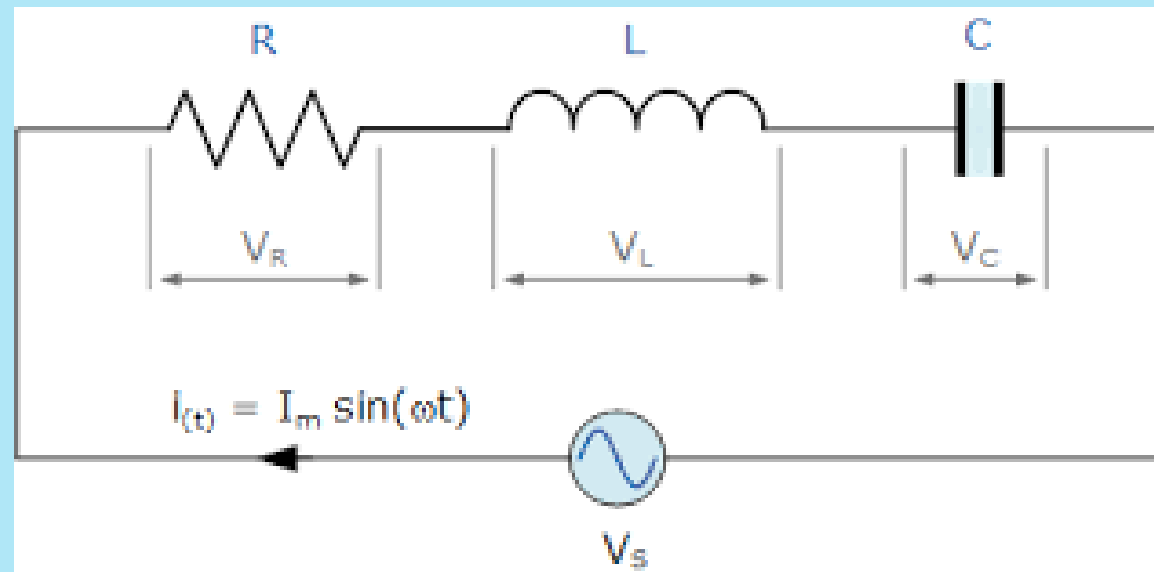
## AC series circuit

- An AC circuit consists of three main components; a resistor, capacitor and an inductor which resist the flow of electric current in their own unique ways.





# Impedance

- Determine how the resistance, capacitance, and inductance **“impede”** the current in ac circuit. Or
- It is the measure of overall opposition of an AC circuit to current denoted by  $Z$
- The symbol for impedance is the letter  $Z$ .
- Unit is the ohm ( $\Omega$ ).
- The **polar form impedance** is written as:
- The magnitude(in ohms) of the impedance is determined as:

$$Z = Z \angle \phi \ (\Omega)$$

$$Z = \sqrt{R^2 + X^2} \ (\Omega)$$

$$\phi = \pm \tan^{-1}\left(\frac{X}{R}\right)$$



# Impedance

- The **rectangular form of impedance** is written as:

$$Z = R \pm jX,$$

Where

- **R is resistance** and **X is reactance** ( $X_L$  or  $X_C$ ).

## Note

**Impedance can be split into two parts:**

**Resistance R** (a part which is constant regardless of frequency)

**Reactance X** (a part that varies with frequency due to capacitance and inductance)




# Impedance

- If we are given the polar form of the impedance, then we may determine the equivalent rectangular expression from as:

$$R = Z \cos \phi \quad \text{and} \quad X = Z \sin \phi$$

Impedance diagram

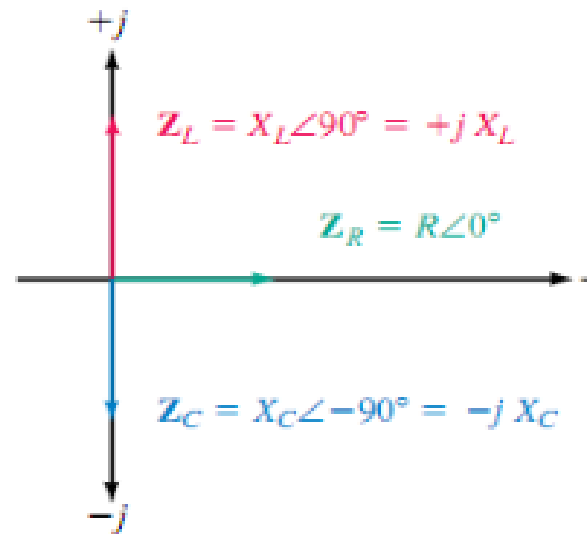




# Impedance

Resistive impedance  $Z_R$  is a vector having a magnitude of  $R$  along the positive real axis;

Inductive impedance  $Z_L$  is a vector having a magnitude of  $X_L$  along the positive imaginary.

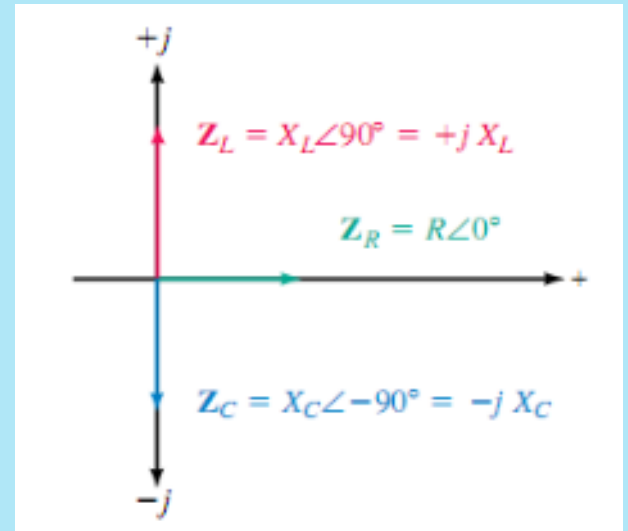capacitive impedance  $Z_C$  is a vector having a magnitude of  $X_C$  along the negative imaginary axis




Mathematically, each of the vector impedance is written as follows

$$\begin{aligned} Z_R &= R \angle 0^\circ = R + j0 = R \\ Z_L &= X_L \angle 90^\circ = 0 + jX_L = jX_L \\ Z_C &= X_C \angle -90^\circ = 0 - jX_C = -jX_C \end{aligned}$$


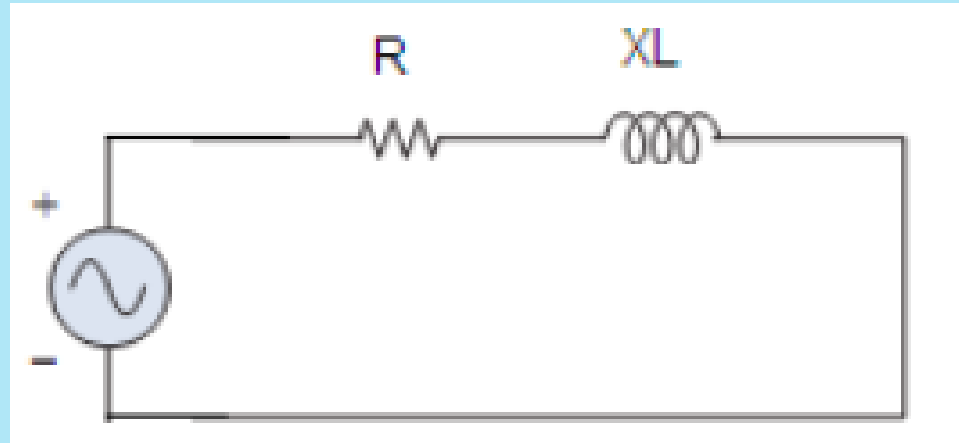
# R-L Circuit

- **R-L circuit is the combination of resistive and inductive load.**




R- L circuit


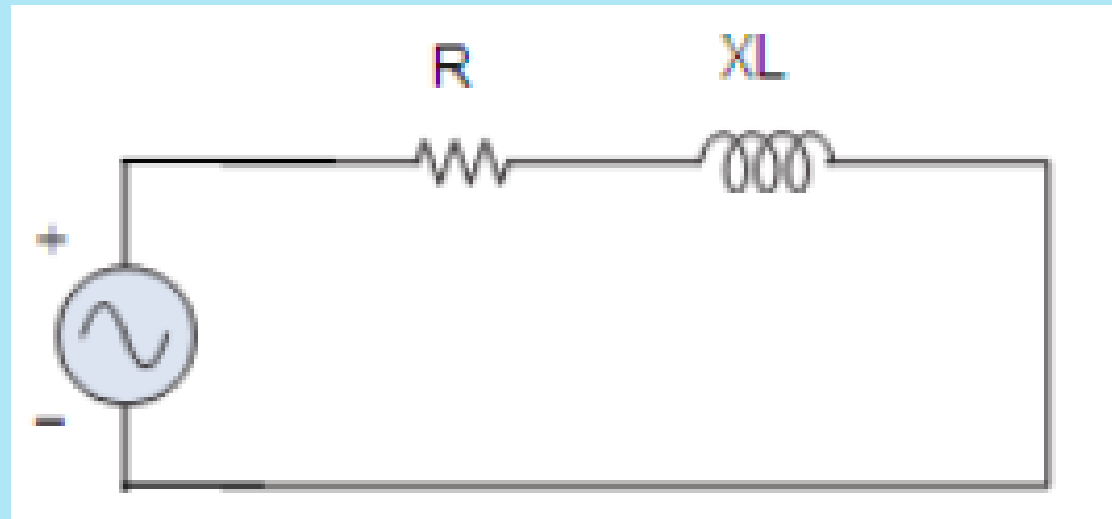
# R-L Circuit


- In R-L circuit the **total impedance Z** is




$$Z = R + jX_L \text{ or } Z = Z < \tan^{-1}\left(\frac{X_L}{R}\right)$$



# R-L Circuit

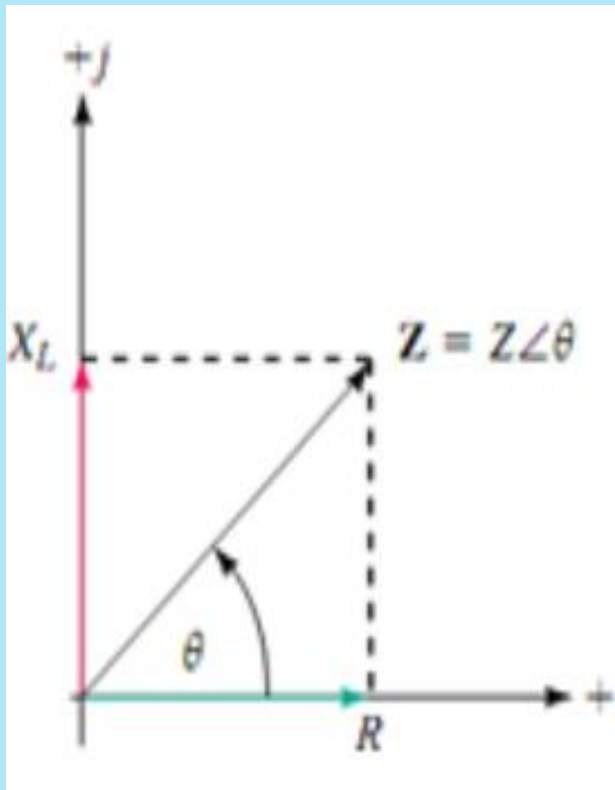

Impedance diagram

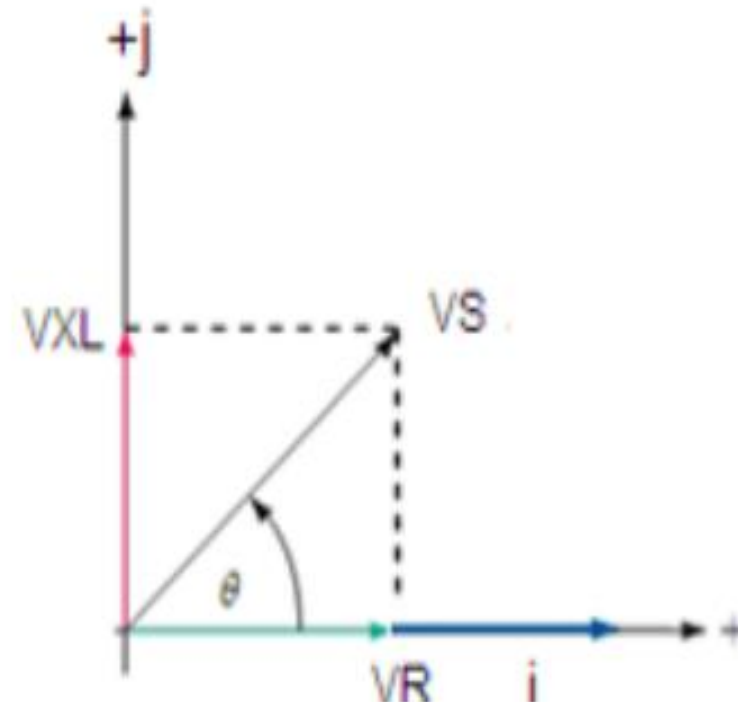

Phasor diagram



# R-L Circuit

- Voltage across resistor(R) and inductor (L) can be determined as

$$V_R = i * Z_R$$

$$V_L = i * Z_L = i * X_L$$

- The total voltage (supply voltage,  $V_s$ )

$$V_s = V_R + jV_L$$

- The total circuit current (i):

$$i = \frac{V_s}{Z} = \frac{V_R + jV_L}{R + jX_L} \text{ or } i = \frac{V_s \angle \phi_1}{Z \angle \phi_2} = \frac{V_s}{Z} \angle \phi_1 - \phi_2$$



# Example

A  **$4\Omega$**  resistor and a  **$9.55\text{mH}$**  inductor are connected in **series** with  **$240\text{ V}$ ,  $50\text{ Hz}$**  AC source.

**Calculate**

- a) Inductive reactance
- b) The impedance,
- c) The total current, and
- d) Draw impedance and phasor diagram.




# Example

## • Solution


- inductive reactance,  $X_L = 2\pi fL = 2\pi(50)(9.55 * 10^{-3}) = 3\Omega$
- impedance,  $Z = \sqrt{R^2 + X_L^2} = \sqrt{4^2 + 3^2} = 5\Omega$
- current,  $i = \frac{v}{z} = \frac{240V}{5\Omega} = 48A$
- $\phi = \tan^{-1} \frac{X_L}{R} = \tan^{-1} \frac{3}{4} = 36.87^\circ$  lagging

$$V_R = i * R = 48 * 4 = 192 < 0 V$$
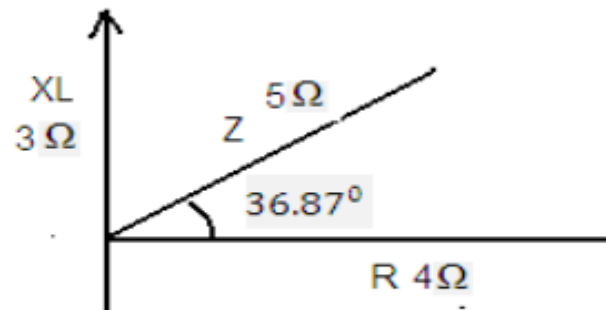
$$V_L = i * X_L = 48 * 3 = 144V \text{ but } V_L = 144 < 90^\circ V$$



Impedance diagram

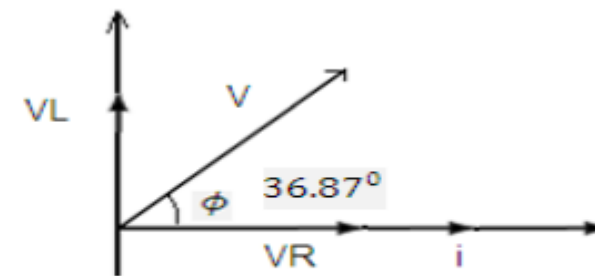

Phasor diagram

current lags voltage  
by 36.87




# R-C Circuit

- An RC series circuit is an electrical circuit consisting of a resistor **R** and a capacitor **C** connected in series, driven by a voltage source or current source.

➤ In RC circuit the total impedance  $Z$  is written as:

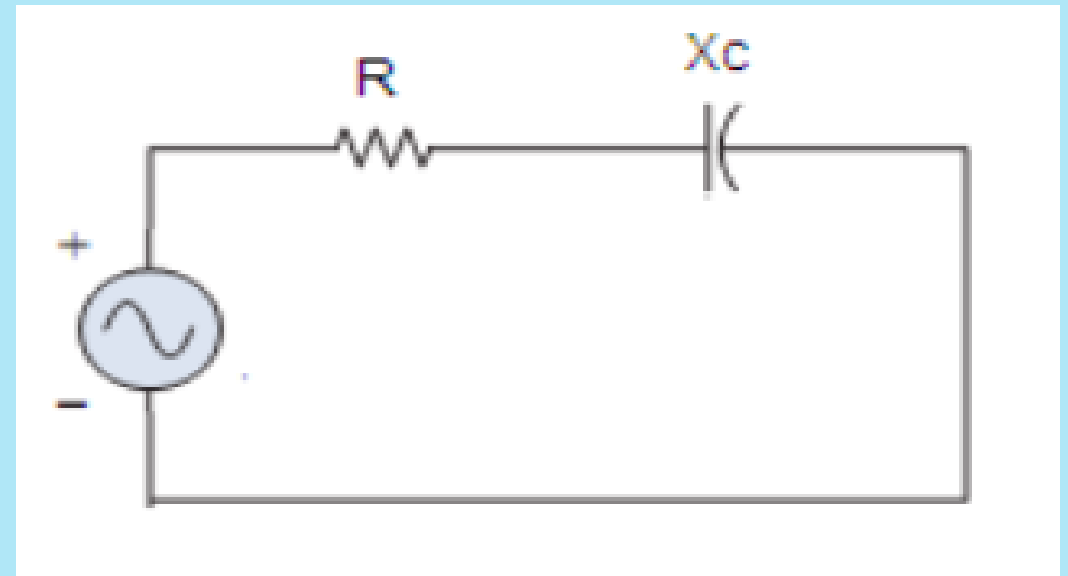
$$Z = R - jX_C \quad \text{or} \quad Z = Z < \tan^{-1}\left(\frac{X_C}{R}\right)$$



RC circuit



# OR Impedance of the RC series circuit

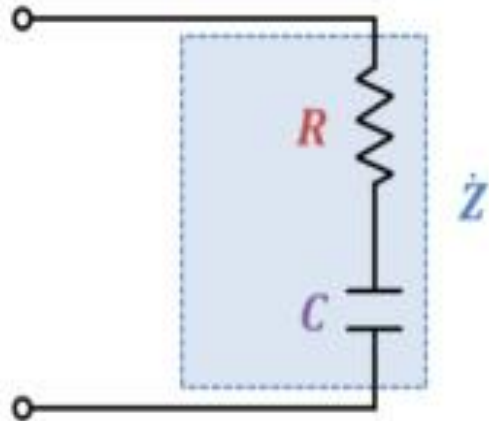

Impedance  $\dot{Z}$

$$\dot{Z} = \underline{R} + \frac{1}{j\omega C} = R - j\frac{1}{\omega C}$$

Impedance of the resistor  $R$

$$\dot{Z}_R = R$$

Impedance of the capacitor  $C$

$$\dot{Z}_C = \frac{1}{j\omega C}$$




# Impedance of the RC series circuit

The impedance  $Z$  of the RC series circuit is the **sum of the respective impedance**, and is as follow:

$$\begin{aligned}\dot{Z} &= \dot{Z}_R + \dot{Z}_C \\ &= R + \frac{1}{j\omega C} \\ &= R - j\frac{1}{\omega C}\end{aligned}$$


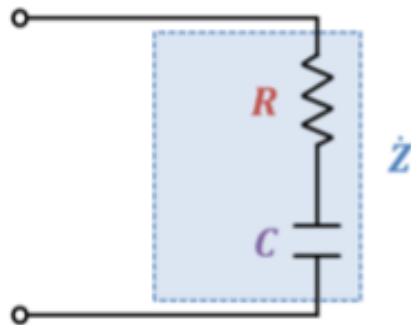
# Magnitude of the impedance of the RC series circuit



Magnitude  $Z$  of the impedance  $\dot{Z}$

$$Z = |\dot{Z}| = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}$$

$$\dot{Z} = R - j \frac{1}{\omega C}$$

Adding the square of the real part  $R$  and the square of the imaginary part  $\frac{1}{\omega C}$  and taking the square root



# Vector diagram of the RC series circuit

The vector diagram of the impedance  $Z$  of the RC series circuit can be drawn in the following steps.

1. Draw a vector of impedance  $Z_R$  of resistor R
2. Draw a vector of impedance  $Z_C$  of capacitor C
3. Combine the vectors




## Draw a vector of impedance $\dot{Z}_R$ of resistor R


The impedance  $\dot{Z}_R$  of the resistor R is expressed as " $\dot{Z}_R = R$ ".

Therefore, the vector direction of the impedance  $\dot{Z}_R$  is the direction of the real axis.

The magnitude (length)  $Z_R$  of the vector of the impedance  $\dot{Z}_R$  is " $Z_R = |\dot{Z}_R| = R$ ".

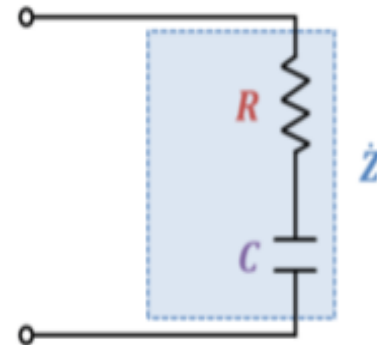
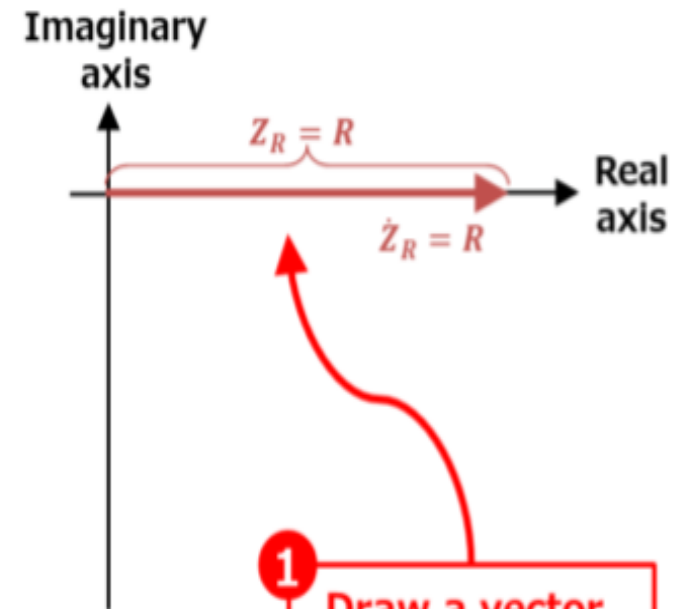
### Vector diagram of the impedance $\dot{Z}$






## Draw a vector of impedance $\dot{Z}_C$ of capacitor C

The impedance  $\dot{Z}_C$  of the capacitor C is expressed as " $\dot{Z}_C = -j * 1 / \omega C$ ".

Therefore, the orientation of the impedance  $\dot{Z}_C$  vector is **90° clockwise** around the real axis (with "-j", it rotates 90° clockwise).

The magnitude (length)  $Z_C$  of the vector of the impedance  $\dot{Z}_C$  is " $Z_C = |\dot{Z}_C| = 1 / \omega C$ ".

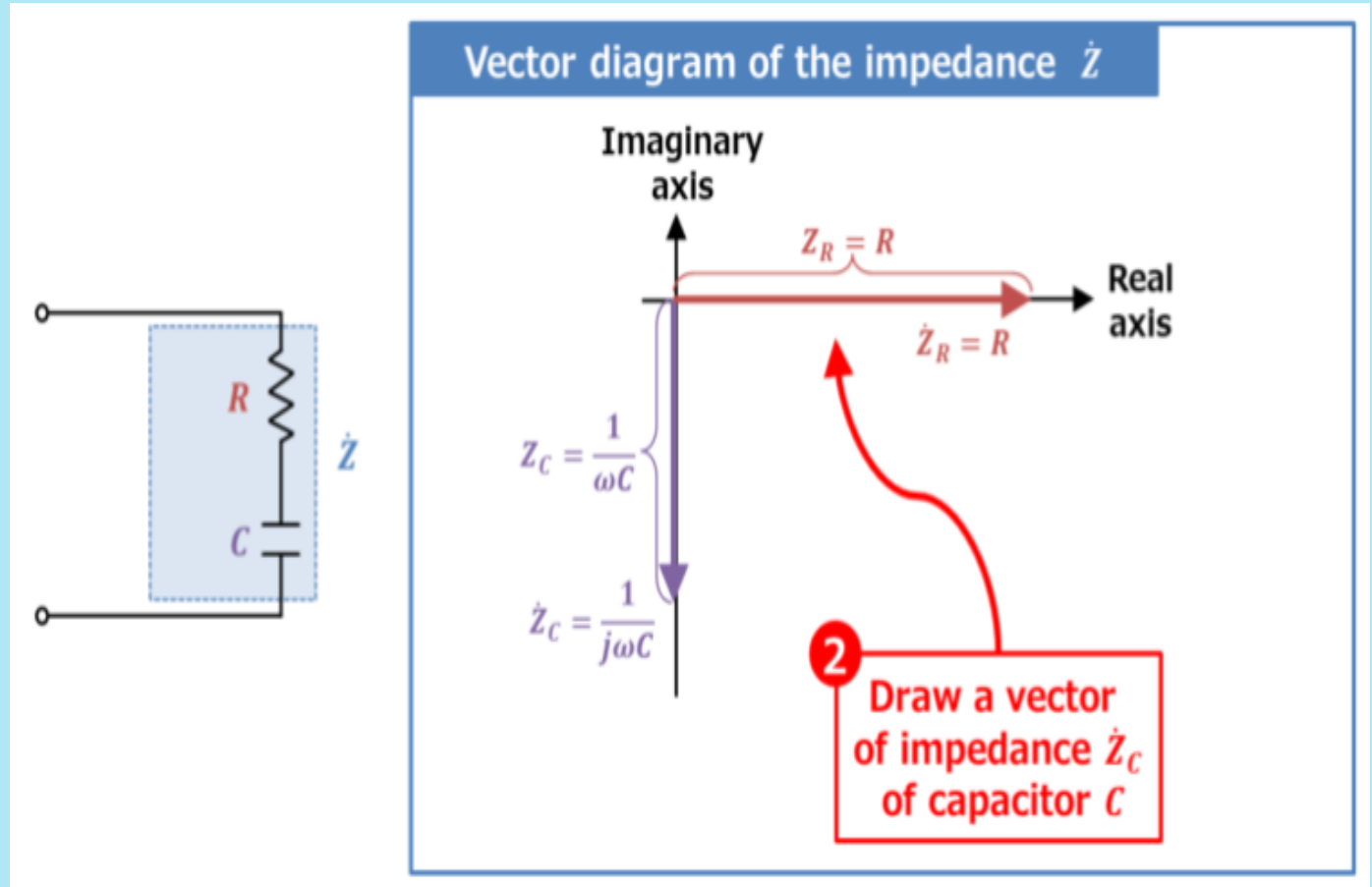




# Combine the vectors

Combining the vector of "impedance  $\dot{Z}_R$  of resistor  $R$ " and "impedance  $\dot{Z}_C$  of capacitor  $C$ " is the vector diagram of the impedance  $\dot{Z}$  of the RC series circuit.

The magnitude (length)  $Z$  of the vector of the impedance  $\dot{Z}$  is

$$|Z| = |\dot{Z}| = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}$$

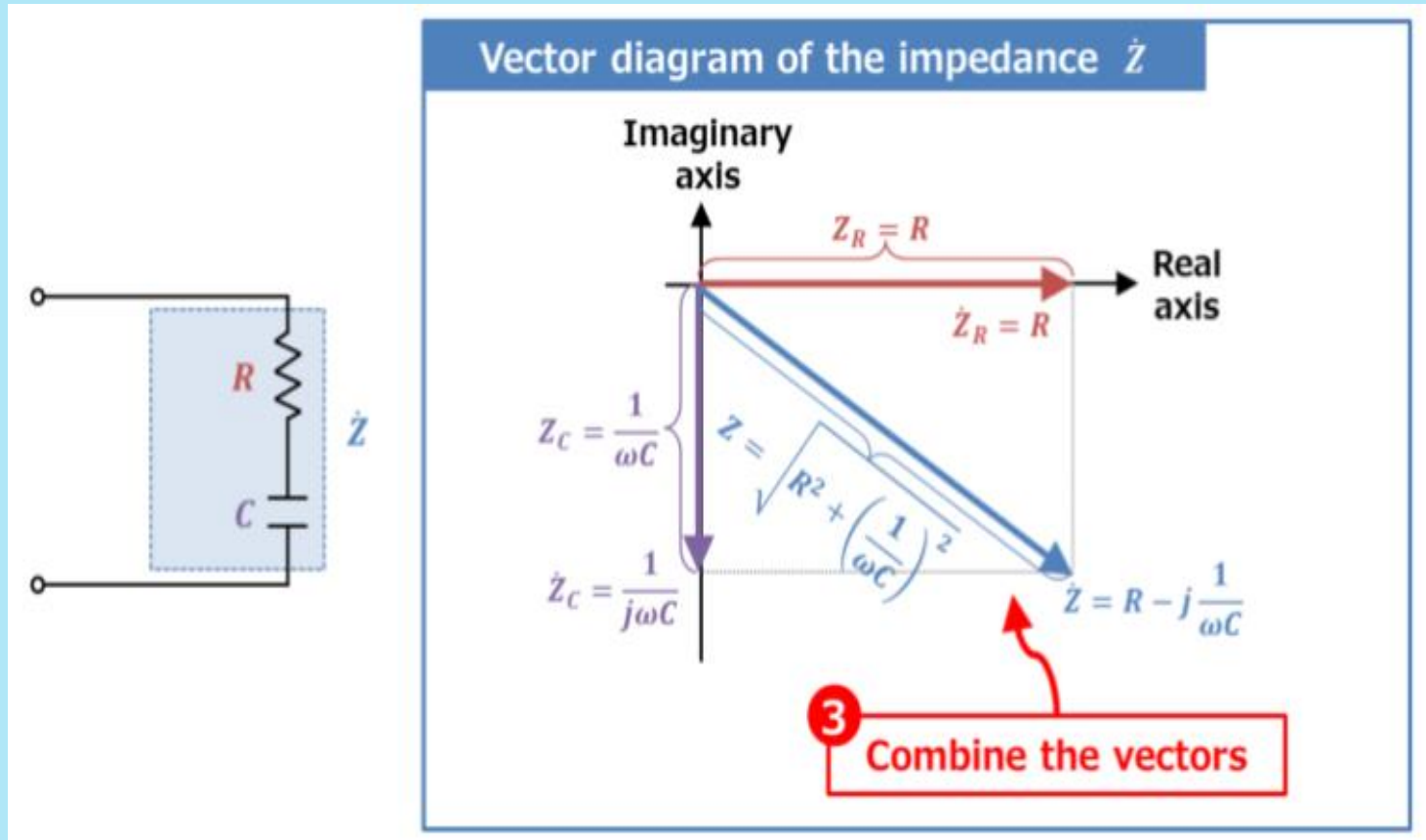




# Vector orientation

With " $+j$ " is attached

☑ The vector rotates **90° counterclockwise**.

With " $-j$ " is attached

☑ The vector rotates **90° clockwise**.

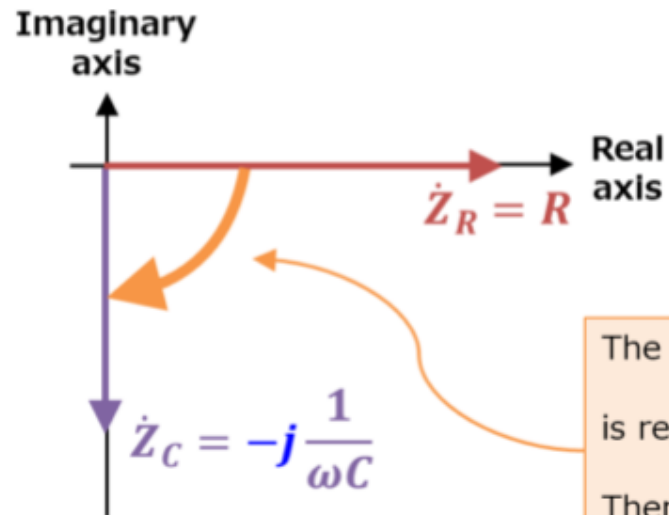

The impedance  $\dot{Z}_C$  of capacitor  $C$

is represented by " $\dot{Z}_C = -j \frac{1}{\omega C}$ ".

Therefore, the direction of vector  $\dot{Z}_C$  is **90° clockwise** around the real axis.



# Vector orientation

When an imaginary unit "j" is added to the expression, the direction of the vector is rotated by  $90^\circ$ .

✓ **With "+j" is attached**

- The vector rotates  **$90^\circ$  counterclockwise**.


✓ **With "-j" is attached**

- The vector rotates  **$90^\circ$  clockwise**.


The impedance  $\dot{Z}_C$  of capacitor  $C$  is represented by " $\dot{Z}_C = -j\frac{1}{\omega C}$ ". Therefore, the direction of vector  $\dot{Z}_C$  is  **$90^\circ$  clockwise** around the real axis.


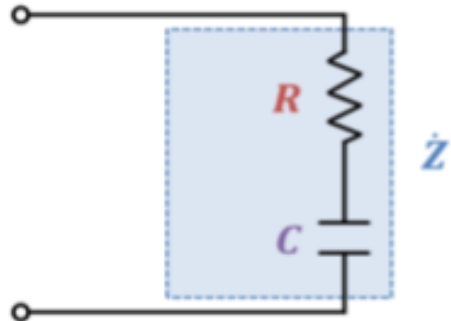
# Impedance **phase angle** of the RC series circuit


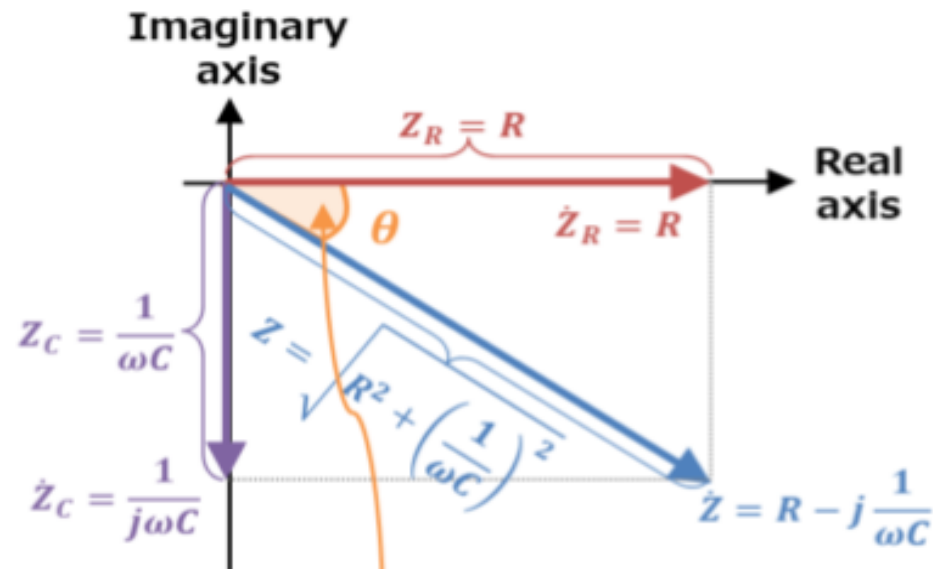
## Impedance phase angle of the impedance $\dot{Z}$



$$\theta = \tan^{-1} \left( -\frac{1}{\omega CR} \right)$$

$$\tan \theta = \frac{-\frac{1}{\omega C}}{R}$$

$$\Leftrightarrow \theta = \tan^{-1} \left( -\frac{1}{\omega CR} \right)$$



# Example

A resistor of  $25\Omega$  is connected in series with a capacitor of  $45\mu\text{F}$ .

calculate

- (a) The impedance,
- (b) The current taken from a 240,50Hz supply.
- (c) Find also the phase angle between the supply voltage and the current.



# Example

## Solution

- Capacitive reactance,  $X_c = \frac{1}{2\pi fC} = \frac{1}{2\pi(50)(45 \times 10^{-6})} = 70.74 \Omega$
- Impedance  $Z = \sqrt{R^2 + X_c^2} = \sqrt{25^2 + 70.74^2} = 75.03\Omega$
- Current,  $i = \frac{V}{Z} = \frac{240V}{75.03\Omega} = 3.2A$


Phase angle between the supply voltage and current

$$\phi = \tan^{-1} \frac{X_c}{R} = \frac{70.74}{25}$$



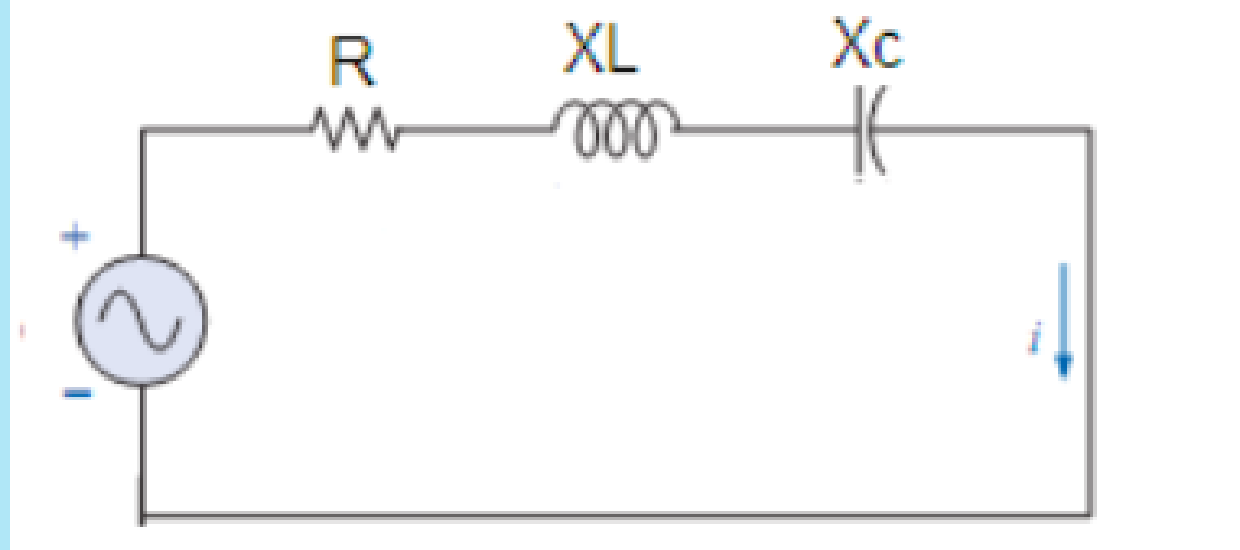
# Series RLC circuit

- An RLC circuit is an electrical circuit consisting of a resistor (R), an inductor (L), and a capacitor (C), connected in series or in parallel.



RLC circuit

# Impedance of the RLC series circuit

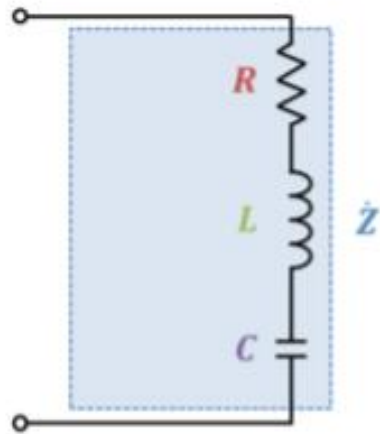

Impedance  $\dot{Z}$

$$\dot{Z} = R + j(\underbrace{X_L}_{\text{Reactance of the inductor } L} - \underbrace{X_C}_{\text{Reactance of the capacitor } C}) = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

Reactance of the inductor  $L$

$$X_L = \omega L$$

Reactance of the capacitor  $C$

$$X_C = \frac{1}{\omega C}$$

The impedance  $\dot{Z}$  can be divided into the following three cases.

$$X_L > X_C$$

$$\dot{Z} > 0$$

$\dot{Z}$  is inductive.

$$X_L < X_C$$

$$\dot{Z} < 0$$

$\dot{Z}$  is capacitive.

$$X_L = X_C$$

$$\dot{Z} = 0$$



# Impedance of the RLC series circuit

The impedance  $Z_R$  of the resistor  $R$ , the impedance  $Z_L$  of the inductor  $L$ , and the impedance  $Z_C$  of the capacitor  $C$  can be expressed by the following equations:

$$\dot{Z}_R = R$$

$$\dot{Z}_L = jX_L = j\omega L$$

$$\dot{Z}_C = -jX_C = -j\frac{1}{\omega C} = \frac{1}{j\omega C}$$

Where

- $\omega$  is the angular frequency, which is equal to  $2\pi f$ , and
- $X_L (= \omega L)$  is called inductive reactance, which is the resistive component of inductor  $L$  and
- $X_C (= 1/\omega C)$  is called capacitive reactance, which is the resistive component of capacitor  $C$ .



# Impedance of the RLC series circuit

The impedance  $Z$  of the RLC series circuit is the sum of the respective impedance, and is as follow:

$$\begin{aligned}\dot{Z} &= \dot{Z}_R + \dot{Z}_L + \dot{Z}_C \\ &= R + jX_L - jX_C \\ &= R + j(X_L - X_C) \\ &= R + j\left(\omega L - \frac{1}{\omega C}\right)\end{aligned}$$



# Impedance of the RLC series circuit

The impedance  $Z$  can be divided into the following three cases, depending on the size of  $X_L$  and  $X_C$ .

✓ In Case  $X_L > X_C$

- The impedance  $\dot{Z}$  is positive ( $\dot{Z} > 0$ ) and inductive.

✓ In Case  $X_L < X_C$

- The impedance  $\dot{Z}$  is negative ( $\dot{Z} < 0$ ) and capacitive.



# Impedance of the RLC series circuit

## ✓ In Case $X_L = X_C$

- The impedance  $\dot{Z}$  is " $\dot{Z} = R$ ". In this case, the circuit is in series resonance. When series resonance is established, the angular frequency  $\omega$  and frequency  $f$  are as follows:

$$X_L = X_C$$


$$\omega L = \frac{1}{\omega C}$$

$$\Leftrightarrow \omega = \frac{1}{\sqrt{LC}}$$

$$\Leftrightarrow f = \frac{1}{2\pi\sqrt{LC}}$$


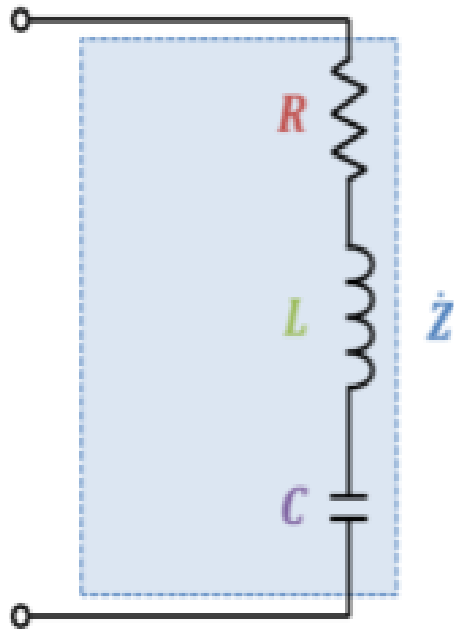
# Magnitude of the impedance of the RLC series circuit



Magnitude  $Z$  of the impedance  $\dot{Z}$

$$Z = |\dot{Z}| = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

The absolute value of

$$\dot{Z} = R + j(X_L - X_C) = R + j\left(\omega L - \frac{1}{\omega C}\right)$$



# Magnitude of the impedance of the RLC series circuit

The magnitude  $Z$  of the impedance  $\dot{Z}$  of the RLC series circuit is the absolute value of "

$$\dot{Z} = R + j \left( \omega L - \frac{1}{\omega C} \right)''.$$

In more detail, the magnitude  $Z$  of the impedance  $\dot{Z}$  can be obtained by adding the square of the real part  $R$  and the square of the imaginary part  $\omega L - \frac{1}{\omega C}$  and taking the square root, which can be expressed in the following equation.

$$Z = |\dot{Z}| = \sqrt{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2}$$





# Vector diagram of the RLC series circuit

The vector diagram of the impedance  $Z$  of the **RLC series circuit** can be drawn in the following steps.

- 1 Draw a vector of impedance  $\dot{Z}_R$  of resistor  $R$
- 2 Draw a vector of impedance  $\dot{Z}_L$  of inductor  $L$
- 3 Draw a vector of impedance  $\dot{Z}_C$  of capacitor  $C$
- 4 Combine the vectors



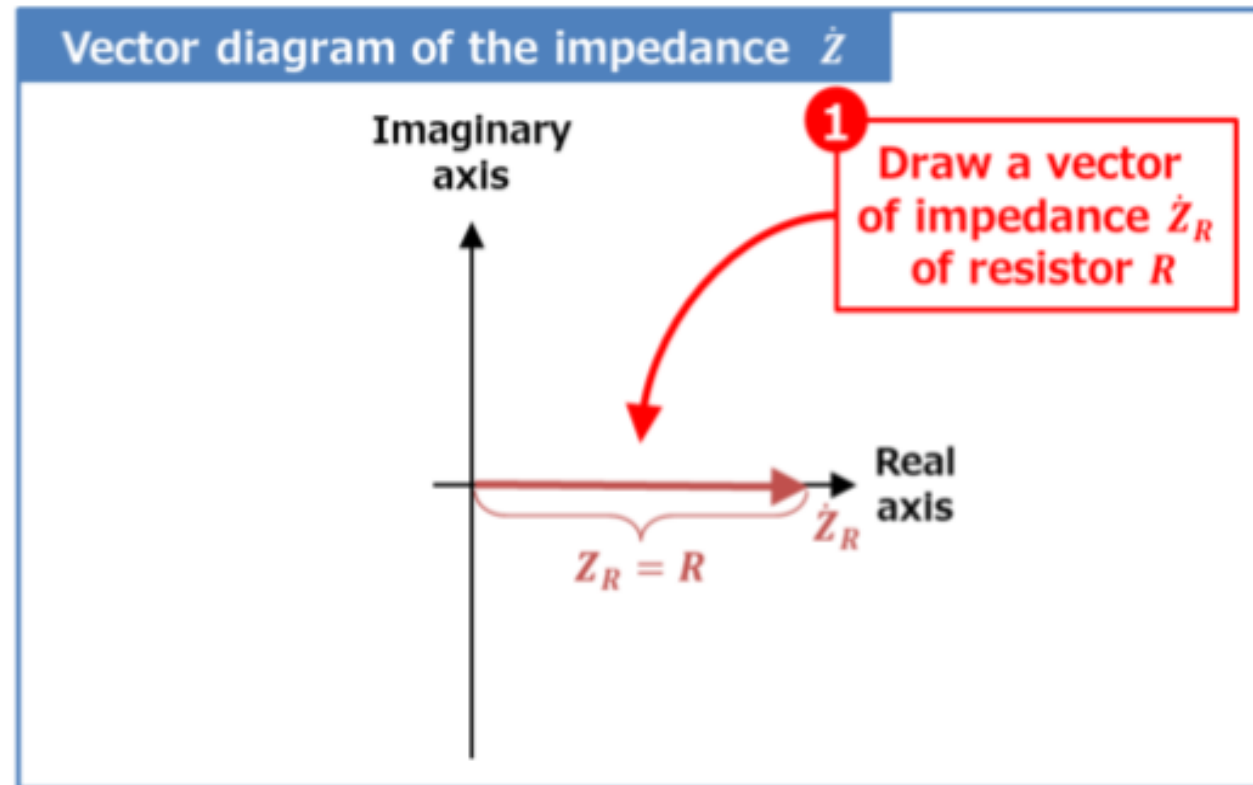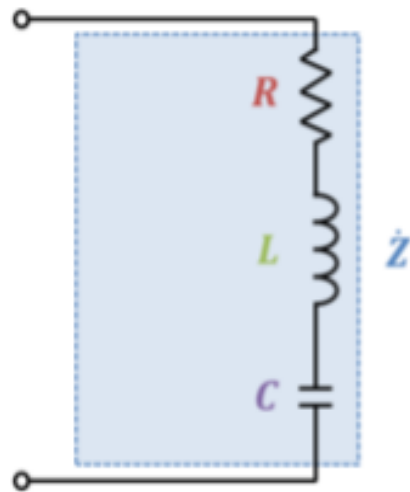
# Draw a vector of impedance $Z_R$ of resistor $R$



The magnitude (length)  $Z_R$  of the vector of the impedance  $\dot{Z}_R$  is " $Z_R = |\dot{Z}_R| = R$ ".


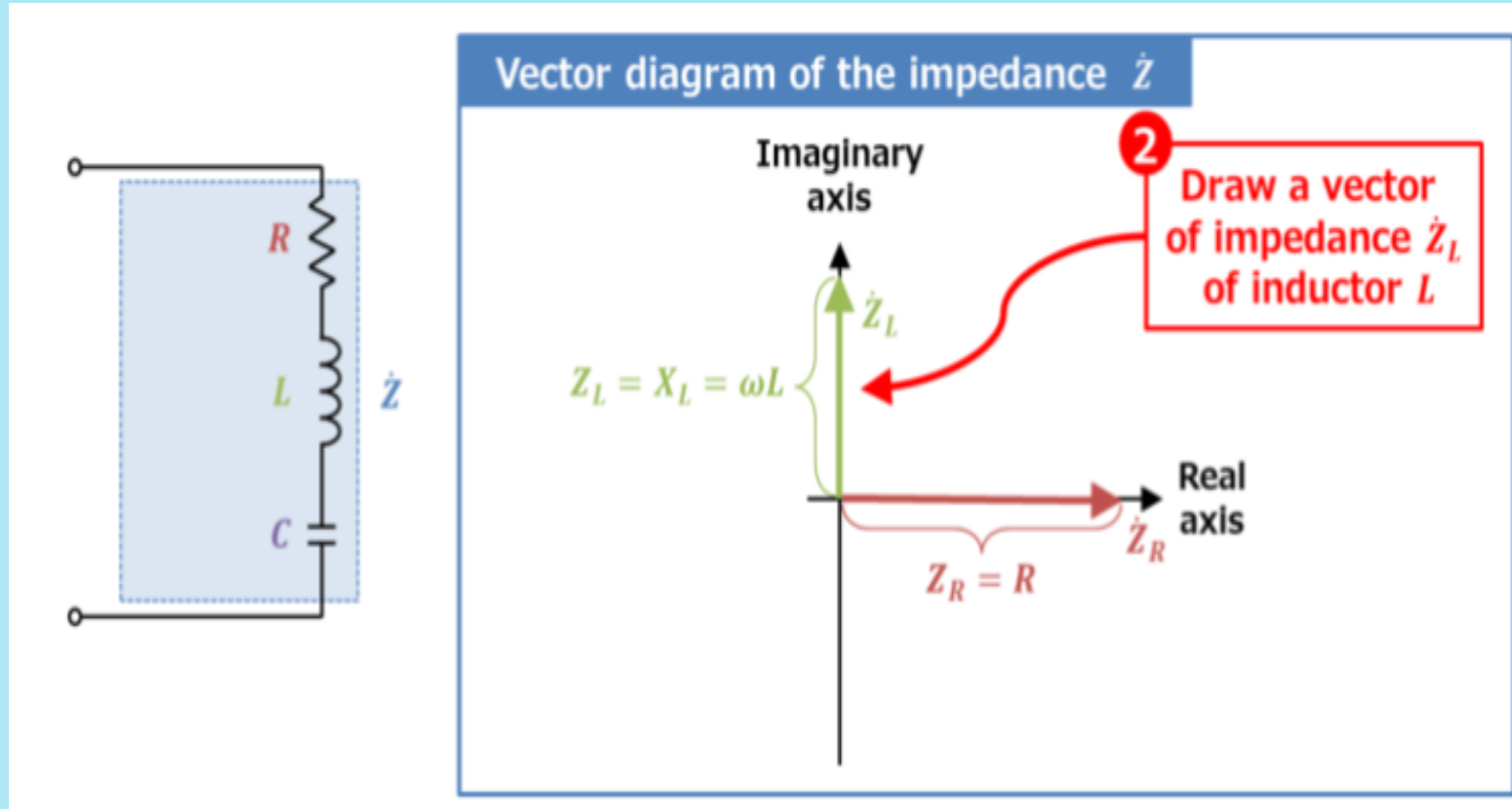
# Draw a vector of impedance $\dot{Z}_L$ of inductor L



The impedance  $Z_L$  of the inductor L is expressed as " $Z_L = j\omega L$ ".





# Draw a vector of impedance $Z_L$ of inductor $L$

Therefore, the impedance  $Z_L$  vector is **90° counterclockwise** around the real axis (with "+j", it rotates 90° counterclockwise).

The magnitude (length)  $Z_L$  of the vector of the impedance  $\dot{Z}_L$  is " $Z_L = |\dot{Z}_L| = \omega L$ ".


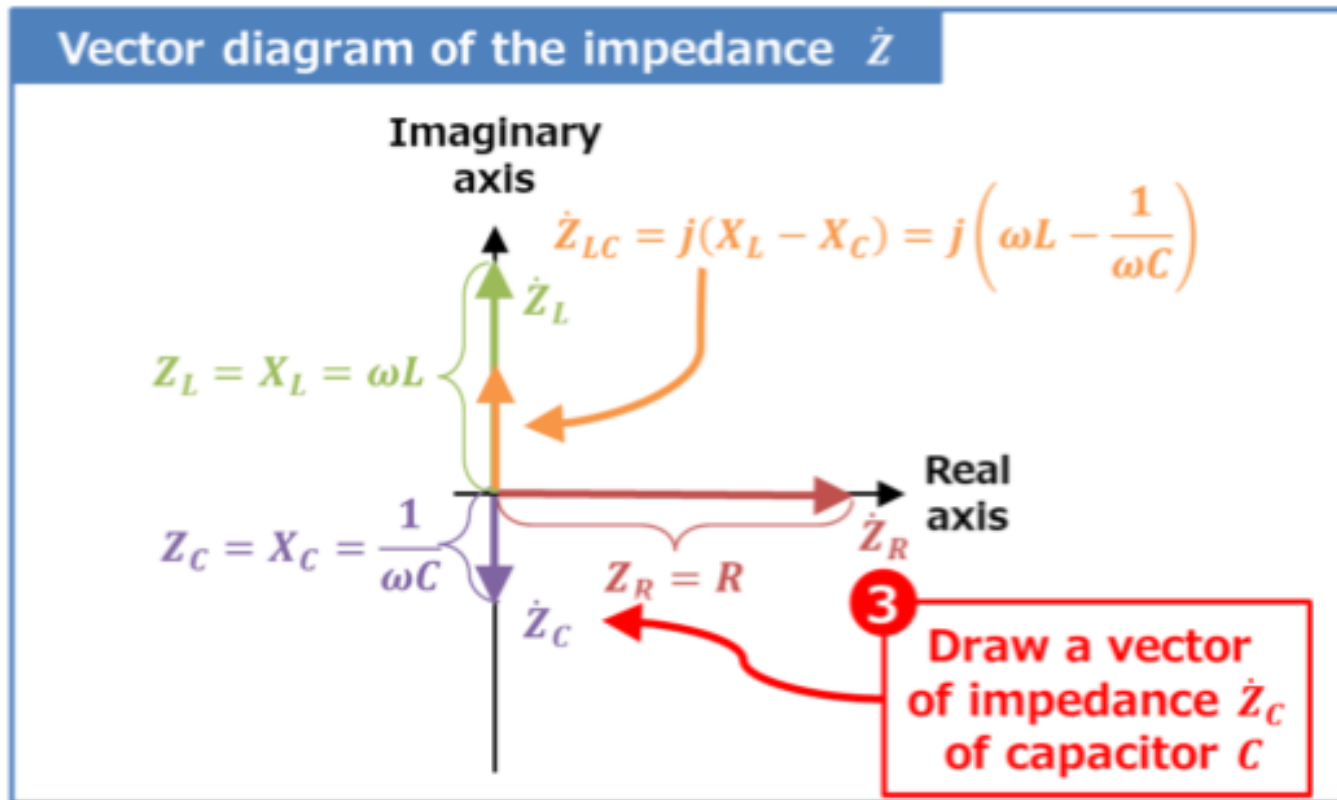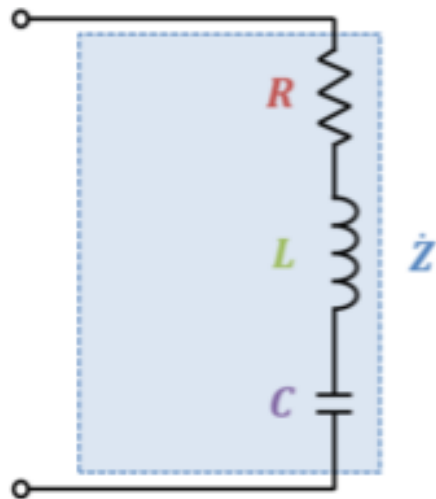
### 3. Draw a vector of impedance $\dot{Z}_C$ of capacitor $C$



The impedance  $\dot{Z}_C$  of the capacitor  $C$  is expressed as " $\dot{Z}_C = -j\frac{1}{\omega C}$ ".








Draw a vector of impedance  $Z_C$  of capacitor  $C$

Therefore, the orientation of the impedance  $Z_C$  vector is  $90^\circ$  clockwise around the real axis (with  $-j$ , it rotates  $90^\circ$  clockwise).

The impedance  $\dot{Z}_C$  of the capacitor  $C$  is expressed as " $\dot{Z}_C = -j \frac{1}{\omega C}$ ".



# 4. Combine the Vectors

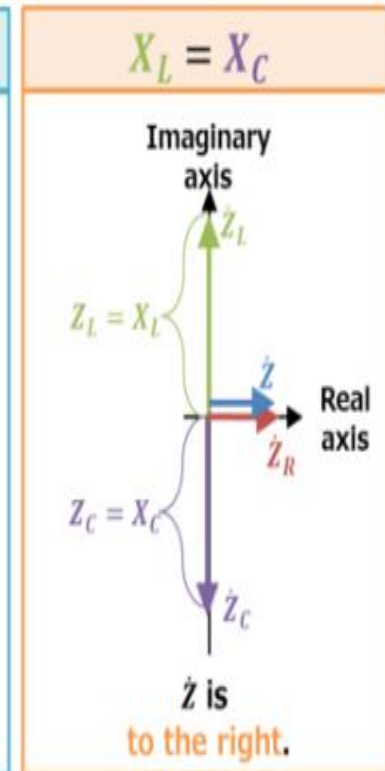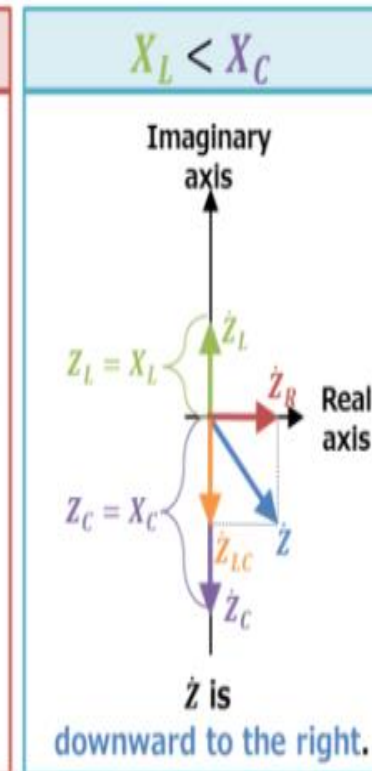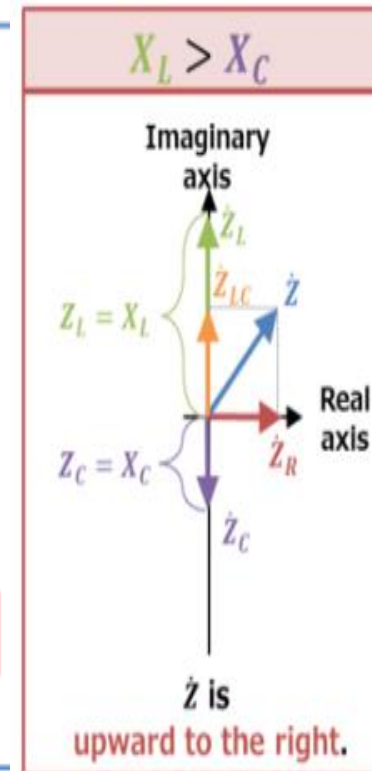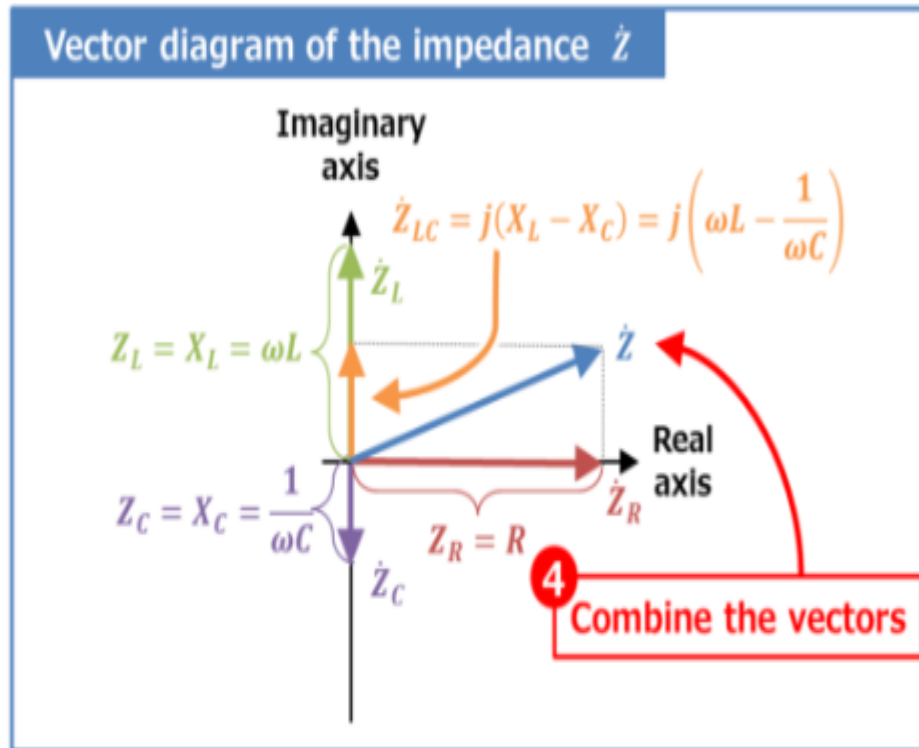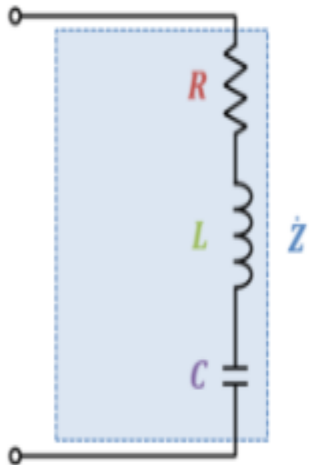



# Combine the Vectors

The **impedance  $Z'$**  of the **RLC series circuit** is the sum of the respective impedance, and is as follow:

$$\begin{aligned}\dot{Z} &= \dot{Z}_R + \dot{Z}_L + \dot{Z}_C \\ &= R + jX_L - jX_C \\ &= R + j(X_L - X_C) \\ &= R + j\left(\omega L - \frac{1}{\omega C}\right)\end{aligned}$$

The magnitude of  $X_L$  and  $X_C$  in the parentheses in the above equation changes the vector direction of the impedance  $Z'$ .



# Combine the Vectors

- ✓ **In Case  $X_L > X_C$** 
  - The vector direction of the impedance  $\dot{Z}$  is upward to the right.
- ✓ **In Case  $X_L < X_C$** 
  - The vector direction of the impedance  $\dot{Z}$  is downward to the right.
- ✓ **In Case  $X_L = X_C$** 
  - Since the impedance  $\dot{Z}$  is " $\dot{Z} = R$ ", the vector direction is to the right.

The magnitude (length)  $Z$  of the vector of the impedance  $\dot{Z}$  can be expressed as follows.

$$Z = |\dot{Z}| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$



# Vector orientation


With "+j" is attached

☑The vector rotates **90° counterclockwise**.

With "-j" is attached

☑The vector rotates **90° clockwise**.

Imaginary axis

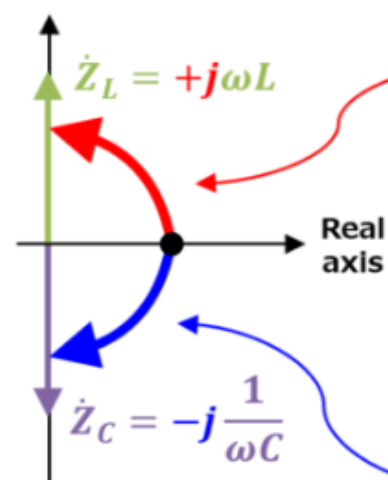

The impedance  $\dot{Z}_L$  of inductor  $L$  is represented by " $\dot{Z}_L = +j\omega L$ ". Therefore, the direction of vector  $\dot{Z}_L$  is **90° counterclockwise** around the real axis.

The impedance  $\dot{Z}_C$  of capacitor  $C$  is represented by " $\dot{Z}_C = -j\frac{1}{\omega C}$ ". Therefore, the direction of vector  $\dot{Z}_C$  is **90° clockwise** around the real axis.



# Vector orientation

When an imaginary unit " $j$ " is added to the expression, the direction of the vector is rotated by  $90^\circ$ .

✓ **With " $+j$ " is attached**

- The vector rotates  **$90^\circ$  counterclockwise**.

✓ **With " $-j$ " is attached**

- The vector rotates  **$90^\circ$  clockwise**.

The impedance  $\dot{Z}_L$  of inductor  $L$  is represented by " $\dot{Z}_L = j\omega L$ ". Therefore, the direction of vector  $\dot{Z}_L$  is  **$90^\circ$  counterclockwise** around the real axis.





The impedance  $\dot{Z}_C$  of capacitor  $C$  is represented by " $\dot{Z}_C = -j\frac{1}{\omega C}$ ". Therefore, the direction of vector  $\dot{Z}_C$  is  **$90^\circ$  clockwise** around the real axis.


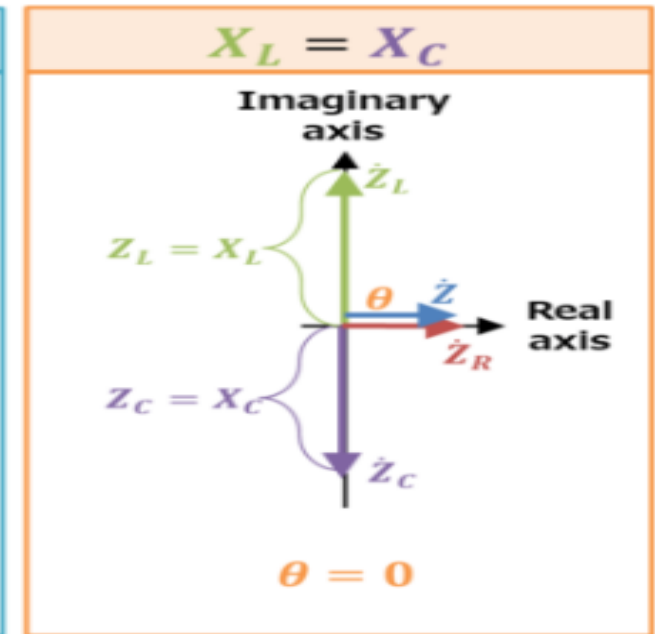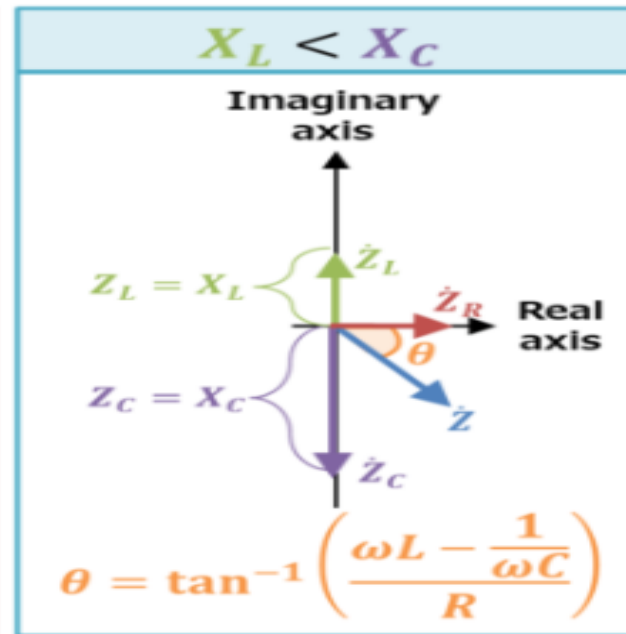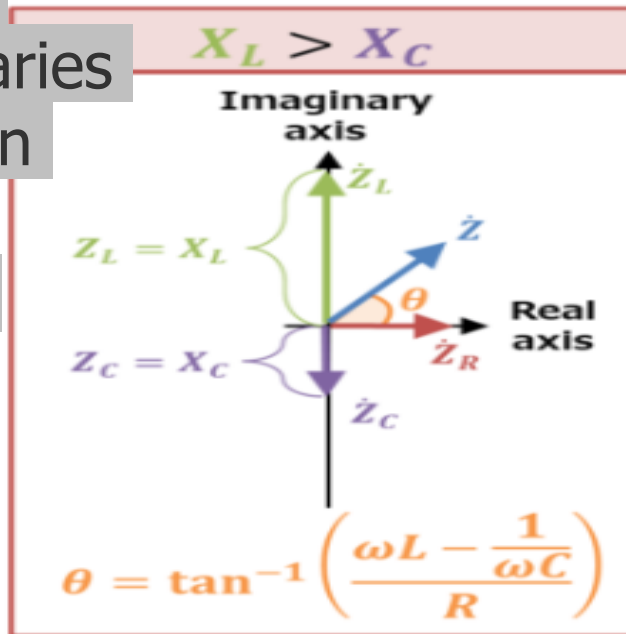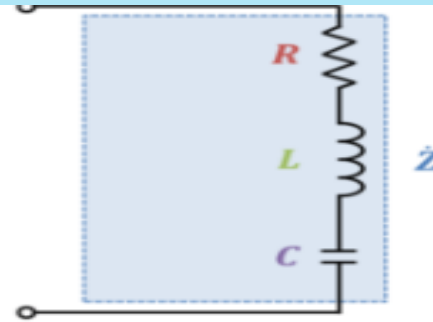
# Impedance **phase angle** of the RLC series circuit



The impedance phase angle ( $\theta$ ) varies depending on the size of  $X_L$  and  $X_C$ .





# Impedance **phase angle** of the RLC series circuit



## ✓ In Case $X_L > X_C$

- The impedance phase angle  $\theta$  is the following value:

$$\theta = \tan^{-1} \left( \frac{X_L - X_C}{R} \right) [\text{rad}]$$

The impedance angle ( $\theta$ ) of the RLC series circuit is "**positive**".

## ✓ In Case $X_L < X_C$

- The impedance phase angle  $\theta$  is the following value:

$$\theta = \tan^{-1} \left( \frac{X_L - X_C}{R} \right) [\text{rad}]$$

The impedance angle ( $\theta$ ) of the RLC series circuit is "**negative**".

## ✓ In Case $X_L = X_C$

- The impedance phase angle  $\theta$  is the following value:

$$\theta = 0 [\text{rad}]$$



# Example

A  $5\Omega$  resistor,  $120\text{mH}$  inductor and  $100\mu\text{F}$  capacitor are connected in series to a  $300\text{V}$ ,  $50\text{Hz}$  AC supply. Calculate

- (a) the current flowing,
- (b) the phase difference between the supply voltage and current,
- (c) the voltage across the circuit elements, and
- (d) draw the phasor and impedance diagram.



# Example

Solution

$$X_L = 2\pi fL = 2\pi(50)(120 * 10^{-3}) = 37.70\Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(50)(100 * 10^{-6})} = 31.83\Omega$$

Since  $X_L$  is greater than  $X_C$  the circuit is inductive

$$X_L - X_C = 37.7 - 31.83 = 5.87\Omega$$

$$\text{impedance } (Z) = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{5^2 + 5.87^2} = 7.71\Omega$$

$$\text{a. current } (i) = \frac{v}{z} = \frac{300}{7.71} = 38.91A$$

$$\text{b. phase angle } \phi = \tan^{-1}\left(\frac{X_L - X_C}{R}\right) = \tan^{-1}\left(\frac{5.87}{5}\right) = 49.58^\circ$$


$$\text{c. } V_R = i * R = 38.91A * 5\Omega = 194.55V$$

$$V_L = i * X_L = 38.91 * 37.7 = 1466.9V$$


$$V_C = i * X_C = 38.91 * 31.83\Omega = 1238.5V$$



# Example

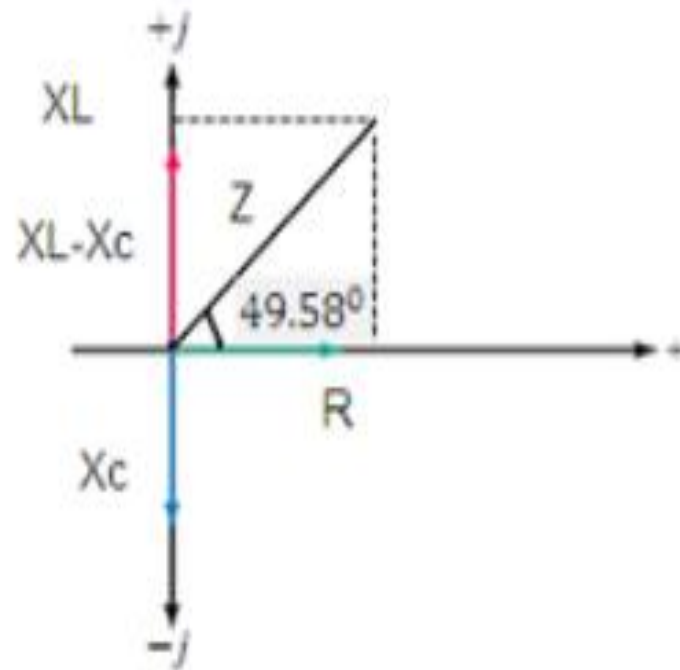

Impedance triangle

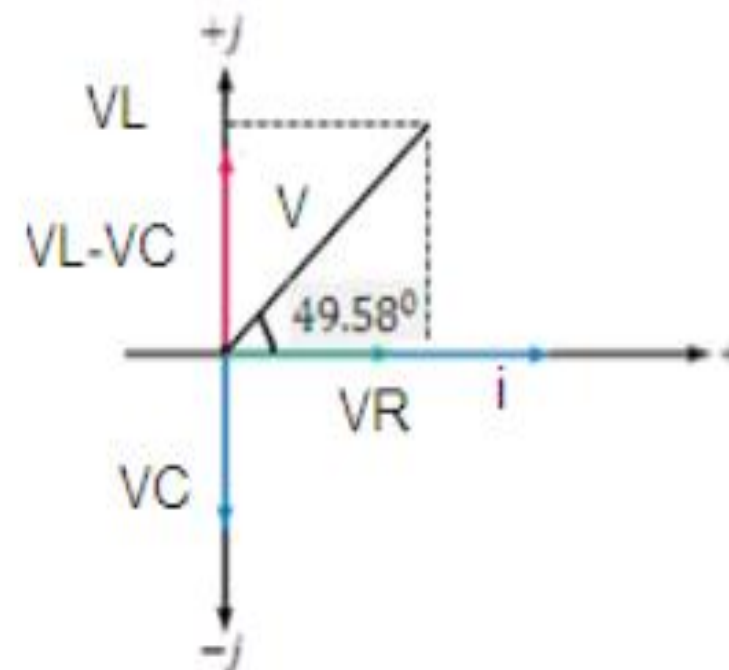

Phasor diagram



# Home Work

- Parallel RLC circuit
- ✓ Impedance
- ✓ Admittance
- ✓ conductance
- ✓ Susceptance
- ✓ Phasor Diagram



<https://electrical-information.com/rlc-series-circuit-impedance/>



# አዳማ ሳይንስ እና ቴክኖሎጂ ዩኒቨርሲቲ Adama Science and Technology University

**Horaa Bulaa!**  
**Thank you**

[www.astu.edu.et](http://www.astu.edu.et)

**We are dedicated to innovative knowledge!**



# ASTU

**School of Electrical Engineering and Computing**

**Department of Electrical Power and Control Engineering**

**Fundamentals of Electrical Engineering (EPCE 2101)**

## **Chapter – 6**

### **Steady State Power Analysis**



# Outlines

1

Instantaneous power

2

Average power

3

Effective or rms value

4

Apparent power and power factor


5

Complex power


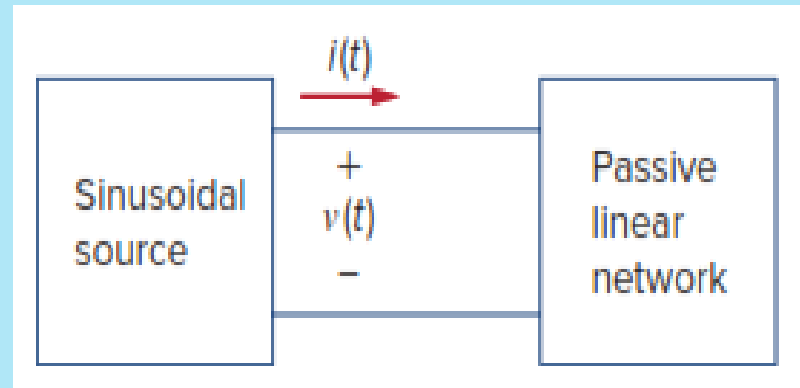
# 1. Instantaneous power

- The **power  $p(t)$  absorbed by an element** is the product of voltage  $v(t)$  across the element and current  $i(t)$  through it.  **$P(t) = v(t) \cdot i(t)$**
- **The instantaneous power** (in watts) is the power at any instant of time.





# 1. Instantaneous power

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

- $V_m$  and  $I_m$  are the amplitudes (or peak values), and
- $\theta_v$  and  $\theta_i$  are the phase angles of the voltage and current, respectively.

➤ The instantaneous power absorbed by the circuit is

$$p(t) = v(t)i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$



# 1. Instantaneous power

- We apply the trigonometric identity

$$\cos A \cos B = \frac{1}{2}[\cos(A - B) + \cos(A + B)]$$

$$p(t) = v(t)i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$



$$p(t) = \frac{1}{2}V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2}V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$




# 1. Instantaneous power

$$p(t) = \frac{1}{2}V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2}V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

- The **instantaneous power** has two parts.
  1. The first part is **constant or time independent**. Its value depends on the phase difference between the voltage and the current.
  2. The second part is **a sinusoidal** function whose frequency is which is **twice the angular frequency** of the voltage or current.



# 1. Instantaneous power

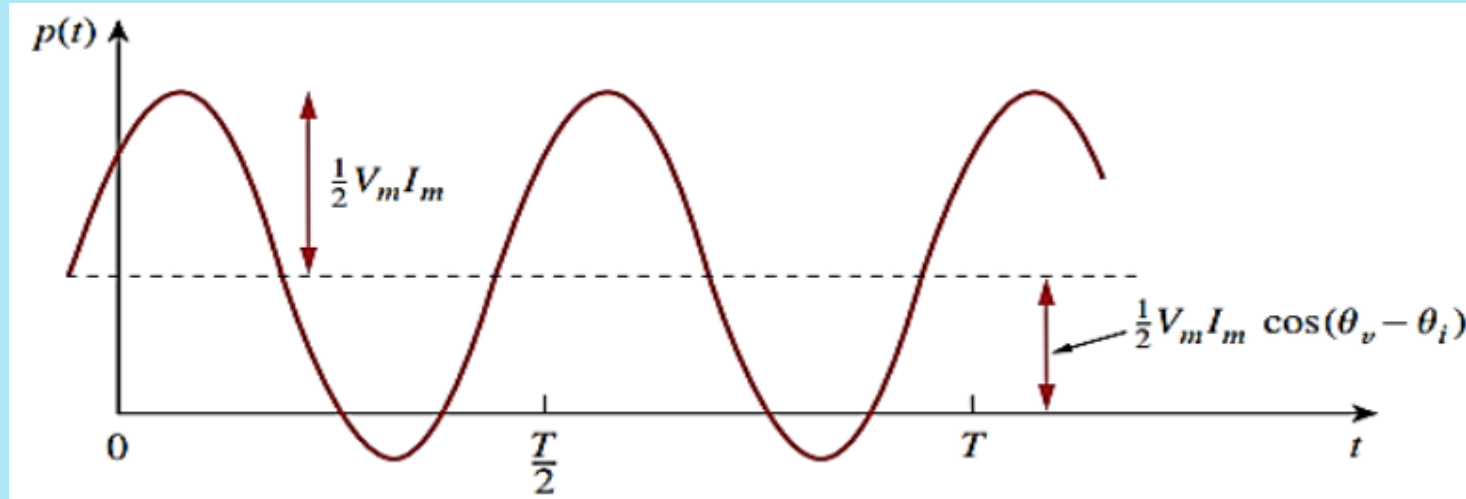

We observe that  $p(t)$  is positive for some part of each cycle and negative for the rest of the cycle.

- ❖ When  $p(t)$  is positive, power is absorbed by the circuit.
- ❖ When  $p(t)$  is negative, power is absorbed by the source



## 2. Average power

- Is the average of the instantaneous power over one period. Thus, the average power is given by

$$P = \frac{1}{T} \int_0^T p(t) dt$$

$$P = \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) dt + \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) dt$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \frac{1}{T} \int_0^T dt + \frac{1}{2} V_m I_m \frac{1}{T} \int_0^T \cos(2\omega t + \theta_v + \theta_i) dt$$



## 2. Average power

- The first integrand is constant, and the average of a constant is the same constant.
- The second integrand is a sinusoid. We know that the average of a sinusoid over its period is zero because the area under the sinusoid during a positive half-cycle is canceled by the area under it during the following negative half-cycle.

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$



## 2.Average power

- To use phasors, we notice that

$$\frac{1}{2}\mathbf{V}\mathbf{I}^* = \frac{1}{2}V_m I_m \angle \theta_v - \theta_i = \frac{1}{2}V_m I_m [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)]$$

- The average power  $P$  thus becomes

$$P = \frac{1}{2}\text{Re}[\mathbf{V}\mathbf{I}^*] = \frac{1}{2}V_m I_m \cos(\theta_v - \theta_i)$$

- **When  $\theta_v = \theta_i$ , the voltage and current are in phase.** This implies a purely resistive circuit or resistive load  $R$ , and

$$P = \frac{1}{2}V_m I_m = \frac{1}{2}I_m^2 R = \frac{1}{2}|\mathbf{I}|^2 R$$



## 2. Average power

- When  $\theta_v - \theta_i = \pm 90^\circ$ , we have a purely reactive circuit, and

$$P = \frac{1}{2} V_m I_m \cos 90^\circ = 0$$

**summary,**

- A resistive load (R) absorbs power at all times, while a reactive load (L or C) absorbs zero average power.



# Example

Given that

$$v(t) = 120 \cos(377t + 45^\circ) \text{ V} \text{ and } i(t) = 10 \cos(377t - 10^\circ) \text{ A}$$

Find the **instantaneous power** and the **average power** absorbed by the passive linear network.



# Solution

- The **instantaneous power** is given by

$$p = v i = 1200 \cos(377t + 45^\circ) \cos(377t - 10^\circ)$$

Applying the trigonometric identity

$$\cos A \cos B = \frac{1}{2} [\cos(A + B) + \cos(A - B)]$$

$$p = 600 [\cos(754t + 35^\circ) + \cos 55^\circ]$$

$$p(t) = 344.2 + 600 \cos(754t + 35^\circ) \text{ W}$$

The average power is

$$\begin{aligned} P &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} 120(10) \cos[45^\circ - (-10^\circ)] \\ &= 600 \cos 55^\circ = 344.2 \text{ W} \end{aligned}$$

which is the constant part of  $p(t)$  above.



# Homework

1. Calculate the average power absorbed by an impedance  $Z = 30 - j70 \, \Omega$  voltage  $v = 120 \angle 0^\circ$  is applied across it.

**Solution:** The current through the impedance is

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{120 \angle 0^\circ}{30 - j70} = \frac{120 \angle 0^\circ}{76.16 \angle -66.8^\circ} = 1.576 \angle 66.8^\circ \text{ A}$$

The average power is

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} (120)(1.576) \cos(0 - 66.8^\circ) = 37.24 \text{ W}$$




# Maximum Average Power Transfer

- In DC circuit analysis we solved the problem of maximizing the power delivered by a supplying resistive network to a load.
- This is done by representing the circuit by its **Thevenin power-equivalent**, *maximum power would be delivered to the load if the load resistance is equal to the Thevenin resistance.*


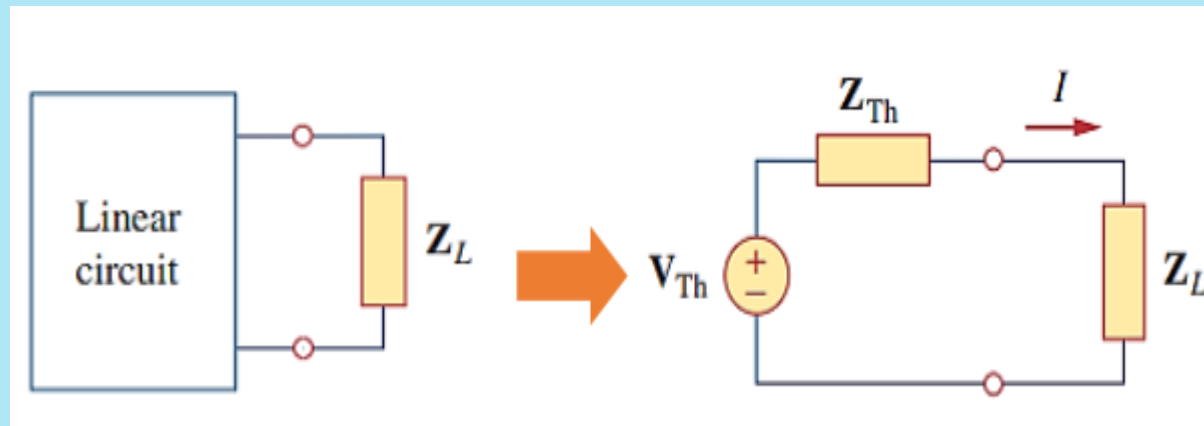
# Maximum Average Power Transfer

- We now extend that result to ac circuits.



$$\mathbf{Z}_{Th} = R_{Th} + jX_{Th}$$

$$\mathbf{Z}_L = R_L + jX_L$$

$$\mathbf{I} = \frac{\mathbf{V}_{Th}}{\mathbf{Z}_{Th} + \mathbf{Z}_L} = \frac{\mathbf{V}_{Th}}{(R_{Th} + jX_{Th}) + (R_L + jX_L)}$$



# Maximum Average Power Transfer

For maximum average power transfer, the load impedance  $Z_L$  must be equal to the complex conjugate of the Thevenin impedance  $Z_{Th}$ .

$$Z_L = R_L + jX_L = R_{Th} - jX_{Th} = Z_{Th}^*$$


The maximum transfer power is given by

$$P_{\max} = \frac{|V_{Th}|^2}{8R_{Th}}$$


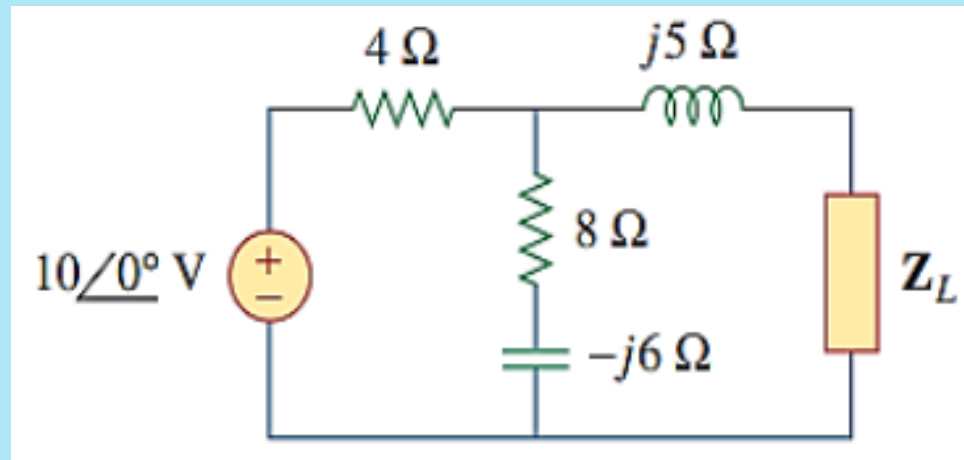
# Homework

Determine the load impedance that maximizes the average power drawn from the circuit shown below. What is the maximum average power?





# solution


First we obtain the Thevenin equivalent

To find  $Z_{th}$ , consider circuit (a)

$$\begin{aligned} Z_{Th} &= j5 + 4 \parallel (8 - j6) \\ &= (2.933 + j4.467) \Omega \end{aligned}$$

To find  $V_{th}$ , consider circuit (b)
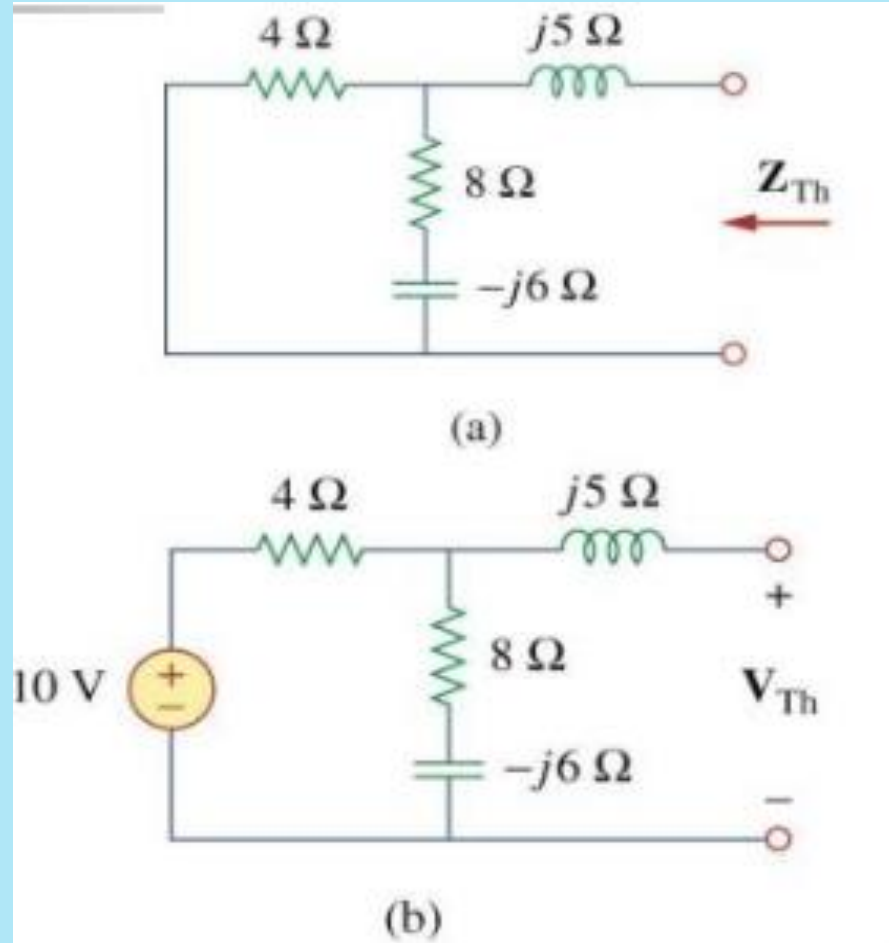
$$\begin{aligned} V_{Th} &= \frac{(8 - j6)}{4 + (8 - j6)} (10 \angle 0^\circ) \\ &= 7.454 \angle -10.3^\circ \text{ V} \end{aligned}$$





# solution

From the result obtained, the load impedance draws the maximum power from the circuit when

$$Z_L = Z_{Th}^* = (2.933 - j4.467)\Omega$$

The maximum average power is

$$P_{\max} = \frac{|V_{Th}|^2}{8R_{Th}} = \frac{(7.454)^2}{8(2.933)} = 2.368W$$




### 3. Effective or rms value

- The idea of effective value arises from the need to measure the **effectiveness of a voltage or current source in delivering power to a resistive load.**
- *The effective value of a periodic current is the dc current that delivers the same average power to a resistor as the periodic current.*
- **The average power absorbed** by the resistor in the **ac circuit is**

$$P = \frac{1}{T} \int_0^T i^2 R dt = \frac{R}{T} \int_0^T i^2 dt$$



### 3. Effective or rms value

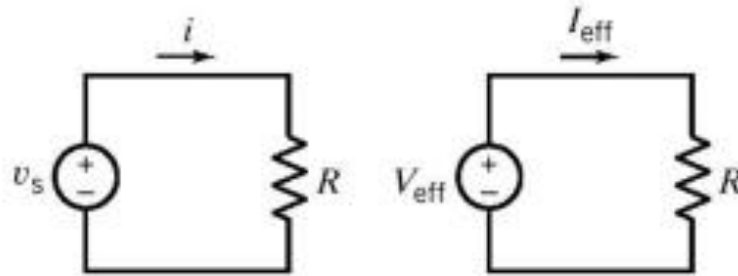

The goal is to find a dc voltage,  $V_{\text{eff}}$  (or dc current,  $I_{\text{eff}}$ ), for a specified  $v_s(t)$  that will deliver *the same average power* to  $R$  as would be delivered by the ac source.

The energy delivered in a period  $T$  is

$$W = PT$$

The average power delivered to the resistor by a periodic current is

$$P = \frac{1}{T} \int_0^T i^2 R dt$$



The power delivered by a direct current is

$$P = I_{eff}^2 R$$

$$\therefore P = \frac{1}{T} \int_0^T i^2 R dt = I_{eff}^2 R$$

Solve for  $I_{eff}$

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

$$= I_{rms} \quad \text{rms} = \text{root-mean-square}$$

The **effective value** of a current is the steady current (dc) that transfer **the same average power** as the given time varying current.



### 3. Effective or rms value

- $I_{\text{rms}} = I_m / \sqrt{2}$

- $V_{\text{rms}} = V_m / \sqrt{2}$

- The average power can be written in terms of the rms values.

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i) \\ = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)$$



# Apparent power(S) and power factor

- If the voltage and current at the terminals of a circuit are

$$v(t) = V_m \cos(\omega t + \theta_v) \text{ and } i(t) = I_m \cos(\omega t + \theta_i),$$

Average power is

$$P = 1/2 (V_m I_m \cos(\theta_v - \theta_i)),$$

$$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i) = S \cos(\theta_v - \theta_i)$$

The average power is a product of two terms.

- The product  $V_{rms}$  and  $I_{rms}$  is known as the **apparent power  $S$** .
- The factor  $\cos(\theta_v - \theta_i)$  is called the **power factor (pf)**.



# Apparent power and power factor

$$P = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i) = S \cos(\theta_v - \theta_i)$$

- Power factor is the cosine of the phase difference between voltage and current .

The power factor is dimensionless, since it is the ratio of the average power to the apparent,

$$\text{pf} = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

The angle  $\theta_v - \theta_i$  is called the power factor angle, since it is the angle, whose cosine is the power factor.



# Apparent power and power factor

## Note

- The **range of pf** is between zero and unity.
- For a purely resistive load, the voltage and current are in phase so that
  - **$\theta_v - \theta_i = 0$  and  $pf = 1$ , the apparent power is equal to average power.**
- For a purely reactive load ,
  - **$\theta_v - \theta_i = \pm 90^\circ$  and  $pf = 0$ , the average power is zero.**
- Leading power factor means that **current leads voltage**,
  - which implies **a capacitive load. [ICE]**
- Lagging power factor means that **current lags voltage**,
  - implying an **inductive load. [ELI]**



# Group Activity

A series-connected load draws a current  $i(t) = 4 \cos(100\pi t + 10^\circ) \text{ A}$  when the applied voltage is  $v(t) = 20 \cos(100\pi t - 20^\circ) \text{ V}$ . Find the **apparent power** and the **power factor** of the load. Determine the element values that form the series-connected load.



# Solution

- The apparent power is



$$S = V_{\text{rms}} I_{\text{rms}} = \frac{120}{\sqrt{2}} \frac{4}{\sqrt{2}} = 240 \text{ VA}$$

- The power factor is



$$\text{pf} = \cos(\theta_v - \theta_i) = \cos(-20^\circ - 10^\circ) = 0.866 \quad (\text{leading})$$

- The pf is leading because the current leads the voltage. The pf may also

$$Z = \frac{V}{I} = \frac{120 \angle -20^\circ}{4 \angle 10^\circ} = 30 \angle -30^\circ = 25.98 - j15 \, \Omega$$

$$\text{pf} = \cos(-30^\circ) = 0.866 \quad (\text{leading})$$

The load impedance  $Z$  can be modeled by a 25.98- $\Omega$  resistor in series with a capacitor

$$X_C = -15 = -\frac{1}{\omega C}$$



$$C = \frac{1}{15\omega} = \frac{1}{15 \times 100\pi} = 212.2 \, \mu\text{F}$$



# Complex Power

- The **complex power S** absorbed by the ac load is the **product of the voltage** and the **complex conjugate of the current**, or

$$S = \frac{1}{2} \mathbf{V} \mathbf{I}^* = V_{\text{rms}} \mathbf{I}_{\text{rms}}^*$$

Where,

$$\begin{aligned} V_{\text{rms}} &= \frac{V}{\sqrt{2}} = V_{\text{rms}} \angle \theta_v & I_{\text{rms}} &= \frac{I}{\sqrt{2}} = I_{\text{rms}} \angle \theta_i \\ S &= V_{\text{rms}} I_{\text{rms}} \angle \theta_v - \theta_i \\ &= V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i) + j V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i) \end{aligned}$$



# Complex Power

- The complex power may be expressed in terms of the load impedance  $Z$ .

$$Z = \frac{V}{I} = \frac{V_{\text{rms}}}{I_{\text{rms}}} = \frac{V_{\text{rms}}}{I_{\text{rms}}} \angle \theta_v - \theta_i$$

Thus,  $V_{\text{rms}} = Z I_{\text{rms}}$ . Substituting this into above equation

$$S = I_{\text{rms}}^2 Z = \frac{V_{\text{rms}}^2}{Z^*} = V_{\text{rms}} I_{\text{rms}}^*$$



Since  $Z = R + jX$ ,

$$S = I_{\text{rms}}^2 (R + jX) = P + jQ$$



# Complex Power

- Where **P** and **Q** are the **real and imaginary** parts of the complex power; that is,

$$P = \text{Re}(\mathbf{S}) = I_{\text{rms}}^2 R$$

$$Q = \text{Im}(\mathbf{S}) = I_{\text{rms}}^2 X$$

- **P** is the **average or real power** and it depends on the load's resistance **R**.
- **Q** depends on the load's reactance **X** and is called the **reactive power**.



# Complex Power

$$S = I_{\text{rms}}^2 (R + jX) = P + jQ$$


$$S = V_{\text{rms}} I_{\text{rms}} \angle \theta_v - \theta_i$$

$$= V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i) + j V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)$$

$$P = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i), \quad Q = V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)$$



# Complex Power[Note]

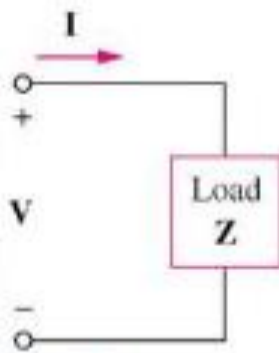

$$S = \frac{1}{2} V I^* = V_{\text{rms}} I_{\text{rms}} \angle \theta_v - \theta_i$$

$$\Rightarrow S = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i) + j V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)$$

$$S = P + jQ$$

P: is the average power in watts delivered to a load and it is the only useful power.

Q: is the reactive power exchange between the source and the reactive part of the load. It is measured in VAR.

- $Q = 0$  for *resistive loads* (unity pf).
- $Q < 0$  for *capacitive loads* (leading pf).
- $Q > 0$  for *inductive loads* (lagging pf).





The **complex power** in rectangular form is

$$\mathbf{S} = \underbrace{\frac{I_m V_m}{2} \cos(\theta_V - \theta_I)}_P + j \underbrace{\frac{I_m V_m}{2} \sin(\theta_V - \theta_I)}_Q$$

or

$$\mathbf{S} = P + jQ$$

*real* or *average power*
*reactive power*

Units    **S: VA,**    **P: W,**    **Q: VAR**  
                  Volt-Amp                    Volt-Amp Reactive



The *impedance* of the element can be expressed as

$$\mathbf{Z}(\omega) = \frac{\mathbf{V}(\omega)}{\mathbf{I}(\omega)} = \frac{V_m \angle \theta_V}{I_m \angle \theta_I} = \frac{V_m}{I_m} \angle (\theta_V - \theta_I)$$

In rectangular form

$$\mathbf{Z}(\omega) = \underbrace{\frac{V_m}{I_m} \cos(\theta_V - \theta_I)}_R + j \underbrace{\frac{V_m}{I_m} \sin(\theta_V - \theta_I)}_X$$

or

$$\mathbf{Z}(\omega) = R + jX$$

A diagram showing the equation Z(ω) = R + jX. Below R is an oval containing the word "resistance" in green. Below jX is an oval containing the word "reactance" in green. Arrows point from R to the "resistance" oval and from jX to the "reactance" oval.



# Complex Power[Note]

- The real power **P** is the **average power in watts** delivered to a load;
  - *It is the only useful power.*
  - *It is the actual power dissipated by the load.*
- The reactive power **Q** is a measure of the energy exchange between the source and the reactive part of the load.
  - *The unit of **Q** is the **volt-ampere reactive (VAR)** to distinguish it from the real power, whose unit is the watt.*



# Summary

$$\begin{aligned}\text{Complex Power} = \mathbf{S} &= P + jQ = \mathbf{V}_{\text{rms}}(\mathbf{I}_{\text{rms}})^* \\ &= |\mathbf{V}_{\text{rms}}| |\mathbf{I}_{\text{rms}}| \angle \theta_v - \theta_i\end{aligned}$$

$$\text{Apparent Power} = S = |\mathbf{S}| = |\mathbf{V}_{\text{rms}}| |\mathbf{I}_{\text{rms}}| = \sqrt{P^2 + Q^2}$$

$$\text{Real Power} = P = \text{Re}(\mathbf{S}) = S \cos(\theta_v - \theta_i)$$

$$\text{Reactive Power} = Q = \text{Im}(\mathbf{S}) = S \sin(\theta_v - \theta_i)$$

$$\text{Power Factor} = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

➤ **Real Power** is the actual power dissipated by the load.

➤ **Reactive Power** is a measure of the energy exchange between source and reactive part of the load



# Summary


1.  $Q = 0$  for resistive loads (unity pf).
2.  $Q < 0$  for capacitive loads (leading pf).
3.  $Q > 0$  for inductive loads (lagging pf).

*Thus, Complex power (in VA) is the product of the rms voltage phasor and the complex conjugate of the rms current phasor. As a complex quantity, its real part is real power  $P$  and its imaginary part is reactive power  $Q$ .*


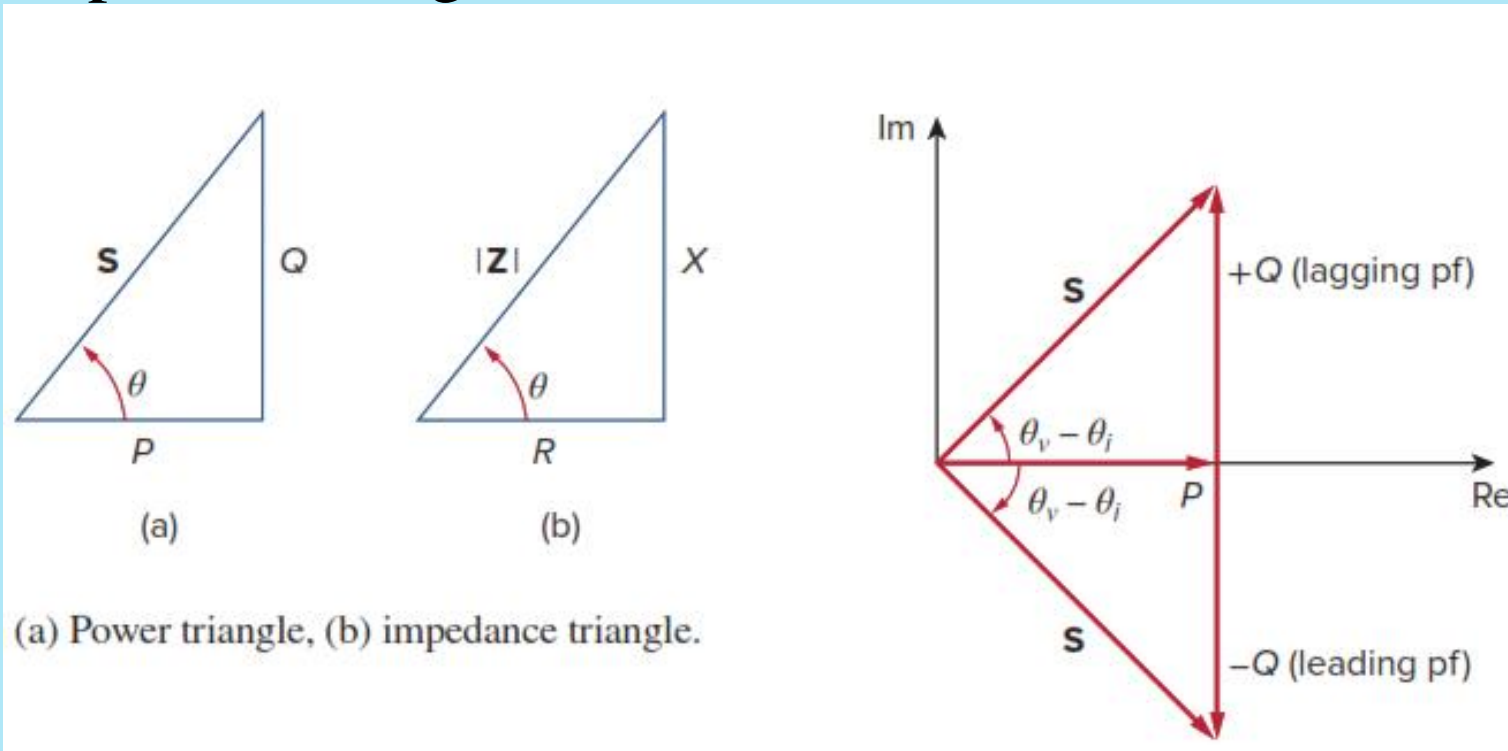
# Summary

- It is a standard practice to represent **S, P, and Q** in the form of a triangle, known as the power triangle,





# Homework


The voltage across a load is  $v(t)=60 \cos (\omega t - 10^{\circ}) \text{ V}$  and the current through the element in the direction of the voltage drop is  $i(t)=1.5 \cos (\omega t + 50^{\circ}) \text{ A}$ . Find: (a) the complex and apparent powers, (b) the real and reactive powers, and (c) the power factor and the load impedance.

**ANS: a).  $45 (60^{\circ}) \text{ VA}$  b).  $P = 22.5 \text{ W}, Q = -38.97 \text{ VAR}$  c). 0.5 (leading)**



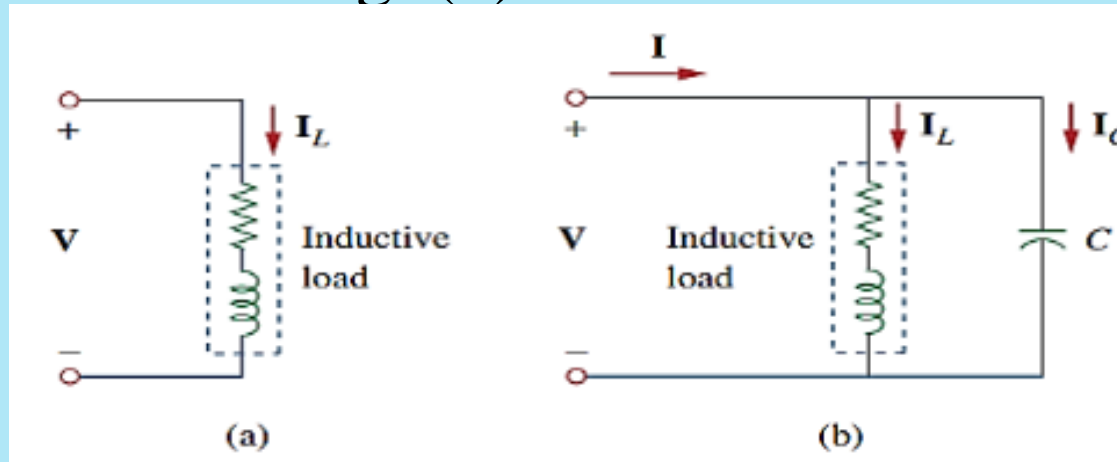
# Power factor and power factor correction

- The **process of increasing the power factor** without changing the voltage or current to the original load is **known as power factor correction**.
- Since **most loads are inductive**, as shown in Fig.(a), a load's power factor is **improved or corrected by deliberately installing a capacitor in parallel with the load**, as shown in Fig. (b).







PF

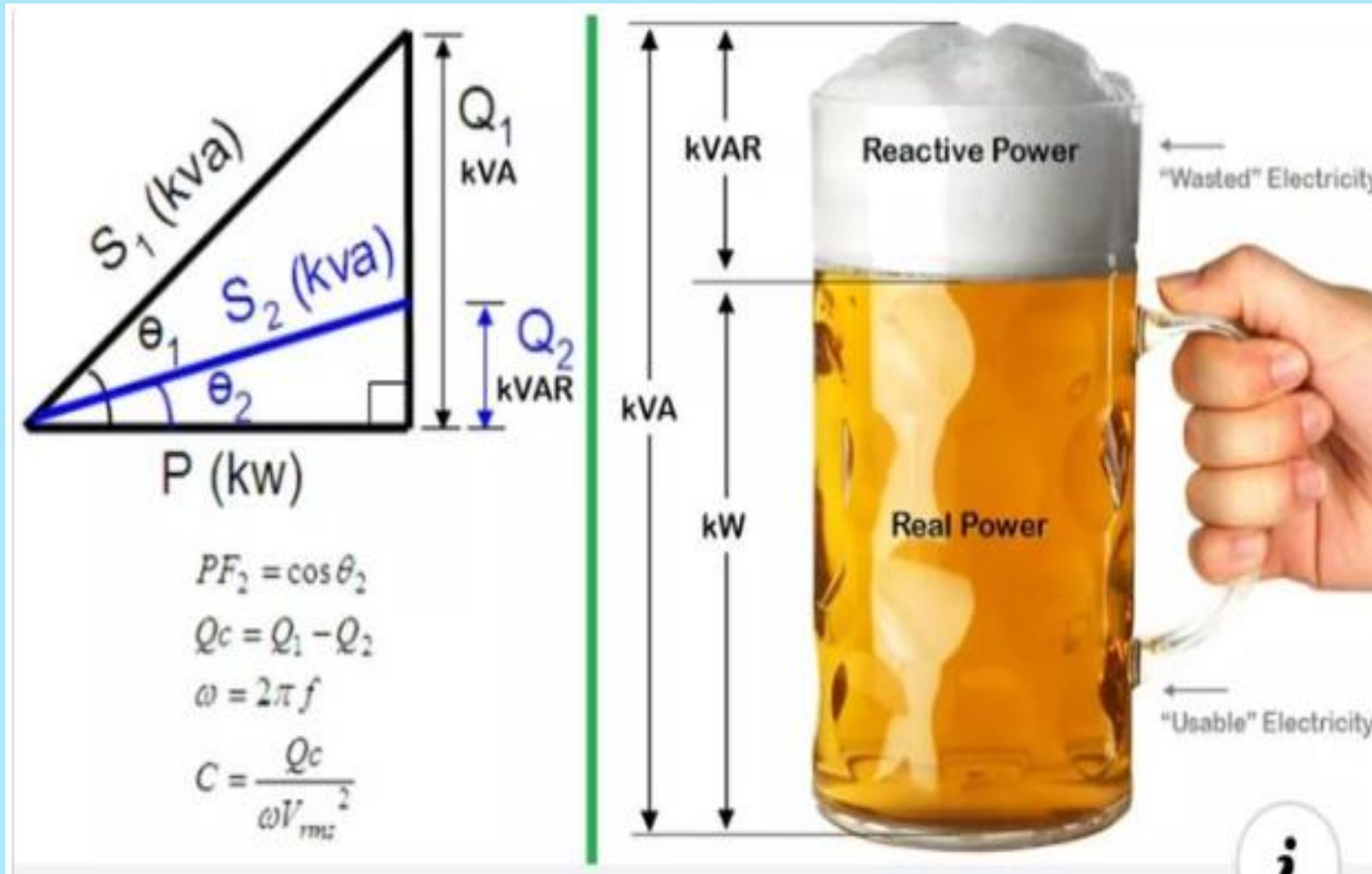
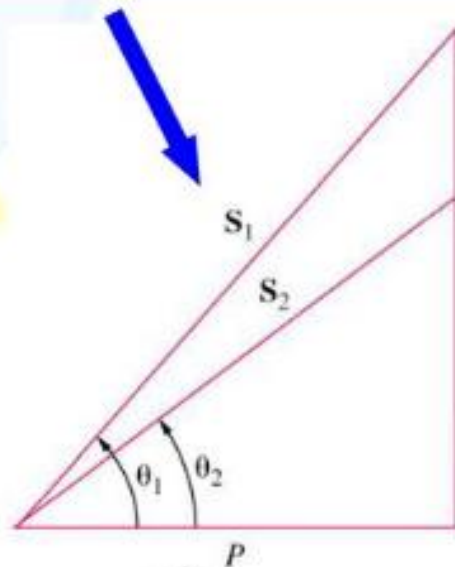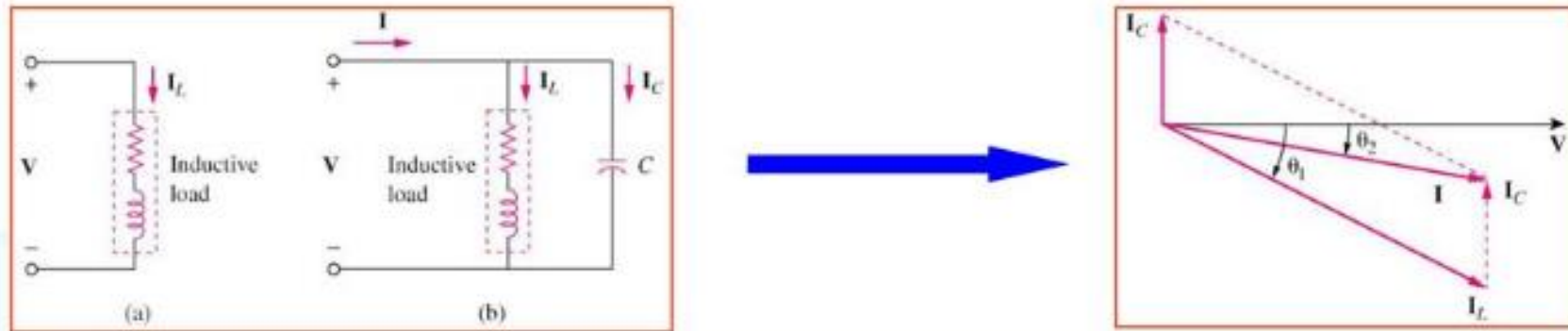
# Power factor and power factor correction



$$Q_c = Q_1 - Q_2$$

$$= P (\tan \theta_1 - \tan \theta_2)$$

$$= \omega C V_{rms}^2$$

$$Q_1 = S_1 \sin \theta_1$$

$$= P \tan \theta_1$$

$$C = \frac{Q_c}{\omega V_{rms}^2} = \frac{P (\tan \theta_1 - \tan \theta_2)}{\omega V_{rms}^2}$$

$$P = S_1 \cos \theta_1$$

$$Q_2 = P \tan \theta_2$$



# Power factor and power factor correction

- The reduction in the **reactive power** is caused by the **shunt capacitor**; that is,

$$Q_C = Q_1 - Q_2 = P(\tan \theta_1 - \tan \theta_2) \quad Q_C = V_{\text{rms}}^2 / X_C = \omega C V_{\text{rms}}^2$$

- The value of the required **shunt capacitance C** is determined as

$$C = \frac{Q_C}{\omega V_{\text{rms}}^2} = \frac{P(\tan \theta_1 - \tan \theta_2)}{\omega V_{\text{rms}}^2}$$



# Power factor and power factor correction

- **Shunt inductance L** can be calculated from

$$Q_L = \frac{V_{rms}^2}{X_L} = \frac{V_{rms}^2}{\omega L} \Rightarrow L = \frac{V_{rms}^2}{\omega Q_L}$$

- Where  **$Q_L = Q_1 - Q_2$** , the difference between the new and old reactive powers.



## Example

When connected to a 120-V (rms), 60-Hz power line, a load absorbs 4 kW at a lagging power factor of **0.8**. Find the **value of capacitance** necessary to raise the pf to **0.95**.



# Solution

- If the  $\text{pf} = 0.8$ , then

$$\cos \theta_1 = 0.8 \Rightarrow \theta_1 = 36.87^\circ$$

Where

*$\theta_1$  is the phase difference between voltage and current.* We obtain the apparent power from the real power and the pf as

$$S_1 = \frac{P}{\cos \theta_1} = \frac{4000}{0.8} = 5000 \text{ VA}$$

The reactive power is

$$Q_1 = S_1 \sin \theta = 5000 \sin 36.87 = 3000 \text{ VAR}$$



# Solution

- When the **pf** is raised to **0.95**,

$$\cos \theta_2 = 0.95 \Rightarrow \theta_2 = 18.19^\circ$$

- The **real power P** has not changed. But the apparent power has changed; its new value is

$$S_2 = \frac{P}{\cos \theta_2} = \frac{4000}{0.95} = 4210.5 \text{ VA}$$

- The new reactive power is  **$Q_2 = S_2 \sin \theta_2 = 1314.4 \text{ VAR}$**



# Solution

- The difference between the new and old reactive powers is due to the parallel addition of the capacitor to the load. The reactive power due to the capacitor is

$$Q_C = Q_1 - Q_2 = 3000 - 1314.4 = 1685.6 \text{ VAR}$$

$$C = \frac{Q_C}{\omega V_{\text{rms}}^2} = \frac{1685.6}{2\pi \times 60 \times 120^2} = 310.5 \mu\text{F}$$



## Benefits of reading

