

CH-4

Transient Circuit Analysis

Terminology

First Order circuit: - Only contains energy storage elements
- their v's or currents are described by 1st ODE.

Two types of 1st order ckt's

① RL circuit

② RC circuit

Natural Response: - How the ckt's respond when a switch is opened or closed.

RC and RL ckt's: - the equation to analyze RC or RL ckt is 1st ODE.
Thus, RC and RL ckt are known as 1st order ckt's.

↳ To analyze the resistor (resistive) ckt, algebraic eq's are needed.

↳ To analyze C and L time-differential equations are involved.


Sources

① Source-free ckt's: - Initial conditions.



The energy is initially stored in C or L, and the energy causes current to flow in the ckt and is gradually dissipated in resistors.

② Independent sources: - DC, sinusoidal & exponential source

SWITCH

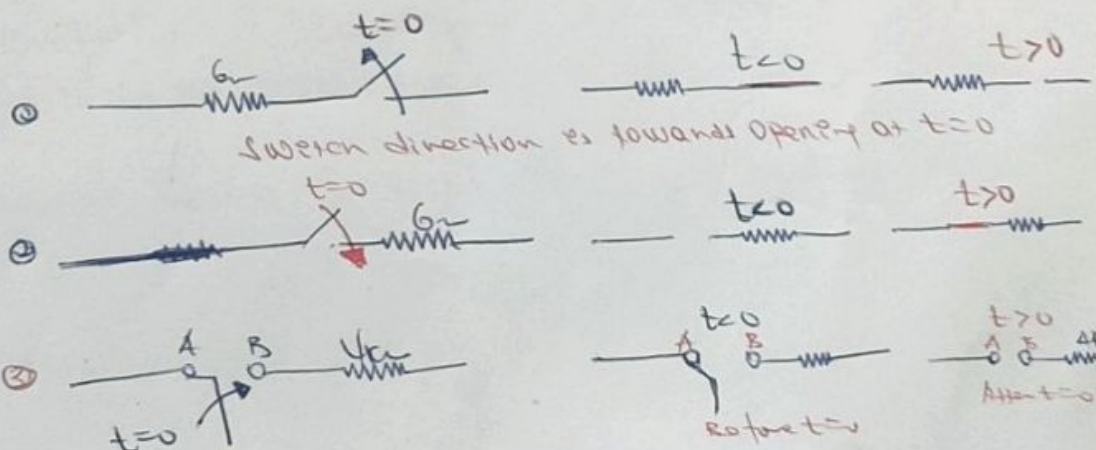

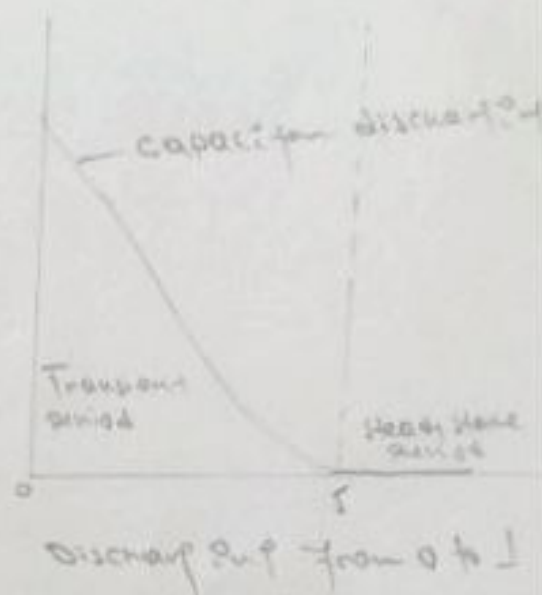
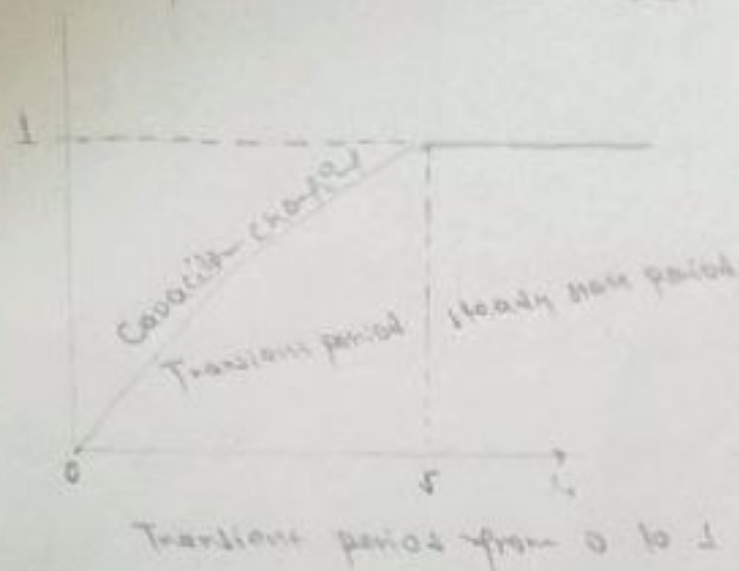
Be for source free R or L or C capacitor
charging and discharging.



③ capacitor voltage cannot change abruptly

① Natural Response of an R circuit

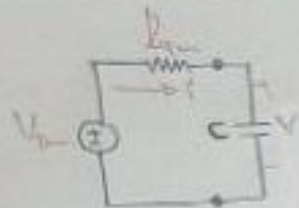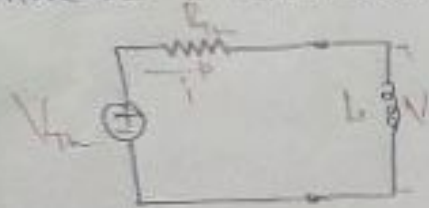A circuit that can be simplified to a Thevenin-Norton equivalent connected to either an inductor or capacitor.




What's natural response?

- It describes the "discharging" of inductor or capacitor via absence of an independent source.
- No external source enforced is called "natural response".

Natural Response of an RL circuit

②

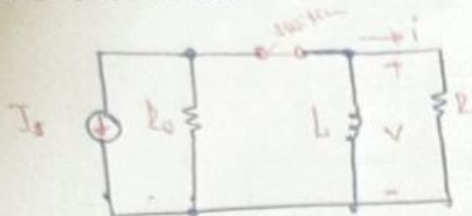
Let the ckt shown which contains an inductor is shown



Suppose the switch has been in a closed position for a long time.
• for the time being ~~long time~~


- All currents and voltages have reached a constant value
- Only constant or DC current can exist in the ckt just prior to the switch's being opened.
- The inductor appears as a short ckt

$$V = L \frac{di}{dt} = 0$$

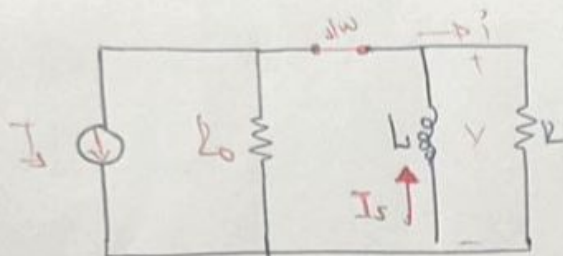


- ⊗ When the switch is closed, the inductor appears as a short, the voltage across the branch is zero.
- ⊗ When L appears as a short, no current goes through R_0 & R .
- ⊗ The current (the source current) I_s all goes through L.
OR
- Because the v/dg across the inductive branch is zero.
- no current on either R_0 or R
- All the source current I_s appears on inductive branch

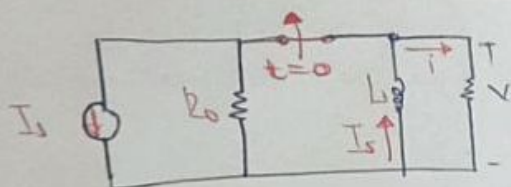Finding the Natural response requires finding the v/dg-current at any branch on the ckt after the switch has been opened.




If we let $t=0$ denote the instant when the switch is opened

for $t \geq 0$ the ckt becomes

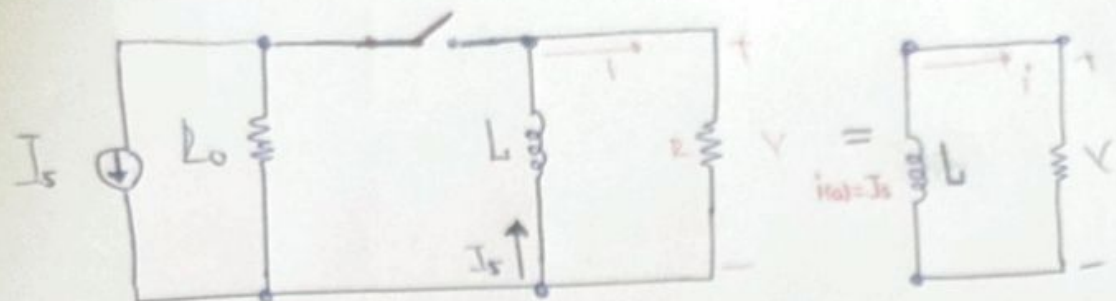

Ⓛ The problem becomes one of finding $V(t)$ & $i(t)$ ($i = i(t)$) for $t \geq 0$

Deriving the Expression for the current

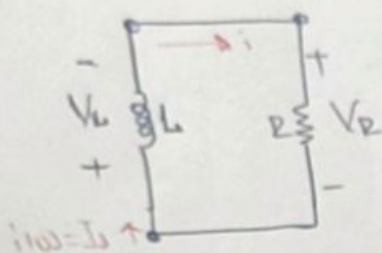

Apply KVL around the loop

$$V_L + V_R = 0$$

$$L \frac{di}{dt} + Ri = 0$$

Inductor Law

Ohm's law


This is a 1st order DE because it contains terms involving the ordinary derivative of the unknown $\frac{di}{dt}$

The Highest order derivative appearing in the eqn is 1st order

- We can still describe the equation further

Ⓛ Since the coefficients on equation 2 & 3 are constant that is not func of either the dependent variable i or independent variable t

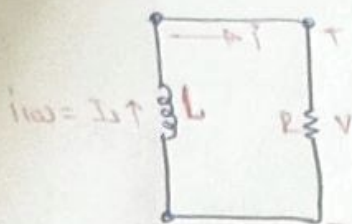- Thus the equations can be described as an ODE w constant coefficients



$$L \frac{di}{dt} + Ri = 0$$

$$L \frac{di}{dt} = -Ri$$

$$\frac{di}{dt} = -\frac{R}{L}i$$

$$\frac{di}{i} dt = -\frac{R}{L} dt \quad \left[\text{Take the differential w respect to time of both sides of the equation} \right]$$

$$di = -\frac{R}{L}i dt$$

$$\frac{di}{i} = -\frac{R}{L} dt$$

③ Integrating both side to obtain explicit expression for i as a function of t

$$\int_{i(t_0)}^{i(t)} \frac{dx}{x} = -\frac{R}{L} \int_{t_0}^t dt$$

Here $t_0 = 0$

$$\int_{i(0)}^{i(t)} \frac{dx}{x} = -\frac{R}{L} \int_0^t dt$$

$$\ln(i(t)) - \ln(i(t_0)) = -\frac{R}{L}(t - t_0) \quad t_0 = 0$$

$$\ln(i(t)) - \ln(i(0)) = -\frac{R}{L}t$$

$$\ln \frac{i(t)}{i(0)} = -\frac{R}{L}t$$

Based on the definition of the natural logarithm $\boxed{\ln x = x}$

- Apply base e to both sides

$$e^{\ln \frac{i(t)}{i(0)}} = e^{-\frac{R}{L}t}$$

$$\frac{i(t)}{i(0)} = e^{-\frac{R}{L}t}$$

$$\boxed{i(t) = i(0) e^{-(R/L)t}}$$

Instantaneous change of current cannot occur in an inductor

✓ The instant ~~resistor~~ ~~switch~~ is opened, the current in the inductor remains unchanged.

Since the current through an inductor cannot change abruptly or instantaneously

$$i(0^-) = i(0^+) = i(0) = I_0$$


⊗ Use 0^- to denote time prior to switching
 Use 0^+ to denote time immediately after switching

Where I_0 is the initial current in the inductor just before the switch is opened (or in some cases closed)

In the ckt above $I_0 = I_s$

Therefore
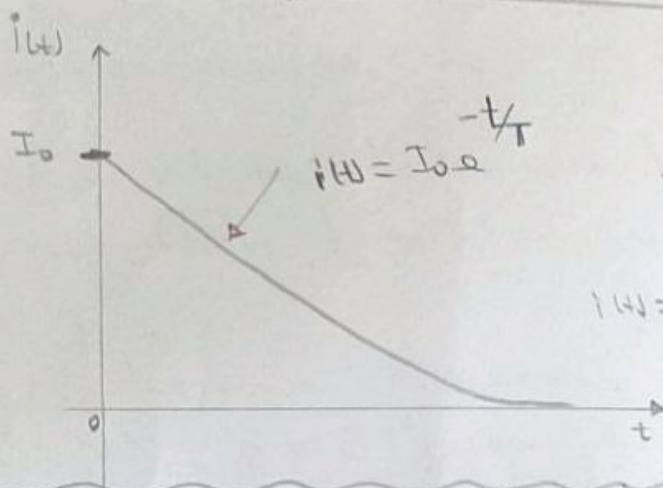
$$i(t) = I_0 e^{-t/\tau} \quad t \geq 0$$



When $t = 0$, $i(t) = I_0$

$i(t) = I_0 e^0 = I_0$

When $t = \tau$

$i(t) = I_0 e^{-1} = \frac{I_0}{e}$

⊗ which shows current starts at the initial value I_0 and decreases exponentially toward zero as t increases.

Voltage


We derive the voltage across the resistor from direct application of Ohm's law.

$$V(t) = Ri(t)$$

$$\text{but } i(t) = I_0 e^{-(R/L)t} \quad t \geq 0^+$$

$$V(t) = RI_0 e^{-(R/L)t} \quad t \geq 0^+$$

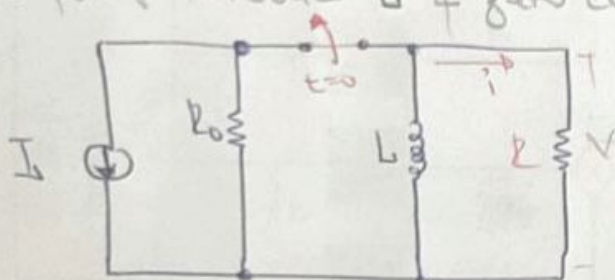Note The Voltage $V(t)$ here is defined for $t \geq 0$ because the voltage across the resistor R is zero for $t < 0$ (all the current I_0 was going through L & zero current through R)



$$\begin{cases} V(0^-) = 0 \\ V(0^+) = I_0 R \end{cases}$$

Voltage is only defined for $t > 0$, not at $t = 0$ because after voltage occurs at $t = 0$.

Because of the step voltage the value at $t = 0$ is unknown therefore only $t \geq 0^+$ defines region of validity

Power

We derive the power dissipated in the resistor

$$P = VI, \quad P = Ri^2, \quad \text{or } P = V^2/R$$

$$P = (I_0 e^{-(R/L)t})^2 \times R \quad \text{for } t \geq 0^+$$

Squaring the current yields:

$$P = I_0^2 R e^{-2(R/L)t} \quad \text{for } t \geq 0^+$$

$$\begin{aligned} & e^{-(R/L)t} \cdot e^{-(R/L)t} \\ &= e^{-(R/L)t + (R/L)t} \\ &= e^{-2(R/L)t} \end{aligned}$$

Note the current $i(t)$ through the resistor is zero for $t < 0$ $\therefore P = 0, \quad t < 0$

Energy:

The energy deliver to the resistor is after the switch is opened because before there was no current passing through the resistor and the voltage across it was zero.

$$\begin{aligned} W &= \int_0^t p dx = \int_0^t I_0^2 R e^{-2(R/L)t} dx = I_0^2 R \int_0^t e^{-2(R/L)t} x dx \\ &= I_0^2 R \left[\frac{1}{-2(R/L)} \left(e^{-2(R/L)t} \right) \right]_0^t \\ &= I_0^2 R \left[\frac{1}{-2(R/L)} \left(e^{-2(R/L)t} - e^{-2(R/L)0} \right) \right] \\ &= I_0^2 R \left[\frac{1}{-2(R/L)} \left(e^{-2(R/L)t} - 1 \right) \right] \\ &= \frac{1}{2} I_0^2 L (1 - e^{-2(R/L)t}) \\ &= \frac{1}{2} L I_0^2 (1 - e^{-2(R/L)t}) \quad \text{for } t \geq 0 \end{aligned}$$

$$\therefore W = \frac{1}{2} L I_0^2 (1 - e^{-2(R/L)t}) \quad \text{for } t \geq 0$$

Recap

$$\begin{aligned} i(t) &= I_0 e^{-(R/L)t} \quad \text{for } t \geq 0 \\ v &= I_0 R e^{-(R/L)t} \quad \text{for } t \geq 0^+ \\ p &= I_0^2 R e^{-2(R/L)t} \quad \text{for } t \geq 0^+ \\ W &= \frac{1}{2} L I_0^2 (1 - e^{-2(R/L)t}) \quad \text{for } t \geq 0 \end{aligned}$$

$$\tau = \frac{L_{eq}}{R_{eq}}$$

The significance of the time constant

The coefficient of the exponential form namely R/L determine the rate at which the exponential form on the current approaches zero.

Time constant (τ) - Determine the rate at which the current or voltage approaches zero.

$$\tau = \text{Time constant} = \frac{L}{R} \quad \tau - \text{tau}$$


* Time constant for R, L ckt is $\tau = L/R$

Re-write the equation w/ τ

$$\begin{aligned} i(t) &= I_0 e^{(-t/\tau)} \quad \text{for } t \geq 0 \\ v &= I_0 R e^{(-t/\tau)} \quad \text{for } t \geq 0 \\ p &= I_0^2 R e^{(-2t/\tau)} \quad \text{for } t \geq 0 \\ W &= \frac{1}{2} L I_0^2 (1 - e^{(-2t/\tau)}) \quad \text{for } t \geq 0 \end{aligned}$$

Time Constant Characteristics

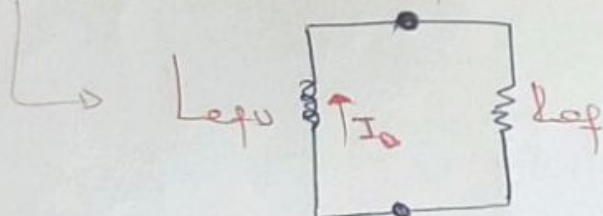- After 5 time constants, currents & vts have reached their final value.
- A long time - implies 5 or more time constants have elapsed.
- Steady-state response - the response that exists a long time after switching has taken place.
- The existence of current in the R, L ckt is a momentary event and is called a transient response.



At t time constant current is less than 1% of its initial value (I_0)

$$t = \frac{- (1/4)}{e}$$

$$I(t) = I_0 e^{- (t/\tau)}$$

$$\tau = 3.6188 \times 10^{-1}$$

When $t = \tau$

$$0.7 = 1.3134 \times 10^{-1}$$

$$i(\tau) = I_0 e^{- (\tau/\tau)}$$

$$3\tau = 4.9781 \times 10^{-2}$$

$$i(3\tau) = I_0 e^{-3}$$

$$4\tau = 1.8316 \times 10^{-2}$$


When $t = 4\tau$

$$5\tau = 6.7399 \times 10^{-3}$$

$$i(4\tau) = I_0 e^{-4} = I_0 e^{-2}$$

$$6\tau = 2.4788 \times 10^{-3}$$

$$10\tau = 2.445 \times 10^{-3}$$


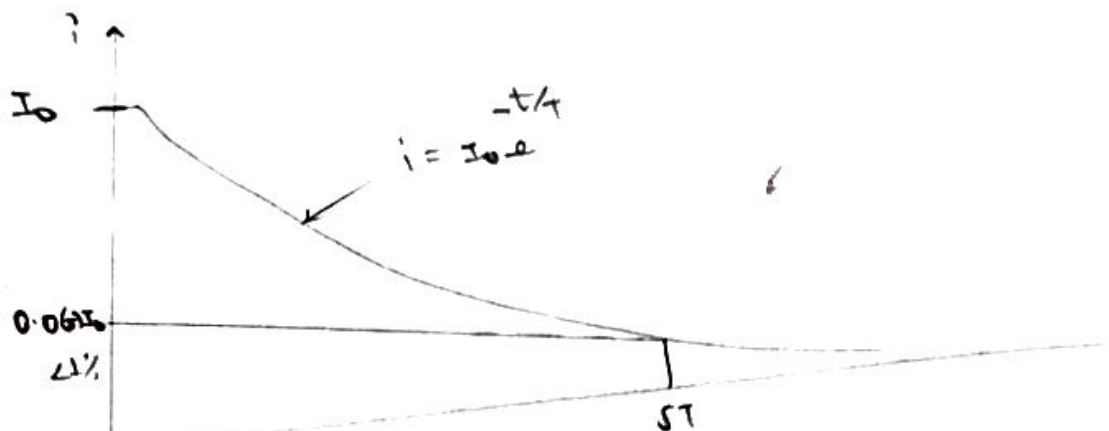


Determining the time constant τ

(1) If the RL circuit can be put as

L - equivalent inductor

R - equivalent resistor

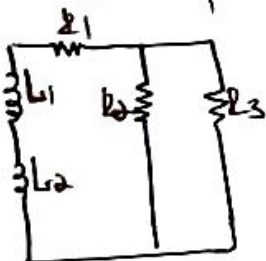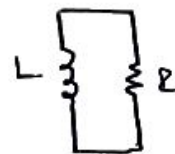

$$\Rightarrow L_{eq} = L_1 + L_2$$



$$R_{eq} = R_1 + (R_2 || R_3)$$

$$\tau = \frac{L_{eq}}{R_{eq}}$$


Steps to calculate the natural response of an RL circuit

#1. Find the initial current, I_0 , through the inductor

#2. Find the time constant of the circuit, $\tau = L/R$

#3. Use $i_L(t) = I_0 e^{-t/\tau}$ to calculate $i_L(t)$

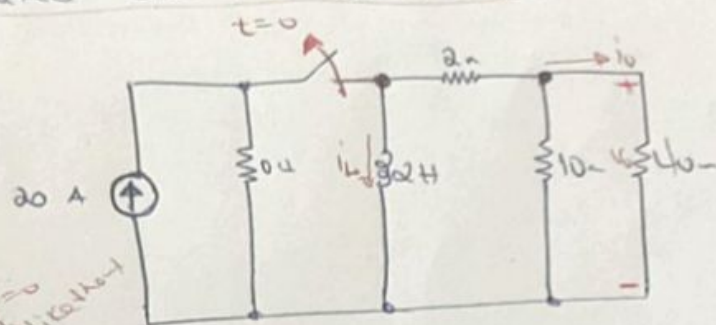Example: The switch has been closed for a long time before it is opened at $t=0$. Find $i_L(t)$, $I_0(t)$, $V_o(t)$, & the percentage of the total energy stored in the 2H inductor that is dissipated in the 10V resistor.



20A

Steady-state condition for $t < 0$
 $V_L = L \frac{di_L}{dt} = 0$
 Inductor as short circuit.

Since the switch has been closed a long period of time, the inductor appears as a short circuit, concluding that the initial current through the inductor is 20A

The equivalent resistance across the terminals of the inductor will be $R_{eq} = 2 + (10 \parallel 40) = 2 + \frac{10 \times 40}{10+40} = 2 + 8 = 10 \Omega$

Time constant $\tau = \frac{L}{R_{eq}} = \frac{2}{10} = 0.2s$

$i_L(t) = I_0 e^{-t/\tau} = 20 e^{-t/0.2} = 20 e^{-5t} A$

$i_L(t) = 20 e^{-5t} A$

Now calculate i_o through 10V resistor

Using a current divider

$i_o(t) = -i_L \left(\frac{10}{10+40} \right) = -20 e^{-5t} \left(\frac{1}{5} \right) = -4 e^{-5t} A$

Using Ohm's law

$$V_o = i_o R \quad \text{but } i_o = -4e^{-5t} \text{ A}$$

$$V_o(t) = (-4e^{-5t})(40)$$

$$V_o(t) = \underline{\underline{-160e^{-5t} \text{ V}}}$$

- ⊗ Find the percentage of the total energy stored in the 2H inductor that is dissipated in the 10Ω resistor

$$V_o(t) = -160e^{-5t} \text{ V}$$

$$P_{\text{diss}}(t) = \frac{V_o^2}{R} = \frac{(-160e^{-5t})^2}{10} = 2560e^{-10t} \text{ W}$$

Total energy dissipated in the 10Ω resistor

$$\begin{aligned} W_{\text{diss}} &= \int_0^{\infty} P \, dt = \int_0^{\infty} 2560e^{-10t} \, dt = \frac{2560e^{-10t}}{-10} \Big|_0^{\infty} \\ &= \frac{2560}{-10} \left(e^{-10(\infty)} - e^{-10(0)} \right) \\ &= \frac{2560}{-10} (0 - 1) \\ &= 256 \text{ J} \end{aligned}$$

- ⊗ Initial energy stored in the 2H inductor

$$W_{\text{ind}} = \frac{1}{2} L i^2(0) = \frac{1}{2} (2) (20)^2 = \underline{\underline{400 \text{ J}}}$$

- ⊗ The percentage of energy dissipated in the 10Ω resistor is

$$\frac{256}{400} \times 100 = 64\%$$