

Fundamental of E.E. Final Exam, 2019

Fundamental of Electrical Engineering (Final Examination)

Part I

1. Define the following terms:

(05pts)

- Resonance
- Power factor correction
- Angular velocity
- Phase difference
- Peak to peak value

14


Part II

1. For the circuit shown in Fig.1, find

(06pts)

- $i(0^+)$ and $v(0^+)$
- $di(0^+)/dt$ and $dv(0^+)/dt$
- $i(\infty)$ and $v(\infty)$

124

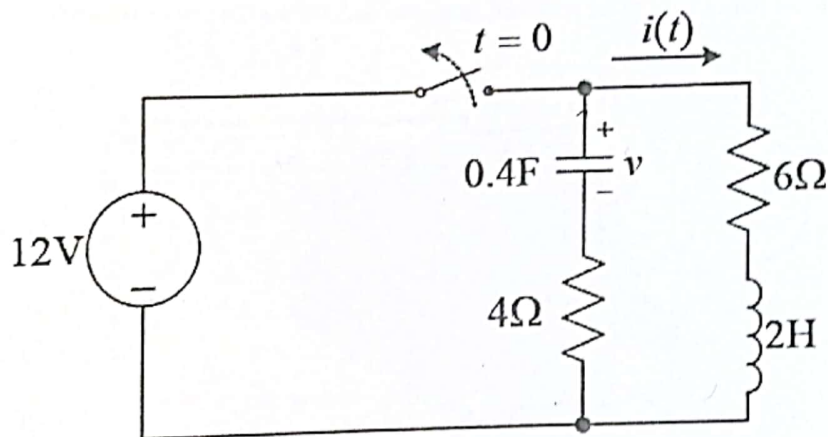

24

Fig.1.

2. An alternating current 'i' is given by; $i(t) = 141.4 \sin(314 t)$. Find

(05pts)

- the maximum value
- frequency
- time period
- the instantaneous value when t is 3ms.
- Phase angle with respect to $i(t)$

1/7

2 314 21
8220

1/7

Fundamental of Electrical Engineering (Final Examination)

3. A 5Ω resistor, 60mH inductor and $10\mu\text{F}$ capacitor are connected in parallel to a 300V , 50Hz

AC supply. Calculate

(8pts)

- the current flowing, I_{am}
- the phase difference between the supply voltage and current,
- the voltage across the circuit elements, V
- draw the phasor and admittance diagram.

4. An R-L-C series Ac circuit consists of resistance 1000Ω , Q-factor of the circuit **10** and the bandwidth of 1000Hz . If a voltage of 100V is applied across the combination. Find

- the resonant frequency f_r
- inductance of the circuit
- capacitance of the circuit
- the half power frequencies

$$P(\omega_0) = \frac{V_{\text{m}}^2}{2R}$$

$$P(\omega_c) = \frac{V_{\text{m}}^2}{4R}$$

(8pts)

5. A 4kVAR , 300-V (peak value), 50-Hz load has a power factor of 0.95 lagging. What value of capacitance have to be removed from the load, where the power factor falls to 0.8 ?

(8pts)

$$\frac{200}{\sqrt{2}}$$

$$B = \omega_1 - \omega_2$$

$$\frac{V}{\sqrt{2}}$$

$$P = \frac{V_{\text{m}}^2}{2R}$$

$$B = \frac{\omega_0}{Q}$$

$$2\pi f = \frac{1}{LC}$$

$$Q = \frac{\omega_0 L}{R}$$

$$V_A = I_A R$$


$$V_{\text{th}} = I_A R$$

$$B_2$$


$$B = 2\pi \times 100$$

$$6.28 \times 100$$

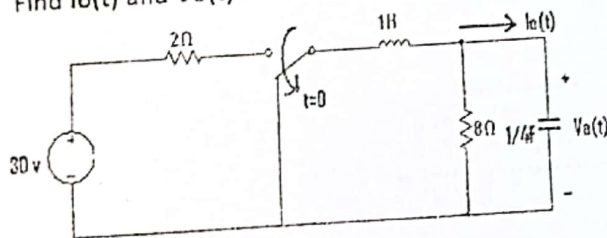1. A 4Ω resistor, 125mH inductor and $10\mu\text{F}$ capacitor are connected in series to a 230V , 50Hz AC supply. Calculate
 - a. The current flowing, (2pts)
 - b. The phase difference between the supply voltage and current, (2pts)
 - c. The voltage across each circuit element, (3pts)
 - d. Draw the phasor and impedance diagram, (4pts)
2. When connected to a 230V (peak), 60-Hz power line, a load absorbs 10 kW at a lagging power factor of 0.8 . Find the value of capacitance necessary to raise the pf to 0.9 . (6pt)
3. A 240-V peak 60Hz supply serves a load that is 20 kW , 25 Kvar (capacitive) and 20 kVAR (inductive). find:
 - a. Apparent power (3pts)
 - b. The current drawn from the supply. (3pts)
 - c. The kVAR rating and capacitance required to improve the power factor to 0.95 lagging. (5pts)
4. Find $i_o(t)$ and $V_o(t)$ for $t > 0$. (7pts)



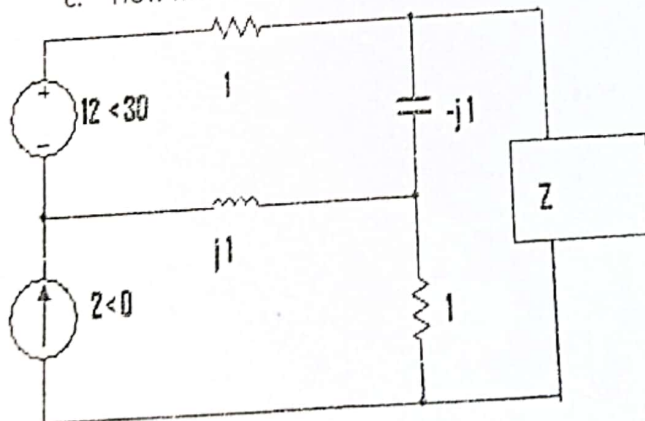5.
 - a. What must be the value of Z for maximum power transfer to it? (4pts)
 - b. What is amount of the average power absorbed by the impedance? (4pts)
 - c. How much is the maximum power? (2pts)



1. A 4Ω resistor, 125mH inductor and $10\mu\text{F}$ capacitor are connected in series to a 230V , 50Hz AC supply. Calculate


- The current flowing, (2pts)
- The phase difference between the supply voltage and current, (2pts)
- The voltage across each circuit element, (3pts)
- Draw the phasor and impedance diagram, (4pts)

2. When connected to a 230V (peak), 60-Hz power line, a load absorbs 10 kW at a lagging power factor of 0.8 . Find the value of capacitance necessary to raise the pf to 0.9 . (6pt)



3. A 240-V peak 60Hz supply serves a load that is 20 kW , 15 Kvar (capacitive) and 20 kVAR (inductive). find:

- Apparent power (3pts)
- The current drawn from the supply (3pts)
- The kVAR rating and capacitance required to improve the power factor to 0.9 lagging (5pts)

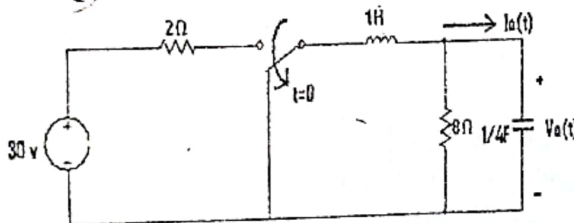4. Find $i(t)$ and $V_o(t)$ for $t > 0$. (7pts)



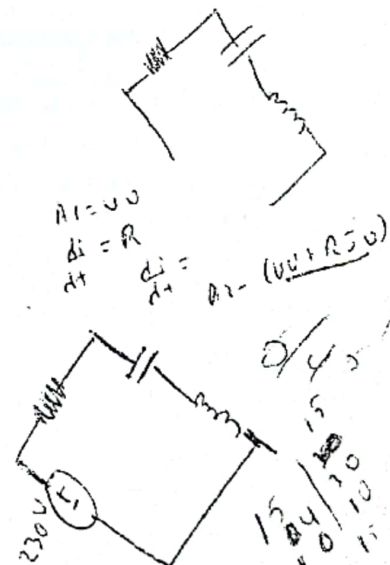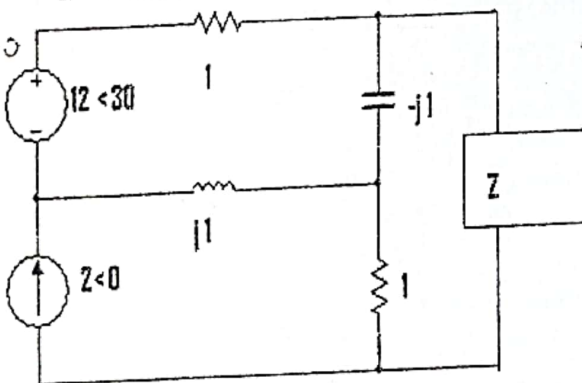- What must be the value of Z for maximum power transfer to it? (4pts)
- What is amount of the average power absorbed by the impedance? (4pts)
- How much is the maximum power? (2pts)



Fundamental of electrical engineering final exam (40%)

1. A certain load has voltage and current variation of a form given by:

$$v(t) = 12\sin(50t + 30^\circ) \text{ V and}$$

$$i(t) = 5\sin(50t - 45^\circ) \text{ A}$$

Find:

- The phase relation between the current and voltage.
- The instantaneous power at $t=1\text{sec}$.
- The average power consumed by the load.

(6 points)


$$v(t) = 12\sin(50t + 30^\circ) \text{ V}$$

$$i(t) = 5\sin(50t - 45^\circ) \text{ A}$$

$$P = VI \cos \phi = 12 \times 5 \cos 75^\circ = 6 \text{ W}$$

2. A 600V, 300KVA small electrical utility supplies a factory with the power triangle shown in the figure here under.

(6 points)

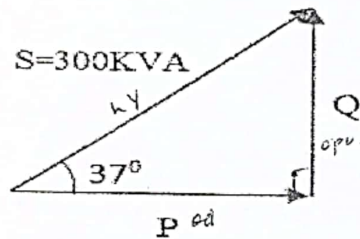


Determine:

- Total reactive power and real (true) power.
- Total current.

$$P = 300 \cos 37^\circ$$

$$Q = 300 \sin 37^\circ$$

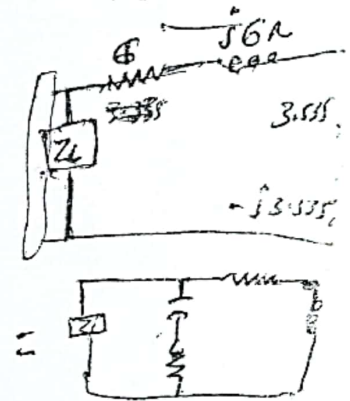

3. Referring to figure 1 determine:

$$I = 1.2 \text{ V}$$

(12 points)

- Total impedance seen by the source (Z_T).
- Total current supplied by the source (I_T).
- The output voltage (V_o).
- Draw the phasor diagram and impedance diagram.

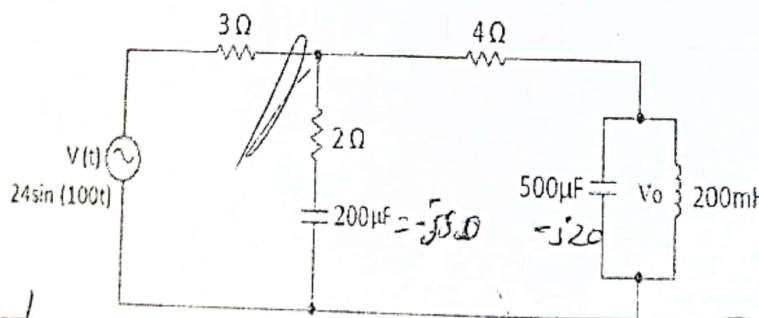


Fig 1

$$200 \times 100 \times 10^{-6}$$

$$= 2 \times 10^{-2} = \frac{100}{5} = 20$$

$$-j30 + 4$$

$$= \frac{500 \times 100 \times 10^{-6}}{5} = \frac{100}{5} = 20$$

$$\frac{3.04}{2.12} = \frac{608}{608} = 1$$

4. Referring to fig 2 Determine:

(6 points)

- The value of Z_L to transfer maximum power to the load.
- Maximum power transfer to the load under this condition.

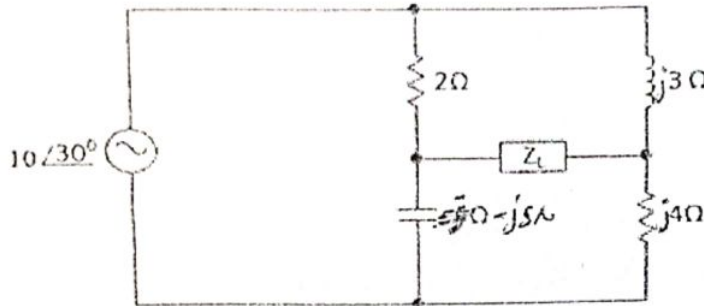


Fig. 2

5. Referring to figure 3 determine $V_C(t)$ for $t > 0$ and draw the response graph (use the appropriate method).

(10 points)

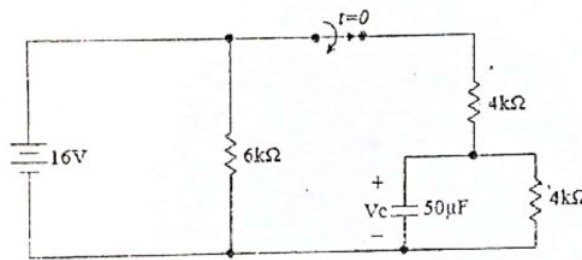


Fig.3

$R_{TH} = 2k\Omega$

$$\tau = R_{TH} C = 2k\Omega \times 50\mu F = 0.1s$$

Bonus question

6. Referring to figure 4 find $i(t)$ for $t > 0$

(5 points)

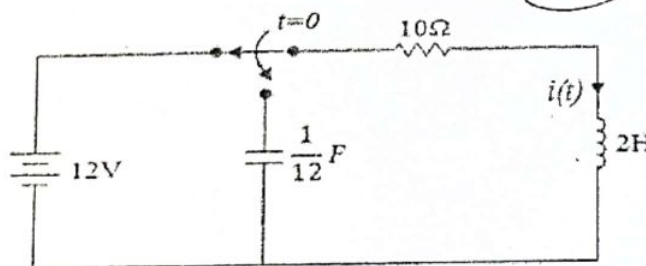


Fig 4


Step 1

from previous answer:
 $K_1 = V_C(\infty) = 8V$
 $K_2 = V_C(0^+) - V_C(0^-) = 8V - 0 = 8V$
 $V_C(t) = 8e^{-t/\tau}$


7
 $V(t)$ for $t > 0$

Step 1
 $V_C(t) = K_1 + K_2 e^{-t/\tau}$

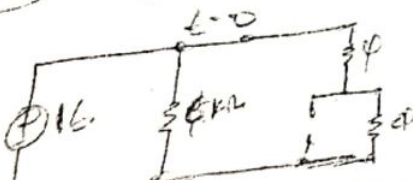at $t=0$ - at steady state $t \rightarrow \infty$



Step 3

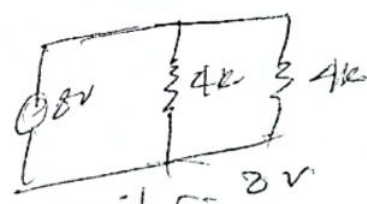

$V_C(0^+) = V_C(0^-) = 8V$
 Step 4 $V_C(\infty) = 0$

(5)