

①


Tutorial problems

Chapter #3.

- ① An Input Voltage of 2 V_{rms} [Measured from base to ground] is applied to the circuit below. Assuming that the emitter voltage follows the base Voltage exactly and that $V_{\text{BE}} (\text{rms}) = 0.1\text{ V}$, calculate the circuit voltage amplification [$A_v = V_o/v_i$] and Emitter current for $R_E = 1\text{ k}\Omega$ to find

$$A_v = ?$$

$$I_E = ?$$

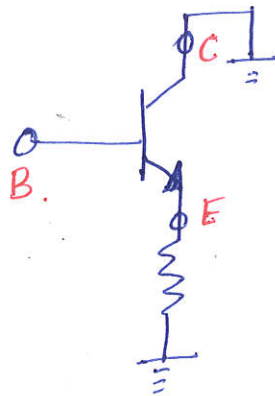

Solutions

Using KVL

$$V_B - V_{\text{BE}} - V_E = 0$$

$$2 - 0.1 - I_E R_E = 0$$

$$I_E = 1.9 / 1000 = 1.9\text{ mA}$$

$$V_E = I_E R_E$$


$$V_E = [1.9\text{ mA}] [1000]$$

$$V_E = 1.9\text{ V}$$

$$V_o = V_E$$

$$A_v = \alpha = 1.9 / 2 = 0.95$$

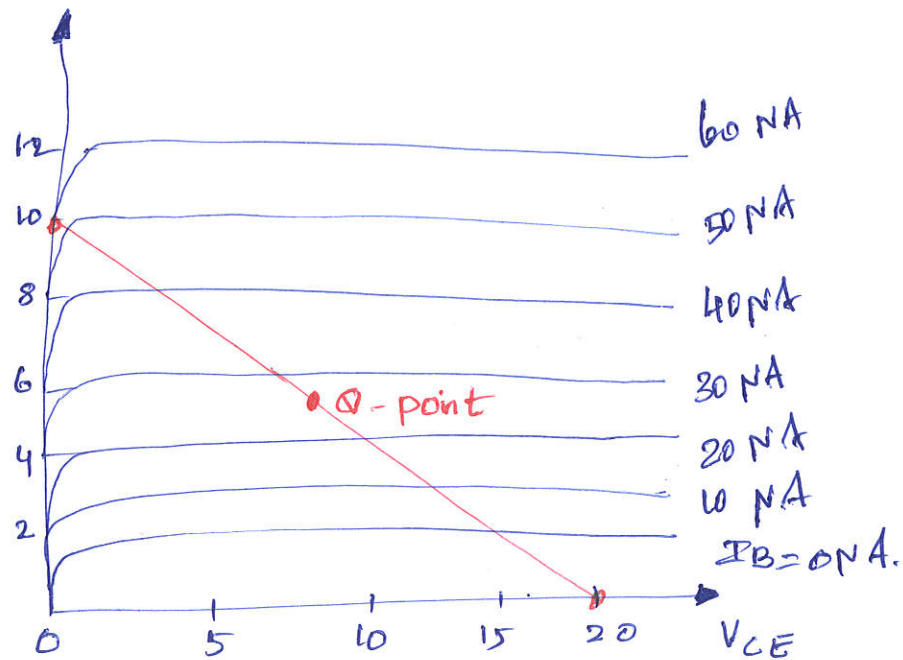② Given the load line below and the defined Q-point, determine the Required values of V_{CC} , R_C , and R_B for a fixed bias configurations.



from above load characteristics.

$$V_{CE} = V_{CC} = 20V \text{ at } I_C = 0mA$$

$$I_C = \frac{V_{CC}}{R_C} \text{ at } V_{CE} = 0V$$

$$R_C = \frac{V_{CC}}{I_C} = \frac{20V}{10mA} = 2k\Omega$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{20V - 0.7V}{25\mu A} = 772k\Omega$$

Solutions


$$V_{CC} = 20V$$

$$R_C = 2k\Omega$$

$$R_B = 772k\Omega$$

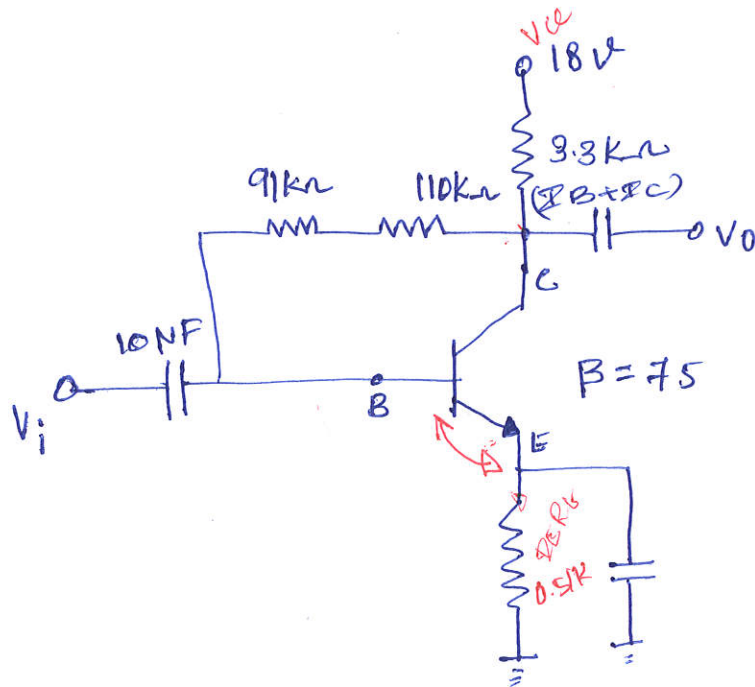(2)

③ Determine the d.c. level of I_B and V_C for the network in figure below.



Solutions

In this case, the base Resistance for the d.c analysis is composed of two resistors with a capacitors connected from their Ins to ground. the capacitors assumes the open circuit equivalence and $R_B = R_1 + R_2$.

Solving for I_B .

from K.V.L.

$$V_{CC} - 3.3k\Omega (I_B + I_C) - I_B (R_1 + R_2) - V_{BE} - I_E R_E = 0.$$

$$-V_{BE} - I_E R_E = 0.$$

But

$$I_E = I_B + I_C$$

$$I_C = \beta I_B$$

$$R_B = R_1 + R_2$$

Thus,

$$\rightarrow V_{CC} - 3.3k\Omega (I_B + \beta I_B) - I_B \underbrace{(R_1 + R_2)}_{R_B} - V_{BE} - \underbrace{(I_B + I_C)}_{I_E} R_E = 0$$

$$\rightarrow V_{CC} - 3.3k\Omega (I_B + \beta I_B) - I_B R_B - V_{BE} - (I_B + \beta I_B) R_E = 0$$

$$\rightarrow V_{CC} - 3.3k\Omega I_B (1 + \beta) - I_B R_B - V_{BE} - I_B (1 + \beta) R_E = 0$$

Simplifying,

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta) (3.3k\Omega + R_E)}$$

$$\beta = 75$$

$$I_B = \frac{18 - 0.7}{[91k\Omega + 110k\Omega] + [1 + \beta] [3.3k\Omega + 0.51k\Omega]}$$

$$I_B = \frac{17.3V}{490.56k\Omega} = 35.266 \mu A$$

$$I_B = 35.266 \mu A$$

Thus

$$I_C = \beta I_B$$

$$I_C = [75] [35.266 \text{ nA}]$$

$$I_C = 2.645 \text{ mA}$$

Solving for V_C .

from K.V.L.

$$V_C = 18 - 3.3 \text{ k}\Omega (I_B + I_C)$$

$$V_C = 18 - 3.3 \text{ k}\Omega (2.645 \text{ mA} + 35.266 \text{ nA})$$

$$V_C = 18 - 3.3 \text{ k}\Omega [2.68 \text{ mA}]$$


$$V_C = 18 - 8.845$$

$$V_C = 9.155 \text{ V}$$

4. for the network of figure below.

a) Determine I_{CQ} and V_{CEQ}

b) find V_B , V_C , V_E , and V_{BC} ,

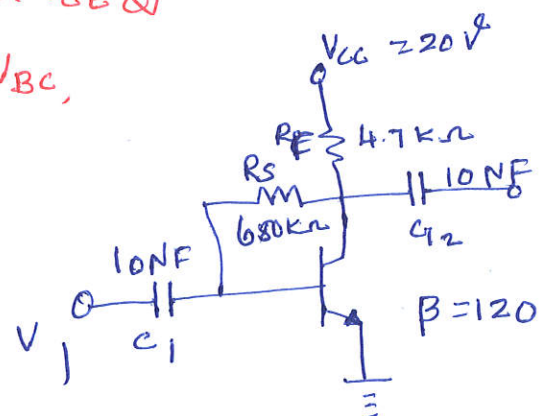

The absence of R_E reduce the reflection of resistive levels to simply that of R_C and equation for I_B reduce to.

Using KVL

$$V_{CC} - [I_B + I_C] R_C - I_B R_B - V_{BE} = 0$$

And

$$I_C = \beta I_B$$

$$\begin{aligned} 1 + \beta &= 120 + 1 \\ &= 121 \end{aligned}$$

$$20 - [I_B + \beta I_B] 4.7k\Omega - I_B [680k\Omega] - 0.7 = 0$$

$$I_B = \frac{19.3}{121 [4.7k\Omega] + 680k\Omega}$$

$$I_B = 15.456 \text{ NA}$$

$$I_{CQ} = \beta I_B$$

$$I_{CQ} = 120 [15.456 \text{ NA}]$$

$$I_{CQ} = 1.85 \text{ mA.}$$

$$V_{CEQ} = 20 - [I_{CQ} + I_B] [4.7]$$

$$V_{CEQ} = 20 - [1.85 \text{ mA} + I_E] [4.7 \text{ k}\Omega]$$

$$V_{CEQ} = 20 - [1.85 \text{ mA} + 15.456 \text{ nA}] [4.7 \text{ k}\Omega]$$

$$V_{CEQ} = 11.23 \text{ V}$$

Solving Base Voltage using KVL.

$$V_B - V_{BE} = 0$$

$$V_B = 0.7 \text{ V}$$

$$V_C = V_{CEQ} = 11.23 \text{ V}$$

$$V_E = 0$$

$$V_{BC} = V_B - V_C$$

$$V_{BC} = 0.7 - 11.23$$

$$V_{BC} = -10.53 \text{ V}$$

Solutions.


$$I_B = 15.456 \text{ nA}$$

$$V_{CEQ} = 11.23 \text{ V}$$

$$V_C = 11.23 \text{ V}$$

$$V_{BC} = -10.53 \text{ V}$$

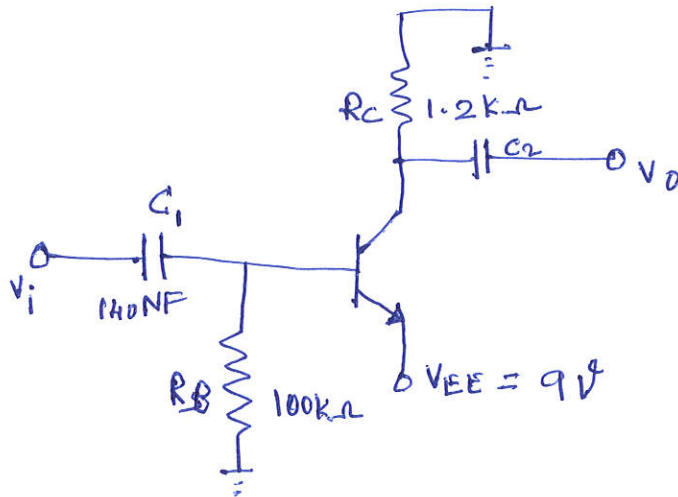- ⑤ Determine V_C and V_B for the network of figure below.



$$-I_B R_B - V_{BE} + V_{EE} = 0$$

$$I_B = \frac{V_{EE} - V_{BE}}{R_B}$$

$$I_B = \frac{9V - 0.7V}{100k\Omega}$$

$$= \frac{8.3V}{100k\Omega}$$

$$I_B = 83\mu A$$

$$I_C = \beta I_B$$

$$= [15] [83\mu A]$$

$$I_C = 1.245\text{ mA}$$

$$V_C = -I_C R_C$$

$$= -[3.735 \text{ mA}][1.2 \text{ k}\Omega]$$



$$V_C = -4.48 \text{ V}$$

$$V_B = -I_B R_B$$

$$= -[83 \text{ }\mu\text{A}][100 \text{ k}\Omega]$$

$$V_B = -8.3 \text{ V}$$

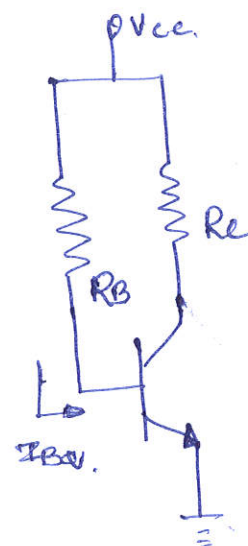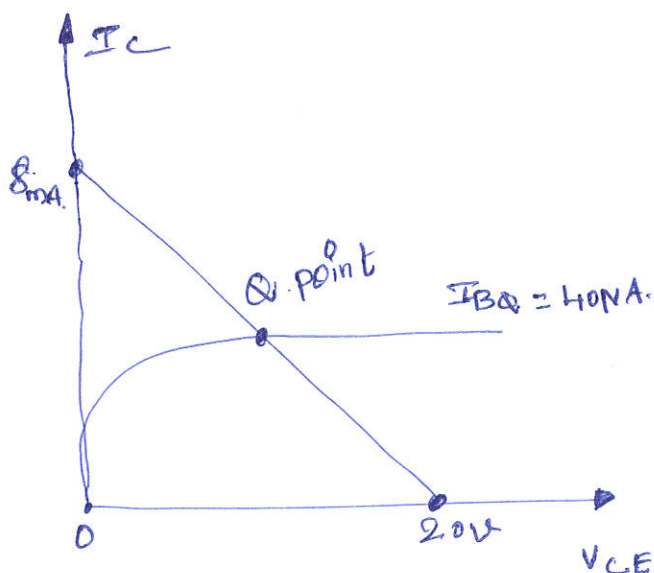6] Given the device characteristics and the fixed bias configuration from the figure below, determine V_{CC} , R_B , and R_C .



$V_{CC} = 20V$ from the load line

$$I_C = \frac{V_{CC}}{R_C} \quad \left| \quad V_{CE} = 0V \right.$$

$$R_C = \frac{V_{CC}}{I_C} = \frac{20V}{8mA} = 2.5K\Omega$$

WKT

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_B}$$

$$R_B = \frac{20V - 0.7V}{40\mu A}$$

$$R_B = \frac{19.3V}{40\mu A}$$

$R_B = 482.5K\Omega$

AL.

7) Given $\beta = 120$ and $I_E = 3.2 \text{ mA}$ for a Common-Emitter Configuration with $r_o = \infty$, determine

a) Z_i

b) A_v if a Load of $2 \text{ k}\Omega$ is applied

c) A_i with the $2 \text{ k}\Omega$ load.

a).
$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{3.2 \text{ mA}} = 8.125 \Omega$$

and $Z_i = \beta r_e = [120][8.125 \Omega]$

$$Z_i = 975 \Omega$$

b)
$$A_v = \frac{-R_L}{r_e}$$


$$= \frac{-2 \text{ k}\Omega}{8.125 \Omega}$$

$$A_v = -246.15$$

c)
$$A_i = \frac{I_o}{I_i} = \beta = 120.$$

$$A_i = 120$$

8) For given ckt. determine.

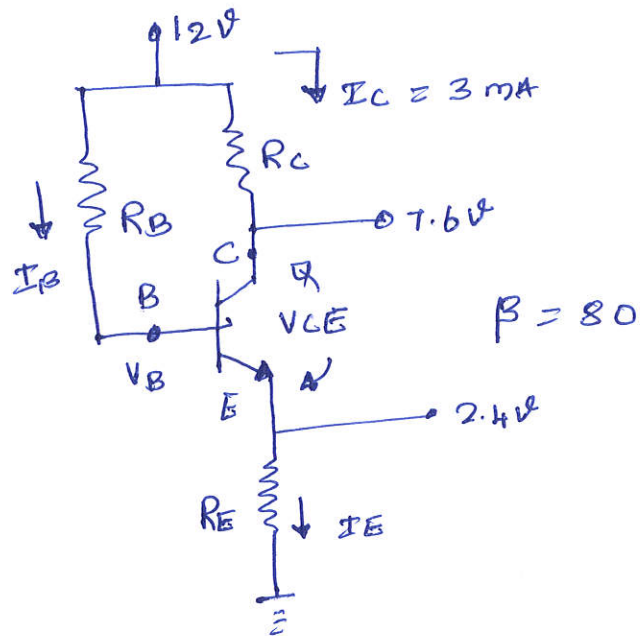

determine

- a) R_C b) R_E c) R_B d) V_{CE} e) V_B

Given

$$I_C = 3\text{mA}$$

$$V_C = 7.6\text{V}$$

$$V_E = 2.4\text{V}$$

$$\beta = 80$$

$$V_{CC} = 12\text{V}$$

Solutions

e) $V_B = ?$

$$V_{BE} = 0.7V \quad [Si]$$

$$V_B - V_E = 0.7V$$

$$V_B = 2.4V + 0.7V$$

$$V_B = 3.1V$$

d) V_{CE}

$$V_{CE} = V_C - V_E$$

$$= 7.6V - 2.4V$$

$$V_{CE} = 5.2V$$

c) R_B

Apply KVL in Input loop

$$V_{CC} - I_B R_B = V_B$$

$$+12V - I_B R_B = V_B$$

$$+12V - I_B R_B = 3.1V$$

$$I_B = \frac{I_C}{\beta}$$

$$= \frac{3 \text{ mA}}{80}$$

$$I_B = 37.5 \mu\text{A}$$

$$R_B = \frac{12\text{V} - 3.1\text{V}}{37.5 \mu\text{A}}$$

$$R_B = \frac{12\text{V} - 3.1\text{V}}{37.5 \mu\text{A}}$$

$$R_B = 237.4 \text{ k}\Omega$$

b] R_E


Apply KVL in R_E loop

$$2.4\text{V} - I_E R_E = 0\text{V}$$

$$\therefore I_E = I_C$$

$$\frac{2.4\text{V}}{3 \text{ mA}} = R_E$$

$$R_E = 0.8 \text{ k}\Omega$$

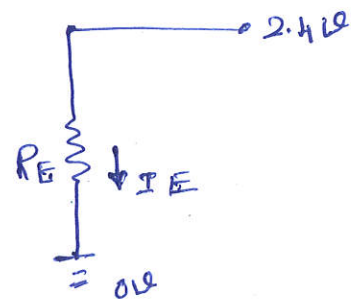


a) R_C


$$12V - I_C R_C = 7.6V$$

$$R_C = \frac{12V - 7.6V}{3mA}$$

$$R_C = 1.47 k\Omega$$

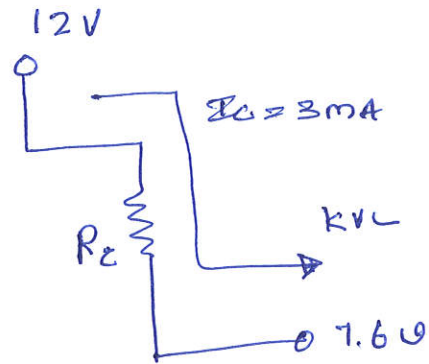

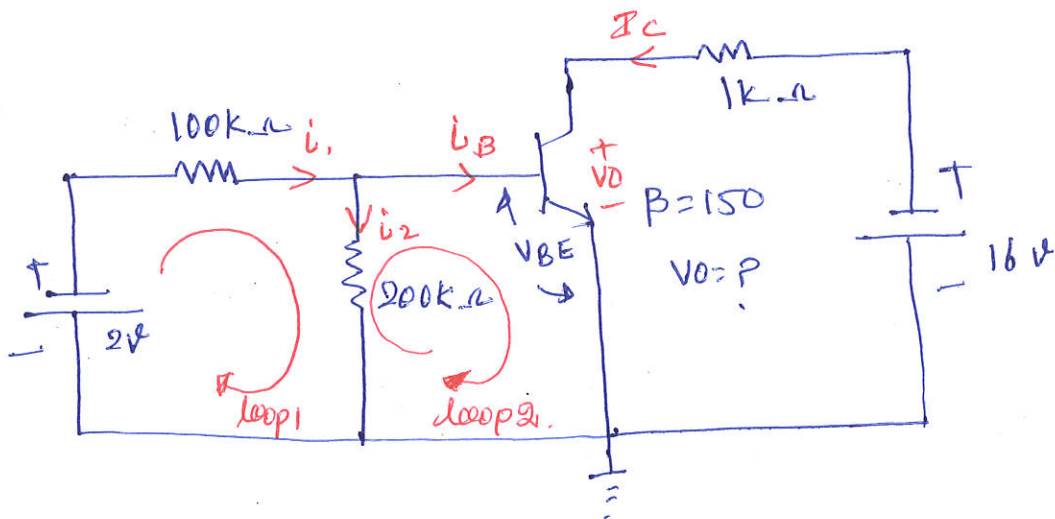9] Analysis given circuit. Find $V_O = ?$



Given

$$\beta = 150$$

$$V_{BE} = 0.7V$$

Relations.

$$I_C = \alpha I_E$$

$$I_C = \beta I_B$$

$$I_E = [1 + \beta] I_B$$

1) KCL $i_1 = i_2 + I_B$

② KCL $\rightarrow i_1(100k) + i_2(200k) - 2V = 0 \rightarrow \text{Loop 1}$

$$-i_2(200k) + V_{BE} = 0 \quad \text{loop 2}$$

$$V_{BE} = i_2(200k)$$

$$\frac{V_{BE}}{200k} = i_2$$

$$i_2 = \frac{0.7}{200k}$$

$$i_2 = 3.5 \mu A$$

Now Sub i_2 value in loop 1

$$i_1(100k) + 3.5 \mu A(200k) - 2V = 0$$

$$i_1(100k) = \frac{2 - (3.5 \mu A)(200k)}{100k}$$

$$i_1 = \frac{2 - (3.5 \mu A)(200k)}{100k}$$

$$i_1 = 13 \mu A$$

③ Now Apply i_1 & i_2 value in KCL equation.

$$i_1 = i_2 + I_B$$

$$13 \mu A = 3.5 \mu A + I_B$$

$$I_B = 9.5 \mu A$$

$$I_B = 13 \mu A - 3.5 \mu A$$

(9)

Now we find $I_C = ?$

$$I_C = \beta I_B$$

$$I_C = 150 \times 9.5 \text{ nA}$$

$$I_C = 0.001425$$

Now we find V_0 using ohms law.


$$16 - V_0 = (0.001425)(1\text{k})$$

$$V_0 = 16 - (0.001425)(1\text{k})$$

$$V_0 = 14.575 \text{ V}$$

⑩ Determine and Analysis

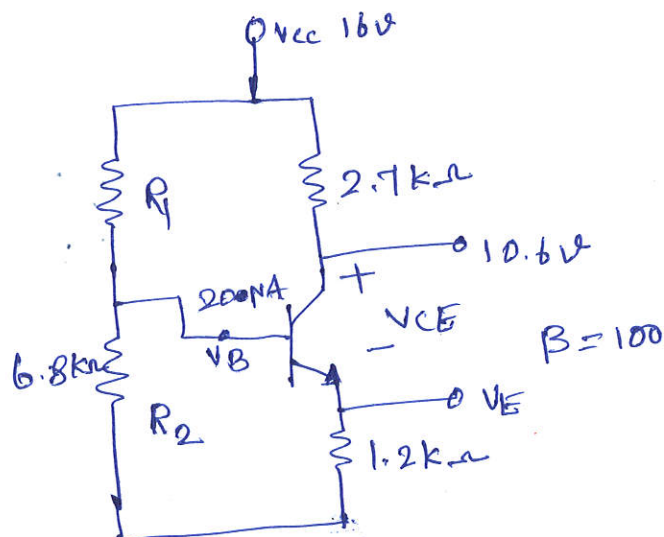a) I_C b) V_E c) V_{CC} d) V_{CE} e) V_B f) R_1




Given

$$I_B = 20 \text{ nA}, V_C = 10.6 \text{ V}, R_C = 2.7 \text{ k}\Omega, R_2 = 6.8 \text{ k}\Omega$$

$$R_C = 2.7 \text{ k}\Omega, B = 100, R_E = 1.2 \text{ k}\Omega$$

Solutions

Now we can draw Thevenin equivalent ckt

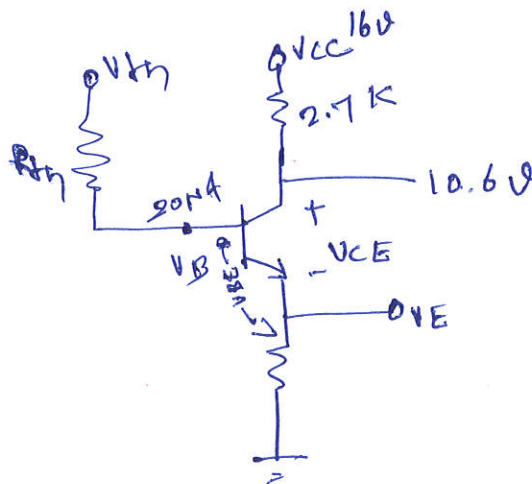

$$V_{th} = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2}$$

a) $I_C = ?$

$$I_C = \beta I_B$$

$$I_C = 100 \times 20 \text{ nA}$$


$$I_C = 2 \text{ mA}$$

c) $V_{CC} = ?$

$$V_{CC} - I_C R_C = 10.6 \text{ V}$$

$$V_{CC} = 10.6 + (2 \text{ mA})(2.7 \text{ k}\Omega)$$

$$V_{CC} = 16 \text{ V}$$

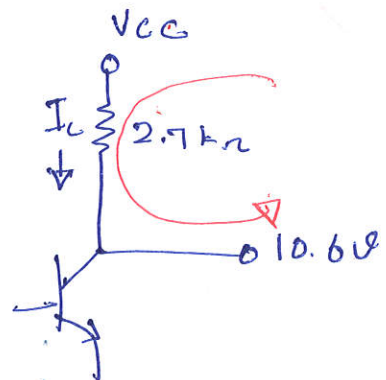

$$b) V_E = ?$$

WKT

$$I_E = I_C + I_B$$

I_B is very small


$\therefore$

$$I_E \approx I_C$$

$$I_E = 2\text{mA} + 20\text{NA}$$

$$= 2\text{mA} + 0.02\text{mA}$$
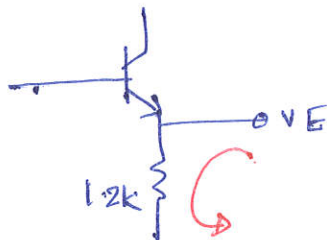
$$I_E = 2.02\text{mA} \rightarrow \text{Reason } I_E \approx I_C$$



$$V_E - I_E R_E = 0$$

$$V_E = I_E R_E$$

$$V_E = (2.02\text{mA})(1.2\text{k}\Omega)$$

$$V_E = 2.424\text{V}$$

$$d) V_{CE} = ?$$

$$V_{CE} = V_C - V_E$$

$$V_{CE} = 10.6\text{V} - 2.424\text{V}$$

$$V_{CE} = 8.176\text{V}$$

$$e) V_B = ?$$

$$V_{BE} = V_B - V_E$$

$$0.7 = V_B - 2.424 \text{ V}$$

$$V_B = 3.124 \text{ V}$$

$$f) R_1 = ?$$

→ potential point

$$V_{th} = V_B$$


$$V_{th} = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$V_{th} = \frac{16 \times 6.8}{R_1 + 6.8 \text{ k}\Omega}$$

$$V_{th} = V_B$$

$$3.12 \text{ V} = \frac{16 \times 6.8}{R_1 + 6.8 \text{ k}\Omega}$$

$$R_1 = 28 \text{ k}\Omega$$

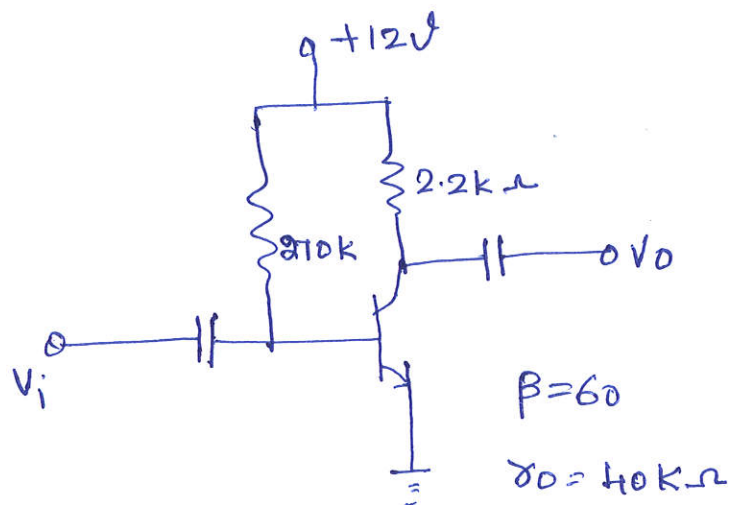

for the network shown,

- i) Determine Z_i and Z_o
- ii) Determine Voltage gain
- iii) Determine Current gain.

Solutions

$$R_B = 270\text{ k}\Omega$$


$$\beta = 60$$

$$R_C = 2.2\text{ k}\Omega$$

$$r_o = 40\text{ k}\Omega$$

$$r_e = \frac{26\text{ mV}}{I_E}$$

D.c. equivalent circuit.

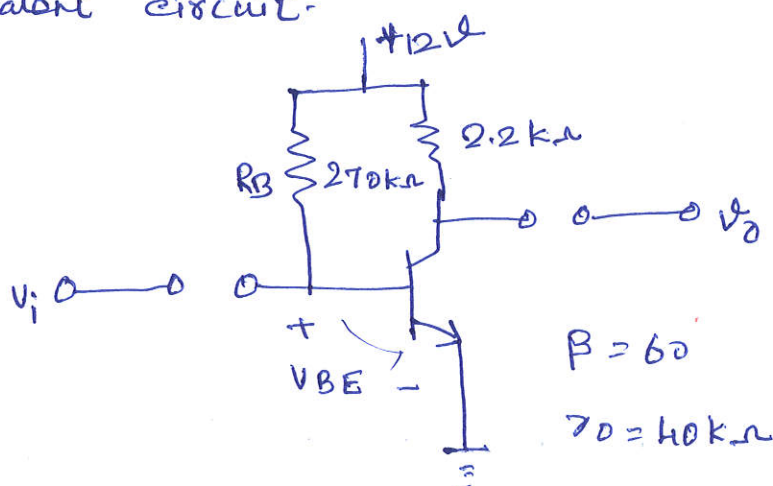

an applying K.V.L $\rightarrow$ Input loop

$$-12\text{ V} - I_B R_B + V_{BE} = 0\text{ V}$$

$$I_B = \frac{12V - 0.7V}{270k\Omega}$$

$$I_B = 0.04185mA = 41.85\mu A.$$

Calculate I_E .

$$I_E = I_C + I_B$$

$$= \beta I_B + I_B = [\beta + 1] I_B$$

$$I_E = 61 \times 41.85\mu A$$


$$I_E = 2552.85\mu A = 2.553mA.$$

$$r_e = ?$$

$$r_e = \frac{26mV}{2.553mA.}$$

$$r_e = 10.18\Omega$$

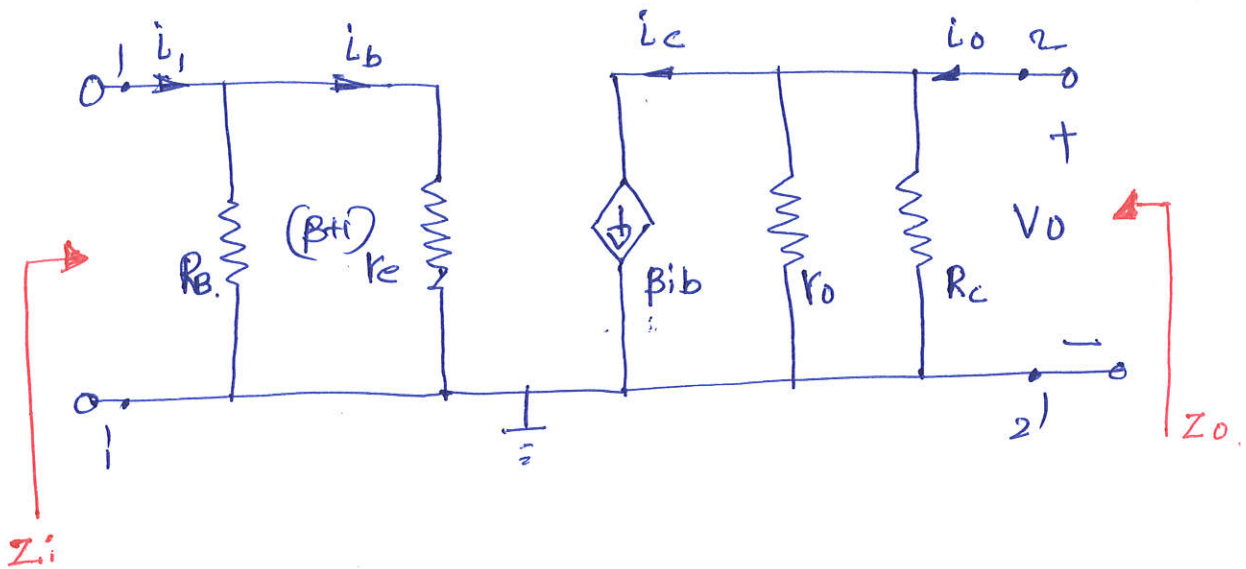to find Z_i and Z_o to obtain A.C. equivalent circuit:



Z_i

$$Z_i = R_B \parallel (\beta+1)r_e$$

$$(\beta+1)r_e = 0.621 \text{ k}\Omega$$

$$= \frac{R_B \cdot (\beta+1)r_e}{R_B + (\beta+1)r_e}$$

$$Z_i = \frac{(270 \text{ k}\Omega)(0.621 \text{ k}\Omega)}{270 \text{ k}\Omega + 0.621 \text{ k}\Omega}$$

$$R_B \geq 10(\beta+1)r_e$$

$$Z_i = (\beta+1)r_e$$

$$Z_i = 0.621 \text{ k}\Omega$$

$$= 0.6195 \text{ k}\Omega$$

$$Z_i = 619.5 \Omega$$

$$Z_i = 621 \Omega$$

Z_o

$$Z_o = r_o \parallel R_C$$

$$Z_o = 40 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega$$

$$Z_o = 2.085 \text{ k}\Omega$$

$$A_v = \frac{V_o}{V_i} = \frac{-\cancel{\beta} \cancel{i_b} R_c}{\cancel{i_b} (\cancel{\beta} + 1) r_e}$$

$$\beta + 1 \approx \beta$$



$$A_v = \frac{-R_c}{r_e} = \frac{-2.2 \text{ k}\Omega}{10.18 \Omega}$$

$$A_v = -216.1$$

$$A_i = \frac{I_o}{I_i} = 60$$

current gain $A_i = \beta = 60$.

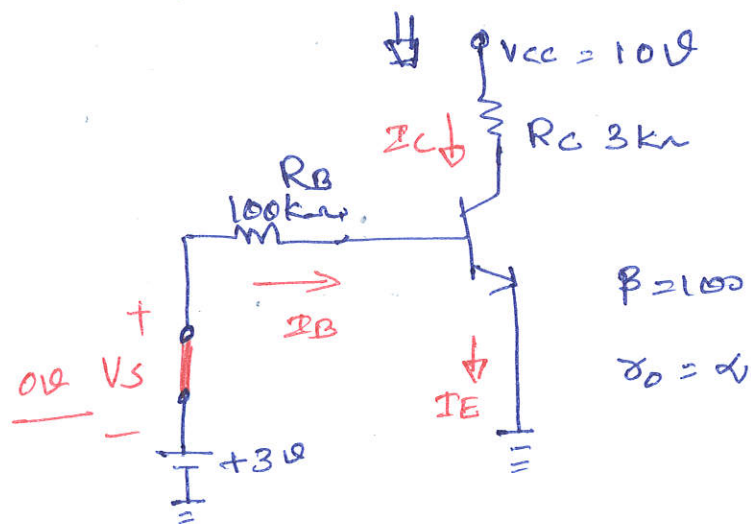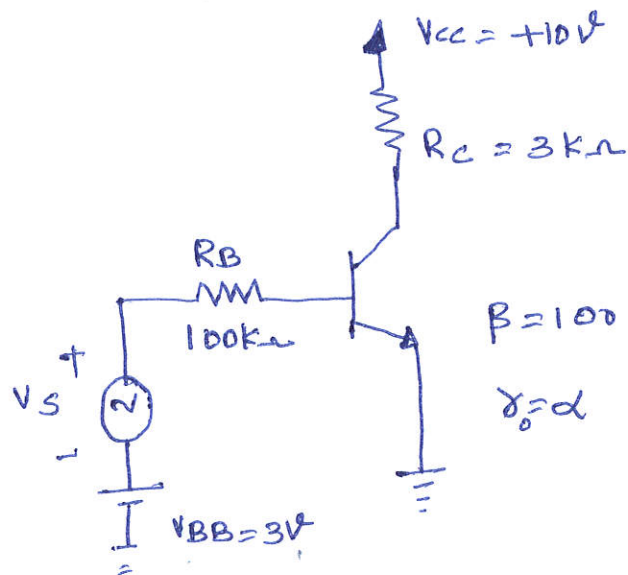11) Determine the voltage gain of the amplifier shown in figure,



Apply KVL Input Side.

$$V_{BE} = 0.7V$$

$$0V + 3V - (100k)I_B - V_{BE} = 0$$

$$I_B = \frac{3V - 0.7V}{100k}$$

$$I_B = 0.023mA \text{ or } \underline{\underline{23\mu A}}$$

$$I_C = \beta I_B$$

$$I_C = 23 \text{ nA} \times 100$$

$$I_C = 2.3 \text{ mA}$$


For network shown in figure.

a) Determine r_c

b) calculate Z_i and Z_o

c) find A_v

d) find A_i .

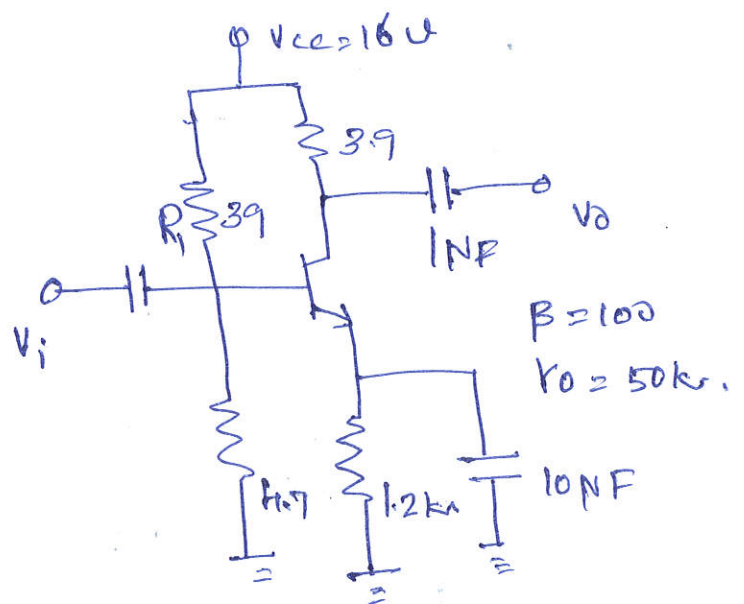

Solutions

$$r_c = \frac{26 \text{ mV}}{I_E}$$

$$R_1 = 39 \text{ k}, R_2 = 4.7 \text{ k}, R_C = 3.9 \text{ k}, R_E = 1.2 \text{ k}$$

$$V_{CC} = 16 \text{ V}, C_1 = 1 \text{ nF}, C_2 = 1 \text{ nF}, C_3 = 10 \text{ nF}, \beta = 100$$


$$R_L = 50 \text{ k}\Omega$$

Find $\gamma_{ce} = ?$


14.

We need to find I_E

D.C. equivalent ckt

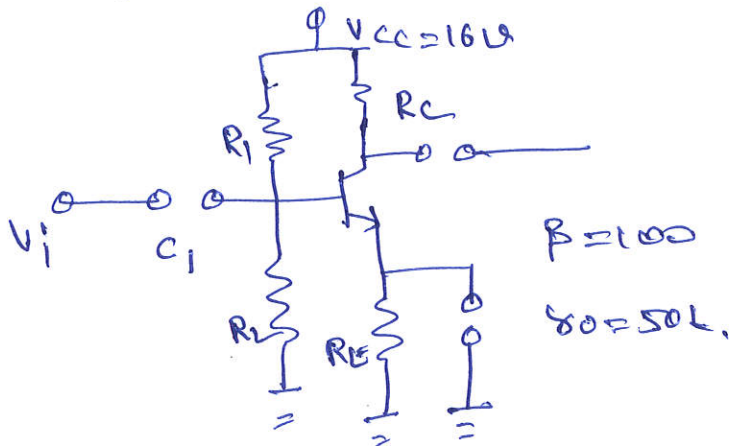

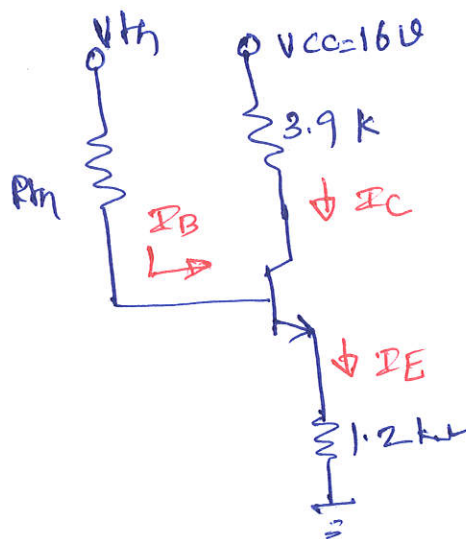voltage divider bias $\rightarrow V_{th}$ ckt



$$V_{th} = \frac{R_2 \cdot V_{CC}}{R_1 + R_2}$$

$$R_{th} = R_1 \parallel R_2$$

$$V_{th} = \frac{4.7k \times 16V}{39k + 4.7k} = 1.72V$$

$$V_{th} = 1.72V$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = 4.194k\Omega$$

Apply KVL in Input loop

$$V_{th} - I_B R_{th} - V_{BE} - \overset{(B+1)I_B}{I_E (1.2k)} = 0$$

WKT

$$I_E = I_B + I_C$$

$$I_C = \beta I_B$$

$$I_E = (\beta + 1) I_B$$

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1)(1.2k)}$$

$$I_B = \frac{1.72V - 0.7V}{4.194_{k\Omega} + (101)(1.2k\Omega)}$$

$$I_B = 8.13 \mu A$$

$$\underline{I_C = \beta I_B}$$

$$I_C = \beta I_B$$

$$I_C = 100 \times 8.13 \mu A$$

$$I_C = 813.4 \mu A$$

$$I_E = 8.13 \mu A + 813.4 \mu A$$

$$I_E = 0.821 \text{ mA}$$


$$r_e = \frac{26 \text{ mV}}{I_E}$$

$$r_e = \frac{26 \text{ mV}}{0.82 \text{ mA}}$$

$$r_e = 31.6 \Omega$$

to the calculation Z_i and Z_o we need AC equivalent circuit. becoz $X_C \approx 0 \Omega$


A.C. equivalent ckt.

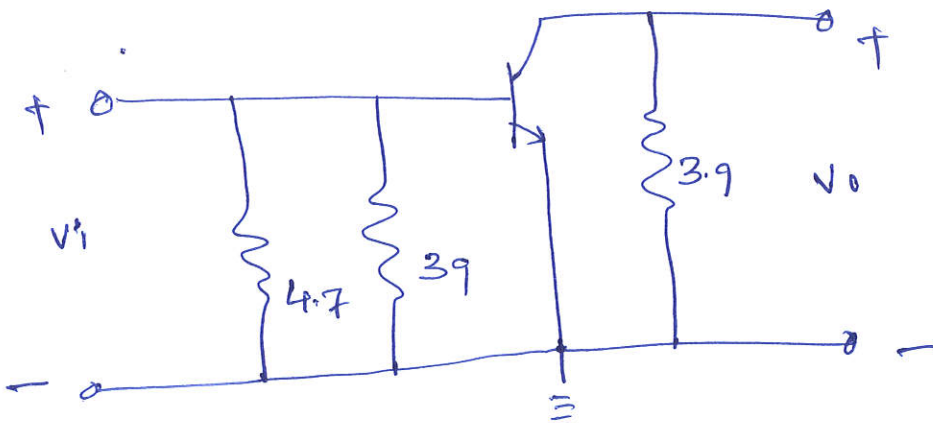

→ r_e model

$$R' = 4.7 \parallel 39$$

$$R' = 4.19 \text{ k}\Omega = R_{th}$$

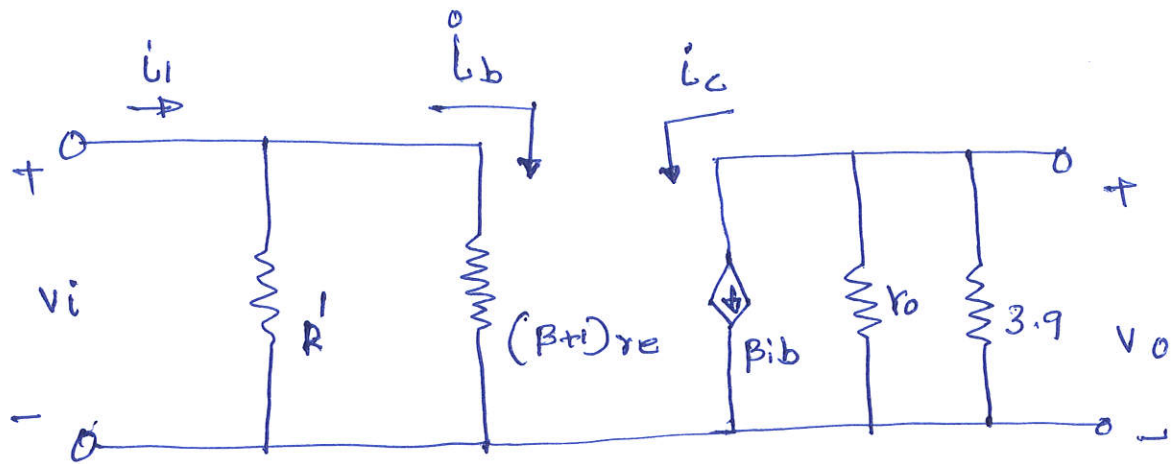

$$Z_i = R' \parallel [(\beta+1)r_e] = \frac{R' [(\beta+1)r_e]}{R' + [(\beta+1)r_e]} = 1.811 \text{ k}\Omega$$

$$[(\beta+1)r_e] = 3.9 \text{ k}\Omega$$

$$Z_o = r_o \parallel 3.9$$

$$r_o = 50 \text{ k}\Omega$$

HW

c) \$A_v\$

d) \$A_i\$

$$A_i = \frac{o/p_i}{I/p_i}$$

$$A_v = \frac{R_c}{R_E} = \frac{R_c}{r_e} = \frac{3.9}{31.6} = 0.123$$

$$A_i = \beta =$$

JFET solved problems.

① The device parameters for n-channel JFET are

* Maximum drain current $[I_{DSS}] = 10 \text{ mA}$.

* Pinch-off Voltage $[V_P] = -4 \text{ V}$

Calculate the drain current for.

a) $V_{GS} = 0 \text{ V}$ b) $V_{GS} = -1 \text{ V}$ c) $V_{GS} = -4 \text{ V}$.

Solutions.

$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2$$

Case a] $V_{GS} = 0 \text{ V}$ d $V_{DS} > |V_P|$

$$I_D = I_{DSS}$$


$$I_D = 10 \text{ mA}$$

Case c:

$$V_{GS} = -4 \text{ V}$$

$$V_P = -4 \text{ V} = I_D = 0$$

$$I_D = 0 \text{ A}$$

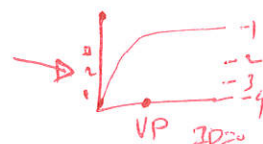

Case b]

$$V_{GS} = -1 \text{ V}$$

$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2$$

$$= 10 \text{ mA} \left[1 - \left[\frac{-1}{-4} \right] \right]^2 = 10 \text{ mA} [1 - 0.25]^2$$

$$I_D = 5.625 \text{ mA}$$

② The reverse gate voltage of JFET when changes from 4.4V to 4.2V, the drain current changes from 2.2 mA to 2.6 mA, find out the value of transconductance.

Solution

$$g_m = \frac{O/P_i}{I/P_V} \quad \left| \text{for constant } O/P_V \right.$$

$$g_m = \frac{\text{Change in output } i}{\text{Change in input } V} \quad \left| \text{constant } O/P_V \right.$$

ΔI_D ΔV_{GS}

$$\Delta V_{GS} = 4.4V - 4.2V$$

$$= 0.2V$$

$$\Delta I_D = 2.2mA - 2.6mA$$


$$= -0.4mA$$

— don't want to take
→ not Required

$$g_m = \frac{0.4mA}{0.2V} = 2mA/V$$


$$g_m = 2mmb.$$

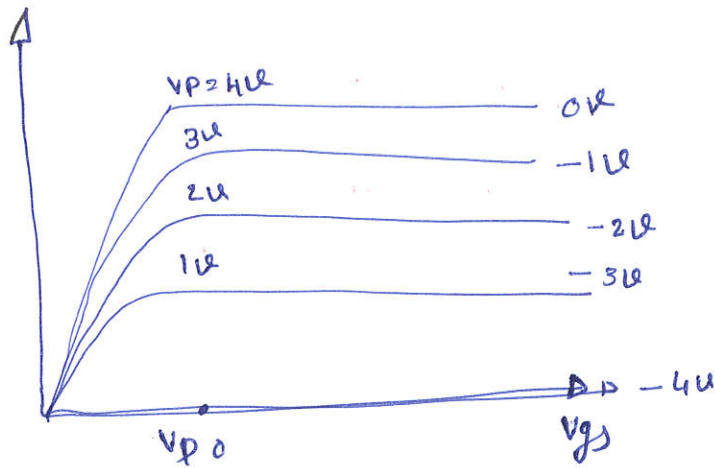2. The pinchoff voltage for an n-channel JFET is 4V. If the pinch off occurs for V_{DS} when $V_{GS} = -1$ V, then



$$V_P = 3V \text{ for } V_{GS} = -1V$$

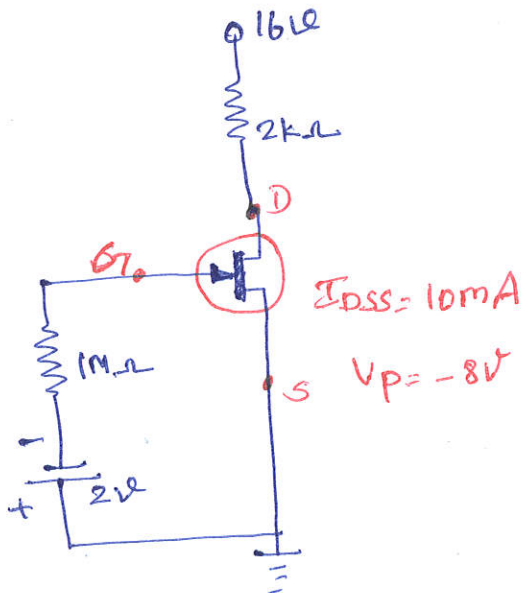3. Determine the following for the network shown in figure.



a) V_{GS}

b) I_{DQ}

c) V_{DS}

d) V_D

e) V_G

f) V_S

* $I_G \approx 0A$

$$a] \rightarrow Q_{i,pt} = [V_{GSQ}, I_{DQ}]$$

c] $V_{DS} \rightarrow$ o/p voltage

d] $V_D \rightarrow$ potential of the drain

e] $V_G \rightarrow$ potential of the Gate.

f] $V_S \rightarrow$ potential at the Source

} $\rightarrow$ not a potential difference
 $\rightarrow$ pot at a pt

$V_D =$ p.d between D and ground
 $\downarrow \quad \downarrow$
 $V_D \quad 0V$

$$V_D = V_D - 0V = V_D - V_S$$

$$\boxed{V_D = V_{DS}}$$

$\rightarrow$ Ans of part e & d as same

$$V_G = V_G - 0V$$

$$\boxed{V_S = 0V}$$

$$V_G = V_G - V_S$$

$$\boxed{V_G = V_{GS}}$$

$\rightarrow$ Ans of a part equal to the
 Ans of e part

already we know that

Source is connected to ground

$$\boxed{V_S = 0V} \leftarrow$$

So.

a) V_{GSQ}

Apply KVL

$$-2V - 1mA(0) - V_{GS} = 0$$

$$V_{GS} = -2V$$

$$V_{GSQ} = V_{GS}$$

c) $V_G = V_{GS}$

$\therefore$

$$V_G = -2V$$

b) $I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2$

$$I_D = 10mA \left[1 - \frac{[-2]}{[-8]} \right]^2$$

$$I_D = 5.62mA$$


c) $V_{DS} = \text{O/p voltage}$

Apply KVL

$$16V - I_D[2k] - V_{DS} = 0$$

$$16V - 5.62[2k] - V_{DS} = 0$$

$$V_{DS} = 4.75V$$

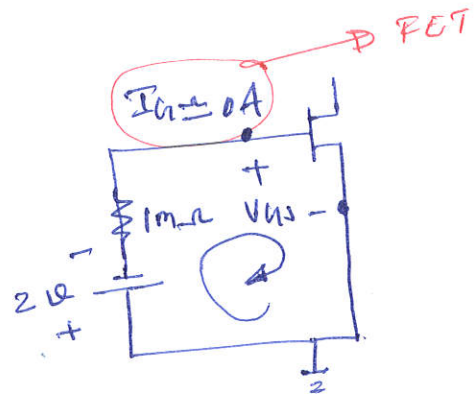

wkt $\rightarrow$ given

$$I_{DSS} = 10mA$$

$$V_P = -8V$$


d) $V_D = V_{DS}$

$$V_D = 4.75V$$


f) $V_S = 0V$

b) $I_D = I_{DQ}$

$$I_{DQ} = 5.62mA$$

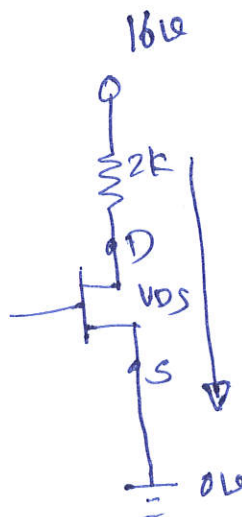

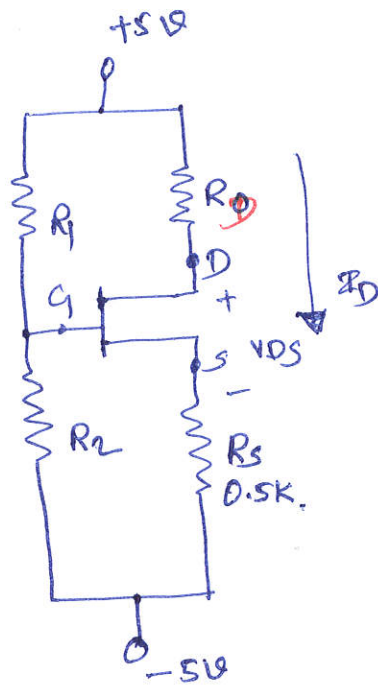3) Determine the following parameters for the network as shown in figure.



$$I_{DSS} = 10 \text{ mA}$$

$$V_P = -3 \text{ V}$$

$$R_1 + R_2 = 120 \text{ K}$$

$$I_D = 5 \text{ mA}$$

$$V_{DS} = 5 \text{ V}$$


find, R_1, R_2, R_D

Apply KVL find R_D in output

$$5 - I_D(R_D) - V_{DS} - 0.5(I_D) + 5 = 0$$

$$5 - 5 \text{ mA}(R_D) - 5 \text{ V} - 0.5(5 \text{ mA}) + 5 = 0$$

$$R_D = 0.5 \text{ K}\Omega$$

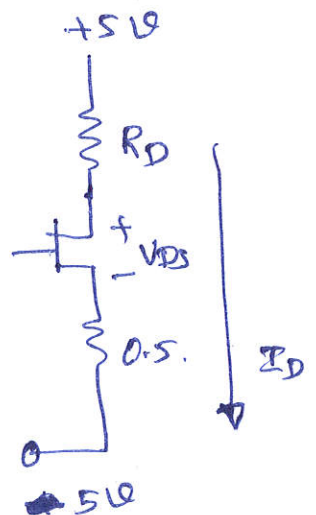

We need two eqn : 2 unknown : R_1 & R_2 .

$$1) R_1 + R_2 = 120 \text{ K}$$

Apply Thevenin logic

$$V_G = V_G' + V_G''$$

$$V_G = V_G'$$

$$V_G = 5 \cdot \frac{R_2}{R_1 + R_2} - 5 \cdot \frac{R_1}{R_1 + R_2}$$

$$V_G' = 5V \rightarrow \text{ON}$$

$$V_G'' = -5V \rightarrow \text{ON}$$

$\frac{R_2}{R_1 + R_2} \rightarrow$ Numerator
Connected to ground

WKT

$$V_{GS} = V_G - V_S$$

$$V_G = V_{GS} + V_S$$

Apply KVL

we will get


$$\frac{V_S + 5}{0.5K} = I_D$$

WKT

$$I_D = 5mA$$

$$\frac{V_S + 5}{0.5K} = 5mA$$

$$V_S = -2.5V$$

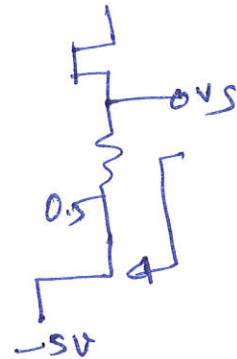

$$V_S + 5 - 0.5K - 2020$$

$$V_S + 5 = 0.5K I_D$$

$$\frac{V_S + 5}{0.5K} = I_D$$

NO USE I_D equations we will get V_{GS}

$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2$$

$$5mA = 10mA \left[1 - \frac{V_{GS}}{-3V} \right]^2$$

Finally we will get

$$V_{GS} = -0.87V$$

$$V_G = V_{GS} + V_S$$

$$V_G = -0.87 - 2.5V$$

$$V_G = -3.37V$$

NOW we can re-write two equations.


$$R_1 + R_2 = 120K. \rightarrow (1)$$

$$5 \frac{R_2}{R_1 + R_2} - 5 \frac{R_1}{R_1 + R_2} = -3.37K \rightarrow (2)$$

Solving these two equations we will get

R_1 & R_2

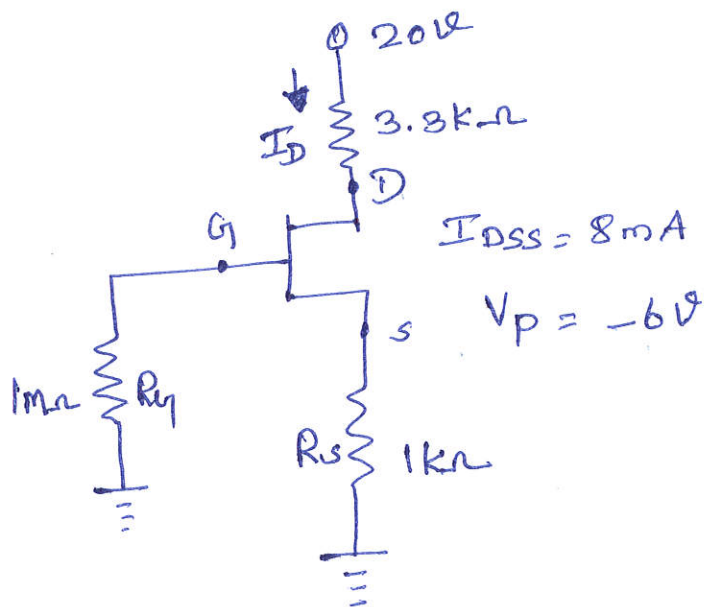4] Determine the following for the network.



- V_{GSQ}
- I_{DQ}
- V_{DS}
- V_S
- V_G
- V_D

Solutions.

a) The Gate to Source voltage.

$$V_{GS} = -I_D R_S$$

Assume $I_D = 4mA$


$$V_{GS} = -[4mA][1k\Omega]$$

$$V_{GS} = -4V$$

$$I_D = 8mA$$

$$V_{GS} = -[8mA][1k\Omega]$$

$$V_{GS} = -8V$$

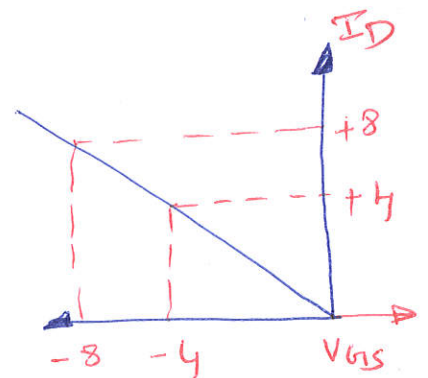

From the Shockly equation.

$$V_{GS} = \frac{V_P}{2} = -3V$$

$$I_D = \frac{I_{DSS}}{4} = 2mA.$$

b) At the quiescent point

$$I_{DQ} = 2.6mA.$$

$$c) V_{DS} = V_{DD} - I_D (R_S + R_D)$$

$$= 20V - (2.6mA)(1k\Omega + 3.3k\Omega)$$

$$= 8.82V.$$

$$d) V_S = I_D \cdot R_S$$

$$= (2.6mA)(1k\Omega)$$

$$V_S = 2.6V$$

$$e) V_G = 0$$

$$f) V_D = V_{DS} + V_S = 11.42V$$

(or)

$$V_D = V_{DD} - I_D R_D = 11.42V.$$