

- What is the difference between bipolar junction transistor and field effect transistor (at least 3)? [3pt]
- For the voltage-divider bias configuration of Fig. 1 given below, determine: [6pt]

- I_{BQ}
- I_{CQ}
- V_{CEQ}
- V_C
- V_E
- V_B

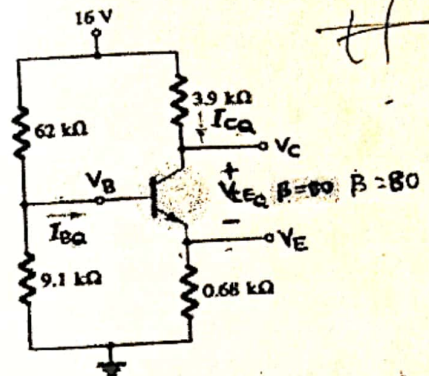


Fig. 1

- For the network of Fig. 2 below by using re-equivalent circuit model: [9pt]

- Determine A_{VNL} , Z_i , and Z_o .
- Determine A_{VL} and A_{VS} .
- Calculate $A_i = \frac{I_o}{I_i}$.
- Change R_L to 5.6 k and calculate A_{VS} .

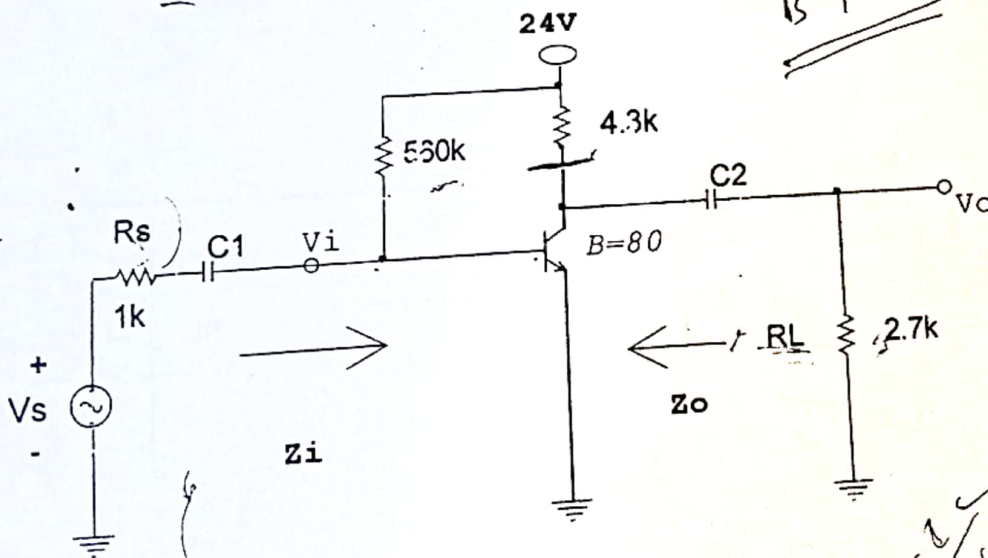


Fig. 2

$$V_{CC} = V$$

$$V_{CC} = I_R$$

$$V_{CC} = V$$

$$V_{CC} = V$$

$$A_{VNL} = \frac{V_o}{V_i}$$

4. Given the measurement $V_S = 1.7\text{ V}$ for the network of Fig.3 below, determine:

[5pt]

- IDQ.
- VGSQ.
- IDSS.
- VD.
- VDS.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = I_{DSS} (1 - \dots)$$

$$u = \frac{2I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P} \right)$$

$$2 = \frac{2I_D(0.51k)}{V_P}$$

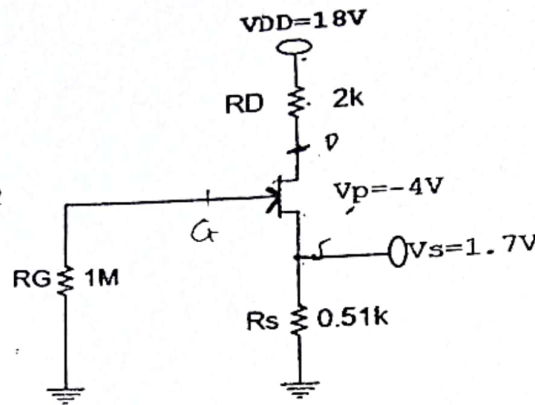


Fig.3

$$V_{GS} + 0.7 = 0$$

$$V_{GS} = -0.7$$

$$I_D$$

5. For the self-bias JFET network of Fig.4 given below:

[8pt]

- Determine Z_i and Z_o .
- Determine A_{vL} and A_{vS} .

4

4

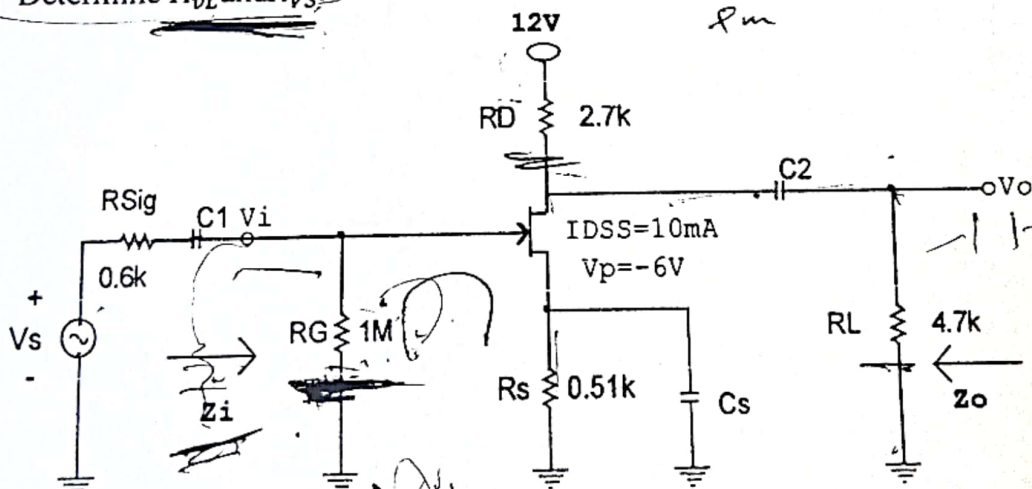


Fig.4

6. Design a Common Emitter Amplifier with Voltage Divider Bias for the following parameters: $V_{CC} = 24\text{V}$, $I_C = 5\text{mA}$, $V_E = 0.1V_{CC}$, $V_C = 0.55V_{CC}$, $\beta = 135$ and $R_2 = 6.2k\Omega$.

[4pt]




Circuit Applied Electronics-I Final-exam (Solved)

Question paper

1. Draw the input and output characteristics curve of common emitter and show the region of operation of BJT. (5 points)
2. Draw the electrical equivalent circuit of bipolar junction transistor (BJT) using **re** and **hybrid** equivalent model. (5 points)
3. Consider the two stage amplifier where the transistor specification and biasing conditions are the same but the voltage gain of the second stage is higher than the first. Why? Reason out (2 points)
4. Compare and contrast BJT with FET (2 points)
5. For the network below determine: (10 points)
 - a. r_e ✓
 - b. Z_i ✓
 - c. Z_o ✓
 - d. A_v ✓
 - e. A_i ✓
 - f. A_p ✓

(note: assume r_o is infinity)

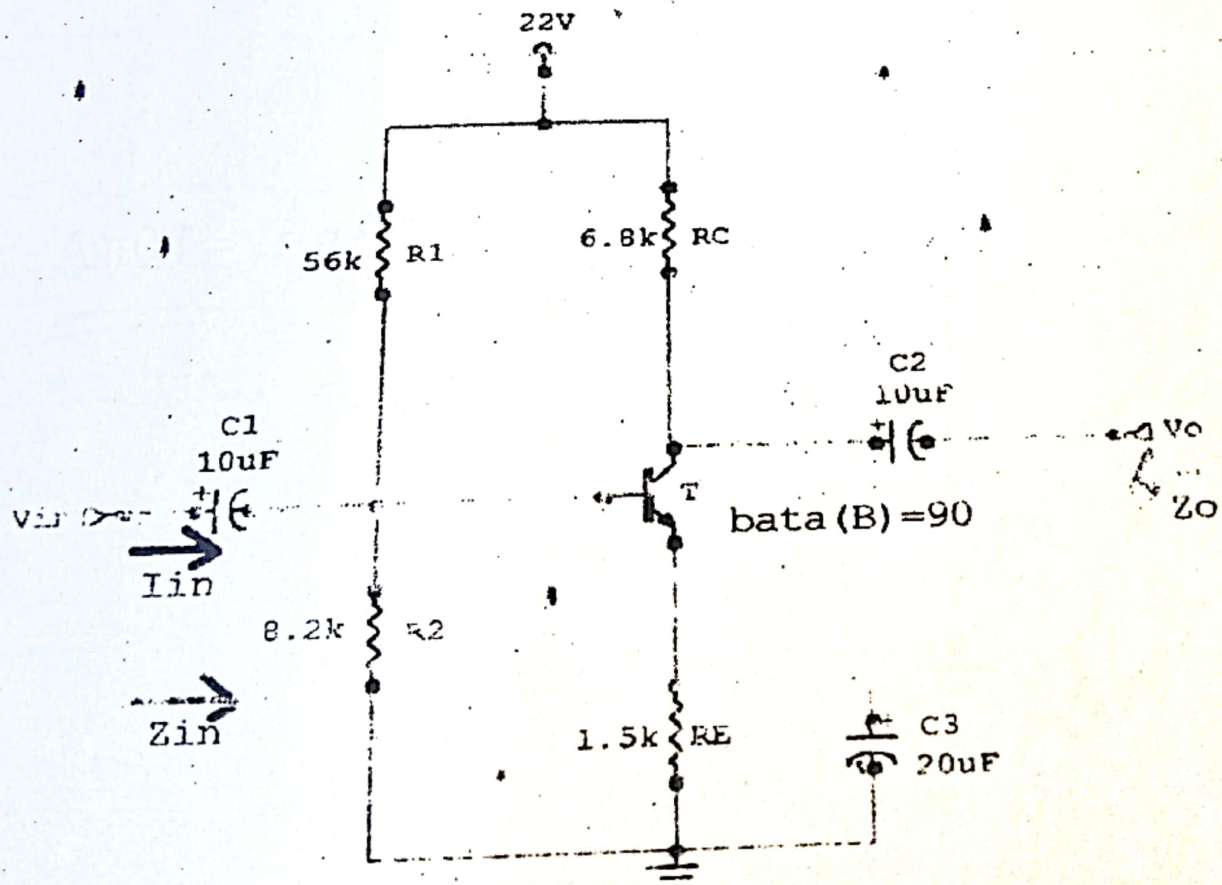

6. Given that a common emitter amplifier has the following h- parameters:

(6 points)


$$h_{ic} = 1.1 \text{ K } \Omega, h_{re} = 0.25 \times 10^{-3}, h_{fe} = 50, h_{oe} = 25 \mu \text{ mho}$$

If the load resistance is $1 \text{ k}\Omega$, and source resistance is also $1 \text{ k}\Omega$, calculate,

- Current gain
- voltage gain
- input impedance
- output impedance

7. Determine I_{DSQ} for the network below using mathematical method

(10 points)

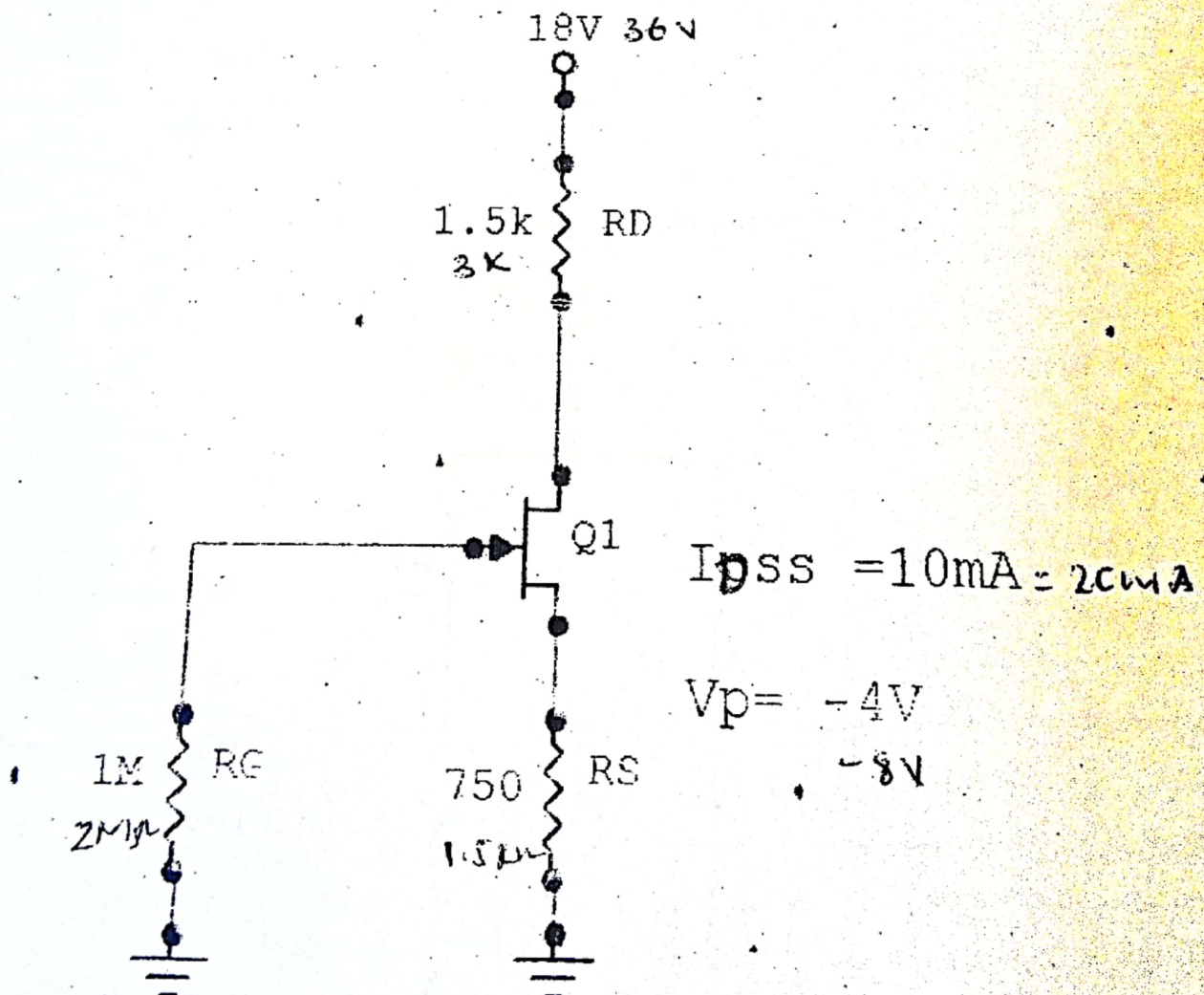

$$\frac{1}{Z_0} = \frac{1}{R_0} + \frac{h_{fe}}{R_{s1} h_i}$$

$$= \frac{1}{25} + \frac{50 \times 0.25 \times 10^3}{100 + 1.1 \text{ k}\Omega}$$

$$= \frac{1}{25} + \frac{12.5}{2.1 \text{ k}\Omega}$$

$$= \frac{1}{25} + 5.95$$


$$\frac{1}{Z_0} = 19.04 \text{ k}\Omega$$

$$Z_0 = \frac{1}{19.04}$$


$$= 0.0525 \text{ m}\Omega$$

$$= 52.5 \text{ k}\Omega$$

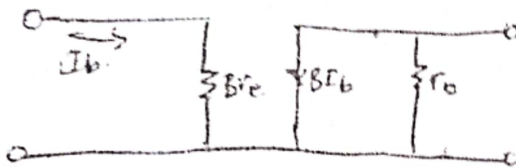2) Draw the electrical equivalent circuit of BJT using re & hybrid equivalent model





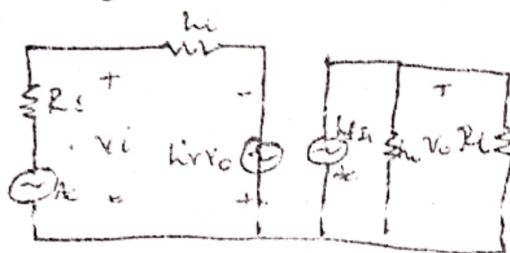3) Draw the re equivalent circuit & analysis



4) Draw the input & output characteristics curve of common emitter & show the region of operation BJT

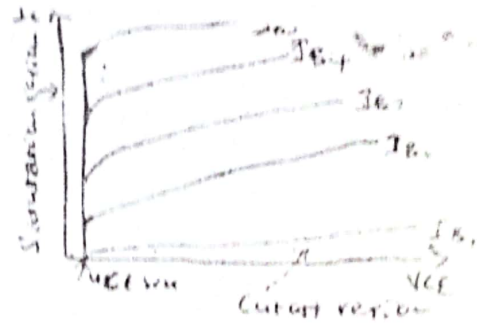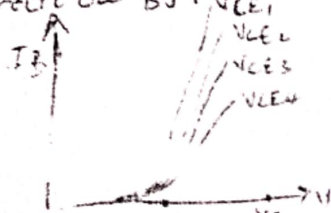5) Draw the input & output characteristics curve of common emitter & show the region of operation BJT



Output Characteristics

6) Draw common emitter & common base BJT & FET

BJT operation involves both electron & holes. Charge flow in such transistor is due to bidirectional diffusion of charge carrier across a junction b/w two region of diff. charge concentration.

FET - is only one carrier type is involved in charge flow due to drift. This charge carrier is either electrons or holes as majority charge carriers only.

5) Given that common emitter amplifier

$$\begin{aligned} h_{ie} &= 1 \text{ k}\Omega \\ h_{re} &= 0.25 \times 10^{-3} & R_2 &= 1 \text{ k}\Omega \\ h_{fe} &= 50 & R_3 &= 1 \text{ k}\Omega \\ h_{oe} &= 25 \text{ H}\mu\text{mho} \end{aligned}$$

* the current Gain

$$A_i = \frac{I_o}{I_i}$$

$$A_i = \frac{h_{fe}}{1 + h_{oe} R_L} \quad \text{-- see the proof on the hand copy in the last page. (BJT)}$$

$$A_i = \frac{50}{1 + 25 \times 1 \text{ k}\Omega}$$

$$= \frac{50}{26} = \underline{\underline{1.92}}$$

* Voltage gain

$$A_v = \frac{V_o}{V_i}$$

$$A_v = \frac{-h_{fe} R_L}{h_{ie} + R_1(h_{ie} h_{oe} - h_{fe} h_{re})} \quad \text{-- you the hand copy}$$

$$\begin{aligned} &= \frac{-50 \times 1 \text{ k}\Omega}{1.1 + (25 \times 1 - 12.5)} \\ &= \underline{\underline{-3.33}} \end{aligned}$$

* Input Impedance

$$Z_i = \frac{V_i}{I_i} \quad \text{-- on the hand copy (BJT)}$$

$$\begin{aligned} Z_i &= h_{ie} - h_{re} A_i R_L \\ &= 1.1 - 0.25 \times 10^{-3} \times 1.92 \times 1 \text{ k}\Omega \\ &= \underline{\underline{0.62 \text{ k}\Omega}} \end{aligned}$$


* Output Impedance

$$Z_o = 1 \quad \text{-- on the hand copy (BJT)}$$


$$\frac{1}{Z_o} = \frac{h_{oe} - h_{fe} h_{re}}{R_2 + h_{ie}}$$

$$Z_o = 52.5 \text{ H}\Omega$$

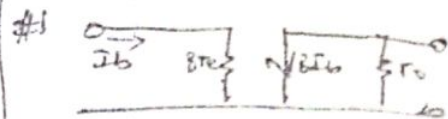(2) Draw the electrical equivalent circuit of BJT using re & hybrid equivalent model




the re equivalent circuit

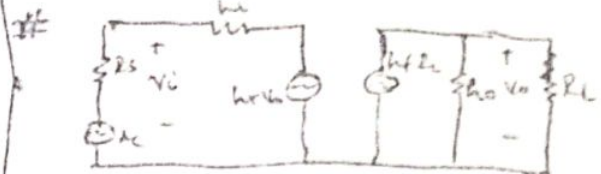

the hybrid equivalent circuit

ASTU General
@fresh_astu

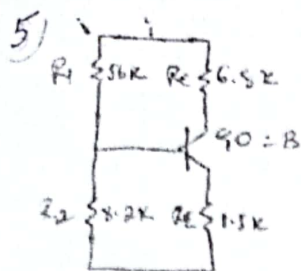

$$V_B = \frac{R_2 V_{CC}}{R_1 + R_2}$$

$$= \frac{8.2 \times 12}{5.5 + 8.2}$$

$$= 2.81V$$

$$V_{BE} = V_B - V_E$$

$$V_E = V_B - V_{BE}$$

$$= 2.81 - 0.7$$

$$= 2.11V$$

$$I_E = \frac{V_E}{R_E} = \frac{2.11V}{1.5k} = 1.41mA$$

$$r_E = \frac{26mV}{1.41mA} = 18.45\Omega$$

$$R' = R_1 || R_2 \Rightarrow \frac{1}{\frac{1}{5.5} + \frac{1}{8.2}} = \frac{5.5 \times 8.2}{5.5 + 8.2} = 3.15k\Omega$$


from input section

$$V_{CC} - R' I_B - V_{BE} - I_E R_E$$

$$V_{CC} - R' I_B - V_{BE} - \beta I_B R_E$$

$$I_B = \frac{V_{CC} - V_{BE}}{R' + \beta R_E} = \frac{12 - 0.7}{3.15k + 90 \times 1.5k}$$

$$I_B = \frac{11.3}{142.5} = 0.079mA$$

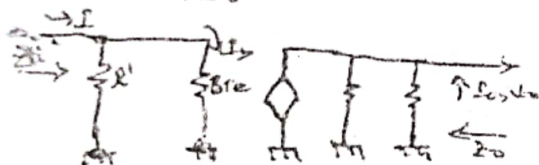

$$Z_i = R' || \beta r_E$$

$$= \frac{1}{\frac{1}{3.15k} + \frac{1}{90 \times 18.45\Omega}}$$

$$= \frac{11.89}{8.81} = 1.349k\Omega$$

$$Z_o = R_C$$

$$= 6.8k\Omega$$

$$V_i = I_B \beta R_E$$

$$= 0.079mA \times 90 \times 1.5k$$

$$= 0.054V$$

$$V_o = -R_C \beta I_B, I_B = \frac{V_i}{\beta R_E}$$

$$= -R_C \frac{V_i}{R_E} = -\frac{R_C}{R_E} V_i$$

$$= -\frac{6.8k\Omega}{1.5k\Omega} \times 0.054V$$

$$= -0.92V$$

$$A_v = \frac{V_o}{V_i} = \frac{-0.92V}{0.25V}$$

$$= -367.96$$


$$A_i = \frac{I_o}{I_i}, \text{ but } I_o = \beta I_B, I_i = I_B$$

$$= \frac{\beta I_B}{I_B} = \beta = 90$$

$$A_p = A_v \times A_i$$

$$= -367.96 \times 90$$

$$= -33116.4$$

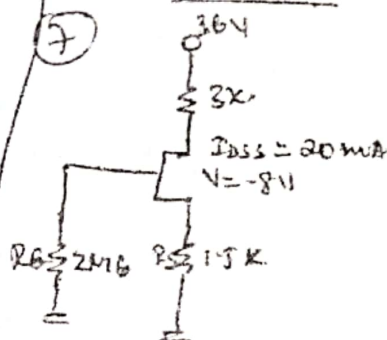

from the input section

$$V_G = -I_{DS} R_S$$

$$I_{DS} = I_{DSS} \left(1 - \frac{V_G}{V_P}\right)^2$$

$$= 0.02 \left(1 - \frac{-I_{DS} R_S}{-8}\right)^2$$

$$= 0.02 \left(1 - \frac{I_{DS} (1500)}{8}\right)^2$$

$$= 0.02 \left(1 - 187.5 I_{DS}\right)^2$$

$$I_{DS} = 703.125 I_{DS}^2 - 75 I_{DS} + 0.02$$

$$0 = 703.125 I_{DS}^2 - 75 I_{DS} + 0.02$$

by using quadratic formula

$$I_{DS} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$I_{DS} = 7.7mA, I_{DS} = 2.8mA$$

but $I_{DS} < I_{DSS}$

hence two possible answers



$$V_B = \frac{R_2 V_{CC}}{R_1 + R_2}$$

$$= \frac{8.2 \times 22}{8.2 + 56}$$

$$= 2.81V$$

$$V_{BE} = V_B - V_E$$

$$V_E = V_B - V_{BE}$$

$$= 2.81 - 0.7$$

$$V_E = 2.11V$$

$$I_E = \frac{V_E}{R_E} = \frac{2.11V}{1.5}$$

$$= 1.406mA$$

$$R_E = \frac{26mV}{1.406mA}$$

$$= 18.48\Omega$$

$$R' = R_1 || R_2$$

$$= \frac{1}{\frac{1}{56} + \frac{1}{8.2}} = \frac{8.2 \times 56}{56 + 8.2}$$

$$= 7.15K\Omega$$

$$V_{CC} - R' I_B - V_{BE} - I_E R_E$$


$$V_{CC} - R' I_B - V_{BE} - \beta I_B R_E$$

$$I_B = \frac{V_{CC} - V_{BE}}{R' + \beta R_E}$$

$$= \frac{22 - 0.7}{7.15K\Omega + 40 \times 1.5}$$

$$I_B = \frac{21.3}{142.5} = 0.15mA$$

~~V_{CE} = V_{CC} - I_C R_C~~

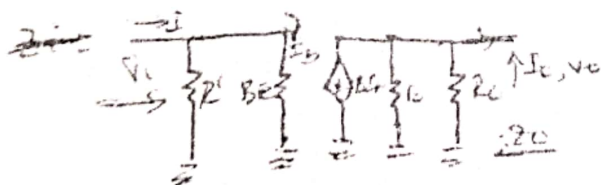

$$Z_i = R' || \beta R_E$$

$$= \frac{1}{\frac{1}{7.15K} + \frac{1}{40 \times 18.48\Omega}}$$

$$= 1.15 \times 1.6632$$

$$7.15 + 1.6632$$

$$= \frac{11.84}{8.81} = 1.344K\Omega$$

$$Z_o = R_C$$

$$= 6.8K\Omega$$

$$V_i = I_B \beta R_E$$

$$= 0.15mA \times 40 \times 18.48\Omega$$

$$= 0.25V$$

$$V_o = R_C \beta I_B, I_B = \frac{V_i}{\beta R_E}$$

$$= R_C \beta \left(\frac{V_i}{\beta R_E} \right)$$

$$= \frac{R_C V_i}{R_E}$$

$$= 6.8K \times \frac{0.25V}{18.48\Omega}$$

$$= 0.0919V = 92V$$

$$A_v = \frac{V_o}{V_i} = \frac{V_o}{V_i} = \frac{0.0919V}{0.25V}$$

$$A_v = \frac{V_o}{V_i} = \frac{92V}{0.25V}$$

$$= 367.96$$

$$A_i = \frac{I_o}{I_i}$$

$$\text{but } I_o = \beta I_B, I_i = I_B$$

$$A_i = \frac{\beta I_B}{I_B} = \beta = 40 \text{ or}$$

$$A_i = \frac{I_o}{I_i}, I_o = V_o / R_C$$

$$I_i = V_i / Z_i$$

$$A_i = \frac{V_o}{R_C} \cdot \frac{Z_i}{V_i} = A_v \cdot \frac{\beta R_E}{R_C}$$

$$= 367.96 \times 40 \times 18.48$$

$$6.8K\Omega$$

$$= \frac{611,991.072}{6.8K\Omega}$$


$$A_p = A_v \times A_i$$

$$367.96 \times 40 = 14718.4$$

Given that Common emitter amplifier

$$\begin{aligned} h_{ie} &= 1.1 \text{ k}\Omega, R_L = 1 \text{ k}\Omega \\ h_{re} &= 0.25 \times 10^{-3}, \beta = 100 \\ h_{fe} &= 50 \\ h_{oe} &= 25 \text{ H}\mu\text{mho} \end{aligned}$$

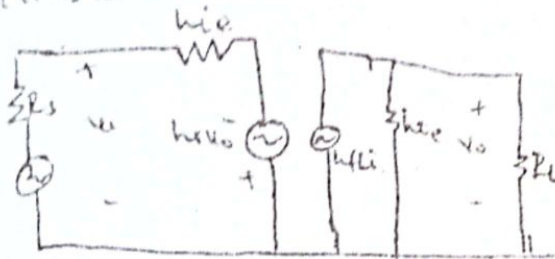The hybrid equivalent model as small signal amplifier circuit will be



Current Gain

$$A_i = \frac{I_o}{I_i}, \text{ but } I_o = h_f I_i + V_o h_o$$

$$I_o = h_f I_i + h_o V_o, V_o = -I_o R_L$$

$$I_o = h_f I_i + h_o (-I_o R_L)$$

$$I_o = h_f I_i - h_o I_o R_L$$

$$I_o + h_o I_o R_L = h_f I_i$$

$$I_o (1 + h_o R_L) = h_f I_i$$

$$I_o = \frac{h_f I_i}{1 + h_o R_L}$$

$$\frac{I_o}{I_i} = \frac{h_f}{1 + h_o R_L}$$

$$A_i = \frac{h_f}{1 + h_o R_L}$$

$$= \frac{50}{1 + 25 \times 10^{-6} \times 1000}$$

$$= \frac{50}{26} = 1.92$$

Voltage gain

$$A_v = \frac{V_o}{V_i}, V_i = h_{ie} I_i + V_o$$

$$\text{but } V_o = -I_o R_L$$

$$A_v = \frac{-I_o R_L}{V_i}, I_o = A_i I_i$$

$$= \frac{-A_i I_i R_L}{V_i}, \text{ but } \frac{I_i}{V_i} = \frac{1}{Z_i}$$

$$= \frac{-A_i R_L}{Z_i}, \frac{1}{Z_i} = \frac{I_i}{V_i}$$

$$= \frac{-1.92 \times 1 \text{ k}\Omega}{Z_i}, Z_i = \frac{V_i}{I_i}$$

but Z_i is unknown therefore by other method.

$$A_v = \frac{V_o}{V_i}, V_i = h_{ie} I_i + V_o$$

$$I_i = \frac{I_o}{h_f} (1 + h_o R_L)$$

$$I_o = \frac{-V_o}{R_L}$$

$$V_i = h_{ie} I_i + V_o$$

$$V_i = h_{ie} \left(\frac{I_o}{h_f} (1 + h_o R_L) \right) + V_o$$

$$V_i = -\frac{h_{ie} V_o}{h_f R_L} (1 + h_o R_L) + V_o$$

$$V_i = \left(-\frac{h_{ie} (1 + h_o R_L)}{h_f R_L} + 1 \right) V_o$$

$$V_i = \frac{(-h_{ie} (1 + h_o R_L) + h_f R_L)}{h_f R_L} V_o$$

$$\frac{V_i (h_f R_L)}{-h_{ie} (1 + h_o R_L) + h_f R_L} = V_o$$

$$= \frac{-h_f R_L}{h_{ie} (1 + h_o R_L) + h_f R_L}$$

$$= \frac{-h_f R_L}{h_{ie} (1 + h_o R_L) + h_f R_L} = \frac{V_o}{V_i}$$

$$= \frac{-h_f R_L}{h_{ie} (1 + h_o R_L) + h_f R_L}$$

b)

$$V_o = \frac{-h_f R_L}{h_i(1+h_o R_L) + h_f R_L h_r}$$

$$= \frac{-h_f R_L}{h_i + h_i h_o R_L + h_f R_L h_r}$$

$$= \frac{-h_f R_L}{h_i + R_L(h_i h_o + h_f h_r)}$$

$$= \frac{-50 \times 1k}{1.1k + 1k(1.1 \times 25 - 50 \times 0.25m)}$$

$$= \frac{-50}{1.1 + (27.5 - 12.5)}$$

$$= \frac{-50}{1.1 + 15}$$

$$= \frac{-50}{16.1}$$

$$A_v = \frac{-50}{16.1} = -3.11$$

$$A_v = \frac{-50}{16.1} = -3.11$$

$$= \frac{-50}{1.1 + (27.5 - 12.5)}$$

$$= \frac{-50}{1.1 + 15}$$

$$= \frac{-50}{16.1}$$

$$A_v = \frac{-50}{16.1} = -3.11$$

cf input impedance

$$Z_i = \frac{V_i}{I_i}, \quad V_i = h_i I_i + h_r V_o$$

$$V_o = -I_o R_L$$

$$I_o = A_i I_i$$

$$V_i = h_i I_i + h_r V_o$$

$$V_i = h_i I_i + h_r (-I_o R_L)$$

$$V_i = h_i I_i - h_r I_o R_L$$

$$V_i = h_i I_i - h_r A_i I_i R_L$$

$$V_i = (h_i - h_r A_i R_L) I_i$$

$$\frac{V_i}{I_i} = h_i - h_r A_i R_L$$

$$Z_i = 1.1k - 0.25m \times 50 \times 1k$$

$$Z_i = h_i - h_r A_i R_L$$

$$= 1.1 - 0.25 \times 10^{-3} \times 50 \times 10^3$$

$$= 1.1 - 12.5$$

$$= -11.4k$$

cut put impedance

$$Z_o = \frac{V_o}{I_o} = Z_o = \frac{1}{Y_o}$$

$$\Rightarrow Y_o = \frac{I_o}{V_o}$$

$$I_o = h_f I_i + h_o V_o$$

$$\frac{I_o}{V_o} = \frac{h_f I_i}{V_o} + h_o$$

$$Y_o = \frac{h_f I_i}{V_o} + h_o, \quad I_i = A_i I_o, \quad V_o = -I_o R_L$$

$$= \frac{h_f I_o}{-I_o R_L} + h_o$$

$$= -\frac{h_f}{R_L} + h_o$$

Or by other method

$$Z_o = \frac{V_o}{I_o}, \text{ with signal } V_s \text{ set } 0$$

from from the input section

$$I_i (R_s + h_i) = -h_r V_o$$

$$I_i = \frac{-h_r V_o}{R_s + h_i}$$

$$I_o = h_f I_i + h_o V_o$$


$$I_o = -\frac{h_f h_r V_o}{R_s + h_i} + h_o V_o$$

$$I_o = \left(-\frac{h_f h_r}{R_s + h_i} + h_o \right) V_o$$

$$\frac{I_o}{V_o} = h_o - \frac{h_f h_r}{R_s + h_i}$$

$$-8-1 \quad Z_o$$

$$\frac{1}{R_s + h_i}$$

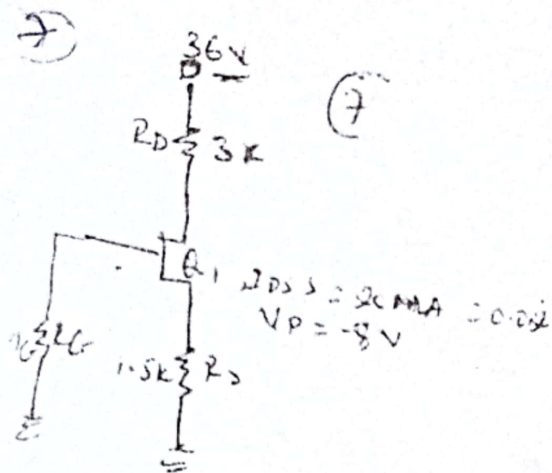

from the input section

$$V_G = -I_{DS} R_S$$

$$\begin{aligned} I_{DS} &= I_{DSS} \left(1 - \frac{V_G}{V_P}\right)^2 \\ &= 0.02 \left(1 - \frac{-I_{DS} R_S}{V_P}\right)^2 \\ &= 0.02 \left(1 - \frac{1500 I_{DS}}{8}\right)^2 \\ &= 0.02 (1 - 187.5 I_{DS})^2 \\ &= 0.02 (35156.25 I_{DS}^2 - 75 I_{DS} + 1) \end{aligned}$$

$$\begin{aligned} I_D &= 703.125 I_{DS}^2 - 75 I_{DS} + 0.02 \\ I_D - I_D &= 703.125 I_{DS}^2 - 75 I_{DS} - I_D + 0.02 \\ &= 703.125 I_{DS}^2 - 8.5 I_{DS} + 0.02 \end{aligned}$$

then using quadratic formula

$$\begin{aligned} I_D &= \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} \\ &= \frac{-(-8.5) \pm \sqrt{(-8.5)^2 - 4 \times 703.125 \times 0.02}}{2 \times 703.125} \\ &= \frac{8.5 \pm \sqrt{72.25 - 56.25}}{1406.25} \\ &= \frac{8.5 \pm \sqrt{16}}{1406.25} \\ &= \frac{8.5 \pm 4}{1606.25} \end{aligned}$$

$$\begin{aligned} I_D &= \frac{8.5 + 4}{1606.25} = \frac{12.5}{1606.25} \\ &= 0.00777 \text{ A} = 7.77 \text{ mA} \\ I_D &= \frac{8.5 - 4}{1606.25} = \frac{4.5}{1606.25} \\ &= 0.0028 \text{ A} = 2.8 \text{ mA} \end{aligned}$$

Here for I_{DS} is two possible answers, they are 7.7mA & 2.8mA

-9-