

Biasing Circuits.

- * when transistor when it is an amplifier the first thing to remember is that it is has to be biased in the active Region.
- * When we give a Small Ac Signal at the input of the transistor then it will be able to amplify it to a large signal
- * Faithful Amplification $\rightarrow$ biased properly.

Biasing

- * the proper selection of the operating point or Maintenance of proper level of Dc Voltage and cnts.
- * Common Emitter transistor $\rightarrow$ High Amplification factor and β .
- * For Faithful Amplification.

$$BEJ \rightarrow FB \quad CBJ \rightarrow RB.$$

to achieve faithful Amplification, the following basic Condition must be satisfied.





- 1) proper Zero Signal collector ckt
- ii) Minimum proper base Voltage (V_{BE}) at any instant
- iii) Minimum collector-emitter Voltage (V_{CE}) at any instant

It should ensure the stabilisation of operating point

Methods of transistor Biasing

- * Fixed Bias ckt [Base Bias]
- * collector-to-Base Bias circuit
- * Fixed Bias with Emitter Resistor.
- * Voltage Divider Bias
- * Emitter Bias.

Fixed Bias

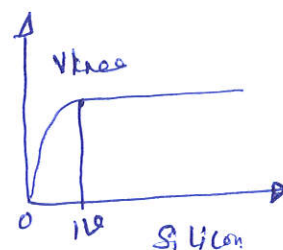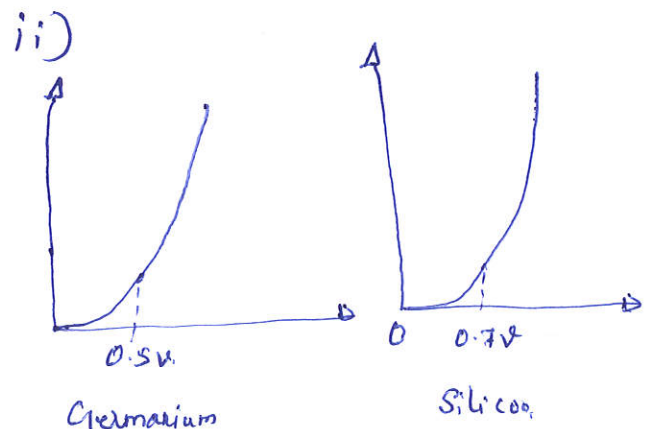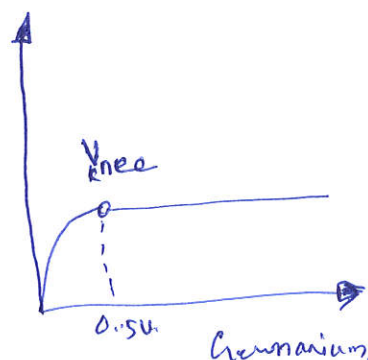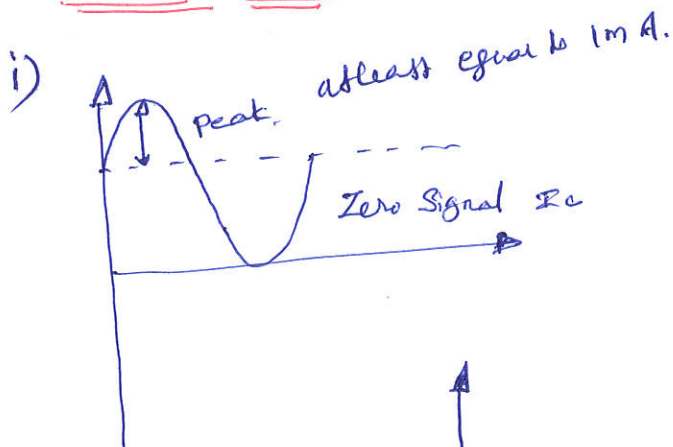

Fixed bias

* This bias also called as Base Bias.

→ I_B Relatively constant.

↳ by collector bias I_C and V_{CC} and R_B

Since V_{CC} , V_{BE} , and R_B are constant, I_B remains constant at particular level. therefore this type of is called fixed bias type of circuit.

Input section.

KVL around the supply - base - ground circuit we get.

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$V_{CC} = I_B R_B + V_{BE}$$

Solving for I_B ,

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

here

$$V_{CC} \gg V_{BE}$$

$$\therefore I_B = \frac{V_{CC}}{R_B}$$

The Main purpose of the dc biasing circuit is to setup initial dc values of.


- * Base current
- * collector current
- * collector - Emitter voltage, from single

power supply V_{CC} .

* The initial dc values are called operating point

also known as bias point, quiescent point,
or Q. point,

Fixed bias ckt.

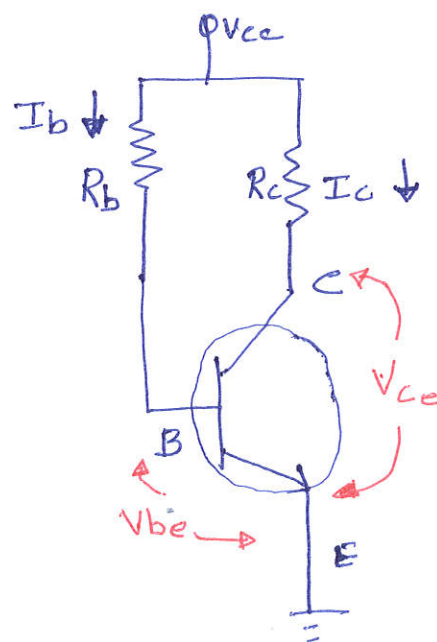

output section.

Applying the KVL around the Supply-collector ground circuit.

$$V_{CC} - I_C R_C - V_{CE} = 0.$$

$$V_{CC} = I_C R_C + V_{CE}$$

$$V_{CE} = V_{CC} - I_C R_C$$

particular CE Txs
is denoted β or h_{fe} .

$$I_C = \beta I_B$$

As per operating point of CE circuit

$$V_{CE} = 0V.$$

$$I_B = \frac{V_{CC}}{\beta R_C} \quad \text{and} \quad I_B = \frac{V_{CC}}{R_B} \quad \rightarrow \textcircled{2}$$

$\rightarrow \textcircled{1}$
Solving R_B from equations $\textcircled{1}$ & $\textcircled{2}$.

$$R_B = \beta R_C$$

Merits.

* Simple circuit, Very Small no of components are Required.


* operations is very Simple.

Demerits.

* I_C does not remain constant with Variation in temperature or power supply voltage. $\therefore$ operating point is unstable.

* when the transistor is replaced with another one, β value also change, so Q point will shift.

*

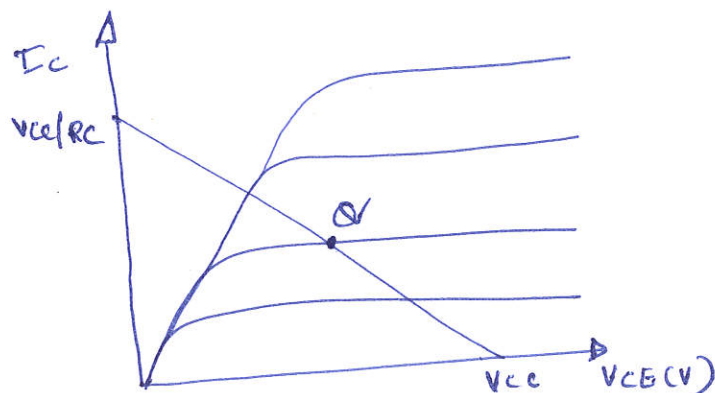

R_B is varied }
 R_C is varied } Q point
 V_{CC} is varied } will shift

* It is used only Small-Signal transistors.

* Stability factor = $\beta + 1$ $\rightarrow$ we ensure the sf.


* Stability factor less than 25 is preferred

* Small Signal Amplifier transistors have large

Stability factors.

* so fixed bias is rarely ^{NOT} used in linear circuits.

Emitter bias.

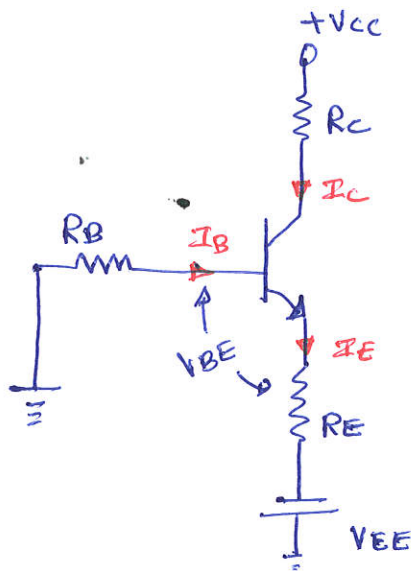

* This circuit differs from Base circuit in two Important Respects.

* first

↳ two separate d.c. voltage sources.

* one +ve V_{CC}

* other -ve V_{EE}

* Normally two supply will be equal.

for example $V_{CC} = +20V$

$V_{EE} = -20V$

* Secondly.

There is a Resistor R_E in the emitter circuit

Circuit Analysis.

i) Collector current. $[I_C]$

$$-I_B R_B - V_{BE} - I_E R_E + V_{EE} = 0$$

$$V_{EE} = I_B R_B + V_{BE} + I_E R_E$$

$$I_C \approx I_E \quad \boxed{I_C = \beta I_B} \quad \therefore I_B \approx \frac{I_E}{\beta}$$

Putting $I_B = I_E / \beta$

$$V_{EE} = \left[\frac{I_E}{\beta} \right] R_B + I_E R_E + V_{BE}$$

$$V_{EE} - V_{BE} = I_E \left(R_B / \beta + R_E \right)$$

$$\boxed{I_E = \frac{V_{EE} - V_{BE}}{R_E + R_B / \beta}} \Rightarrow \frac{V_{EE} - V_{BE}}{R_E}$$


Since $I_C \approx I_E$

$$\boxed{I_C = \frac{V_{EE} - V_{BE}}{R_E + R_B / \beta}}$$


The operating point is independent of β

$$\text{if } R_E \gg \frac{R_B}{\beta}$$

D.c. load line

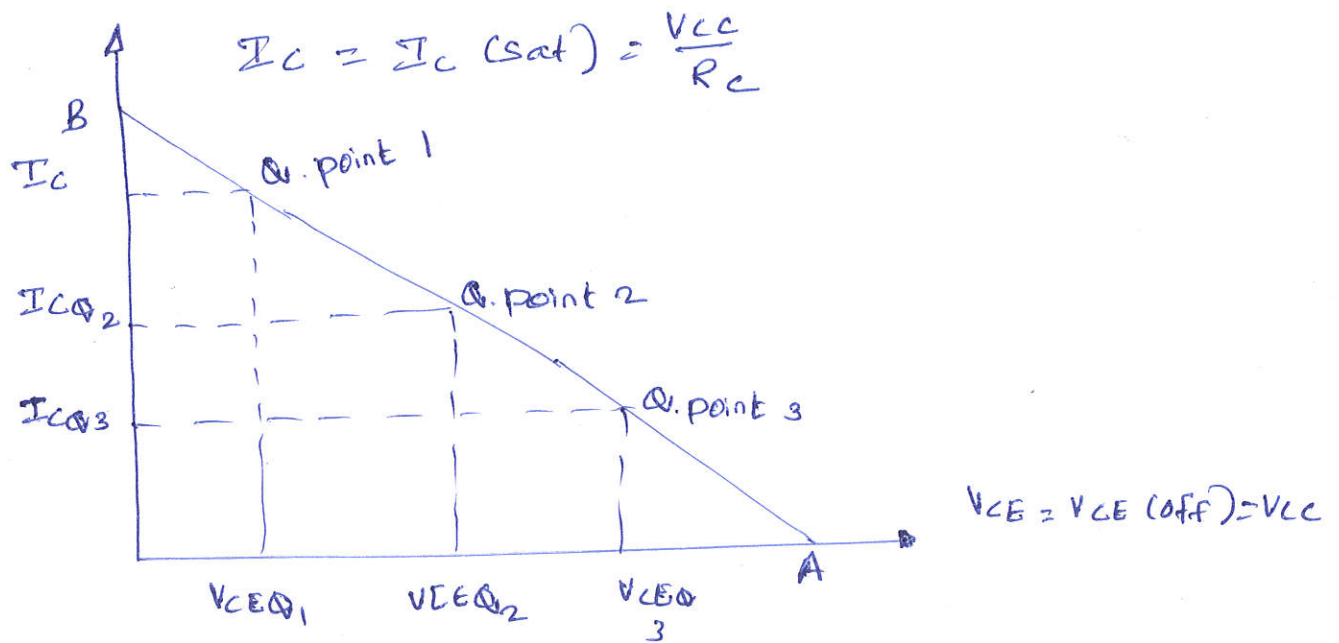

Collector to Base Bias.

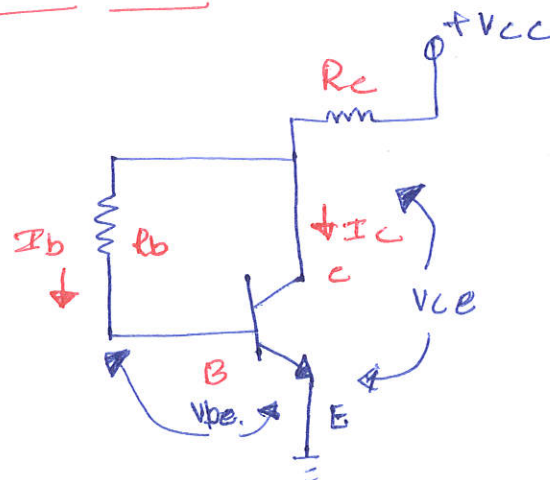

* This configuration employs $-V_c$ feedback to prevent thermal runaway

* R_B is connected to the collector.

Input Section.

KVL

$$V_{CC} = V_{RC} + V_{RB} + V_{BE}$$

Voltage across the Base Resistor.

$$V_{RB} = V_{CC} - \overbrace{(I_C + I_B) R_C}^{\text{voltage drop across } R_C} - V_{BE}$$

$\rightarrow$ voltage at base

from

$$I_C = \beta I_B$$

$$V_{RB} = V_{CC} - [\beta I_B + I_B] R_C - V_{BE}$$

$$= V_{CC} - I_B (\beta + 1) R_C - V_{BE}$$


From Ohm's law at Base current

$$I_B = V_{RB} / R_B \rightarrow V_{RB} = I_B R_B$$

$$I_B R_B = V_{CC} - I_B (\beta + 1) R_C - V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_C}$$

Fixed bias with Emitter resistor.

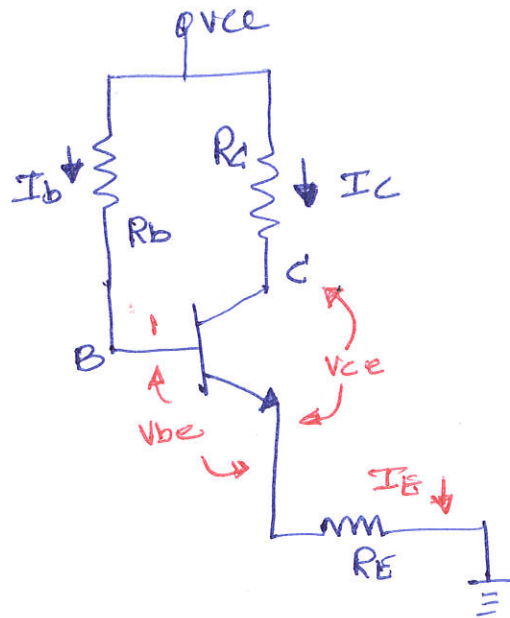

Input Section,

Applying KVL

$$V_{CC} = I_B R_B + V_{BE} + I_E R_E$$

Voltage across Base Resistor is

$$V_{RB} = V_{CC} - I_E R_E - V_{BE}$$

from ohms law

$$\text{Base current is } I_B = \frac{V_{RB}}{R_B} \rightarrow$$

I_E increases the emitter voltage

$$V_E = I_E R_E$$

$$I_C = \beta I_B$$

for $I_B \ll \beta I_B \rightarrow$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta R_C}$$

Output Section.

$$V_{CC} = I_C R_C + V_{CE}$$

$$V_{CE} = V_{CC} - I_C R_C = V_{CC} - \beta I_B R_C$$

$$I_C = \beta I_B$$

$$= \frac{\beta (V_{CC} - V_{BE})}{R_B + R_C + \beta R_C} \approx \frac{V_{CC} - V_{BE}}{R_C}$$

∴

operating point is kept stable

less $\rightarrow I_C \uparrow$ temp $\rightarrow$ opposed.

Merits

Circuit stabilizes the operating point against

Variations in temperature and β .

De-merits

I_C independent of β .

$\rightarrow$ Reduce voltage gain trade off

$\rightarrow$ Q. point stability

Merits

The circuit has the tendency to stabilize operating point against changes in temperature and β value.

De-merits,

$$I_C = \beta I_B = \frac{\beta (V_{CC} - V_{BE})}{R_B + (\beta + 1) R_E} \approx \frac{V_{CC} - V_{BE}}{R_E}$$

$$\therefore (\beta + 1) R_E \gg R_B$$

R_E causes the ac feedback which reduces the voltage gain.

Applications

* The feedback also increases the input impedance of the amplifier when seen from the base.

* Only can be used only with careful consideration of the trade-offs.

Collector ckt and emitter ckt related by $I_C = \alpha I_E$.

with $\alpha \approx 1$ so

Increase in emitter current with temp opposed.

* operating kept stable

$$V_{CC} = I_B R_B + V_{BE} + I_E R_E$$

$$I_E = I_B R_E$$

$$= V_{BE} + I_B R_B + (I_C + I_B) R_E$$

$$I_C + I_B$$

$$= V_{BE} + I_B R_B + I_B (\beta + 1) R_E$$

$$V_{CC} = V_{BE} + I_B [R_B + (\beta + 1) R_E]$$

$$I_B = \frac{V_{CC} - V_{BE}}{[R_B + (\beta + 1) R_E]} \rightarrow$$

Output Section.

$$I_C = \beta I_B$$

$$V_{CC} = V_{CE} + I_C R_C + I_E R_E$$


$$V_{CE} = V_{CC} - (I_C R_C + I_E R_E)$$

$$I_C \approx I_E$$

$$V_{CE} = V_{CC} - (I_C R_C + I_C R_E)$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Voltage divider Bias Method.

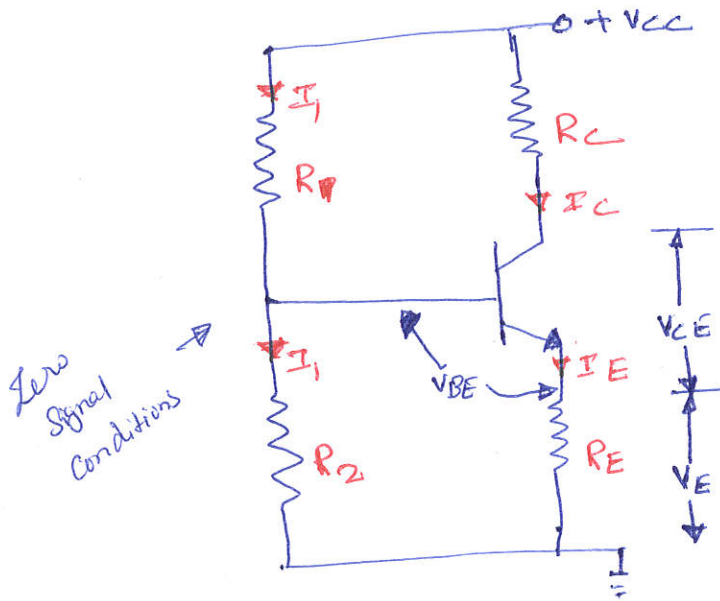

* Most widely used Method of providing biasing and stabilisation to a transistor.

* R_1 & R_2 provide Biasing

* R_E provide stabilisation.

* "Voltage divider" comes from the voltage divider formed by R_1 and R_2 .

Circuit analysis.

i) Collector current I_C

$$I_1 = \frac{V_{CC}}{R_1 + R_2}$$

$\therefore$ Voltage across Resistor R_2 is

$$V_2 = \left[\frac{V_{CC}}{R_1 + R_2} \right] R_2$$

or

$$V_E = I_E R_E$$

$$V_2 = V_{BE} + V_E \Rightarrow V_2 = V_{BE} + I_E R_E$$

$$I_E = \frac{V_2 - V_{BE}}{R_E}$$

$$I_E \approx I_C$$

$$I_C \approx \frac{V_2 - V_{BE}}{R_E}$$

I_C practically Independent of V_{BE}

* so due to I_C $\rightarrow$ provide good stabilisation is ensured.

* It is Universal Method for providing transistor biasing.

Collector emitter voltage, V_{CE}

Applying KVL to the collector side.

$$I_E \approx I_C$$

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E$$

$$= I_C R_C + V_{CE} + I_C R_E$$

$$= I_C (R_C + R_E) + V_{CE}$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$\therefore$ In this circuit Excellent stabilisation is provided by R_E .