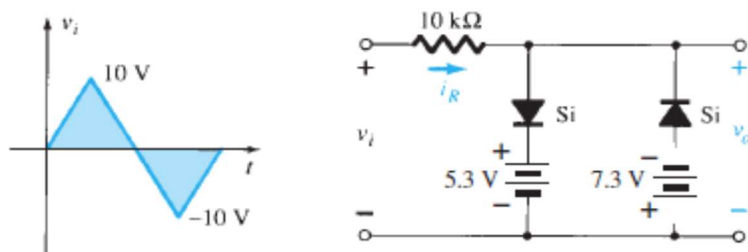



PART-A

- 1) Draw the symbolic representation of PNP and NPN transistor using PN diode. [2P]
- 2) Write any four fundamental differences between BJT and FET. [2P]
- 3) How the two transistor junctions to be biased for proper transistor amplifier? [2P]
- 4) Sketch i_R and v_o for the network of Fig. below for the input shown. [4P]




PART-B

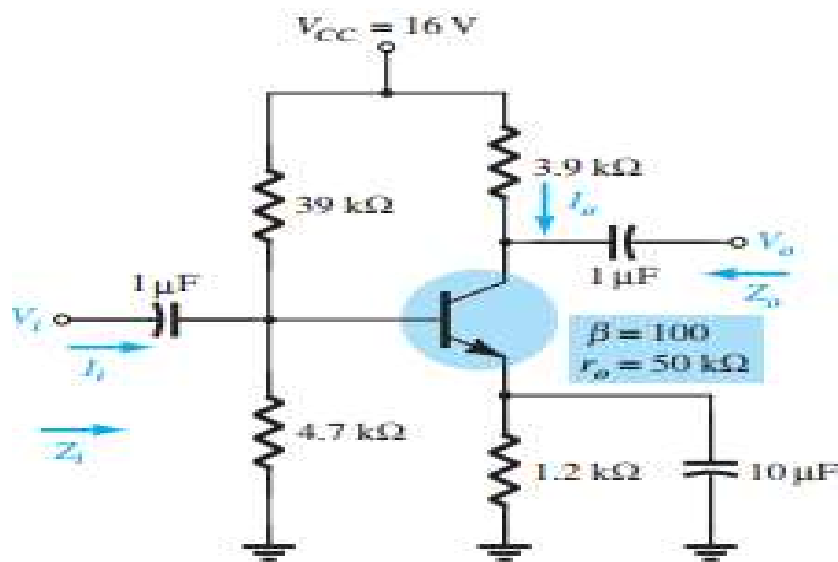
- 5) Determine R_C and R_B for a fixed-bias configuration if $V_{CC} = 12\text{ V}$, $\beta = 80$, and $I_{CQ} = 2.5\text{ mA}$ with $V_{CEQ} = 6\text{ V}$. [4P]
- 6) For the network given below, [8P]
 - a. Determine value of r_e .
 - b. Calculate Z_i and Z_o .
 - c. Find A_v and A_i
 - d. Draw AC small signal r_e model equivalent circuit



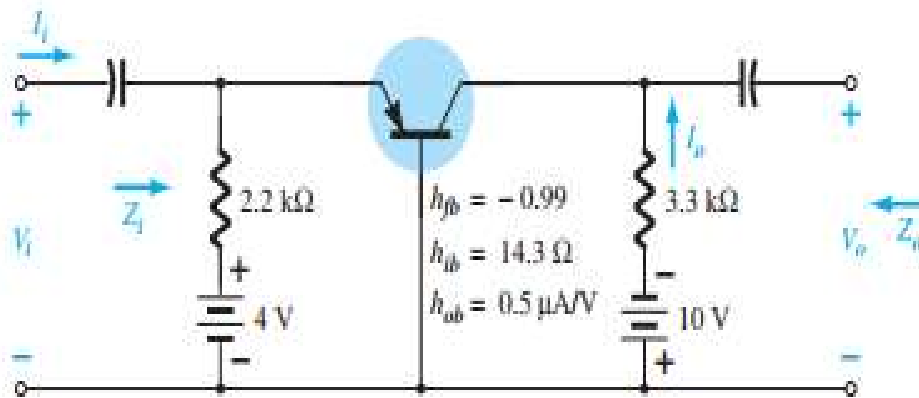- 7) For the network given below, [7P]
- Calculate Z_i and Z_o .
 - Find A_v and A_i
 - Draw AC small signal Hybrid equivalent circuit



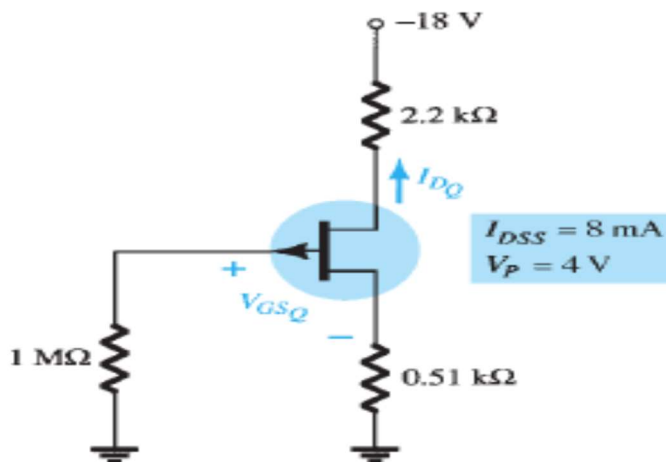- 8) For the network of Figure below, determine: [6P]
- I_{DQ} and V_{GSQ} .
 - V_{DS} .
 - V_D .





ADAMA SCIENCE & TECHNOLOGY UNIVERSITY
SCHOOL OF ELECTRICAL ENGINEERING & COMPUTING
DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING
COURSE: ELECTRONICS CIRCUITS-I (ECEG-2101)

YEAR/SEMESTER: 2ND / 1ST

FINAL EXAMINATION

Student Name: _____

Date: 15/04/2022

ID.No: _____

Duration: 3:00 Hours

Maximum points: 35

Instructions:

- Answer **ALL** Questions from PART I & PART II
- Not allowed to use **RED** pen
- No additional paper is allowed
- Do not detach the answer sheets from the question papers
- **Unreadable Answers will be subjected to point deduction**
- If required and necessary, 2 sides of the answer page can be used.

Question	Section-A	Section-B				Total
	1-4	5	6	7	8	
Weight	10	4	8	7	6	35
Score						

All the best!!!